 




Exploring the limits: Development of Integrated High-Speed Circuits

Prof. Dr. M. Möller
Saarland University
MICRAM Microelectronic GmbH




UNIVERSITÄT
DES
SAARLANDES

MICRAM
MICROELECTRONIC

Fig. 2

40th Anniversary – Moores Law Still Valid

M.Möller, Uni Saarland, MICRAM

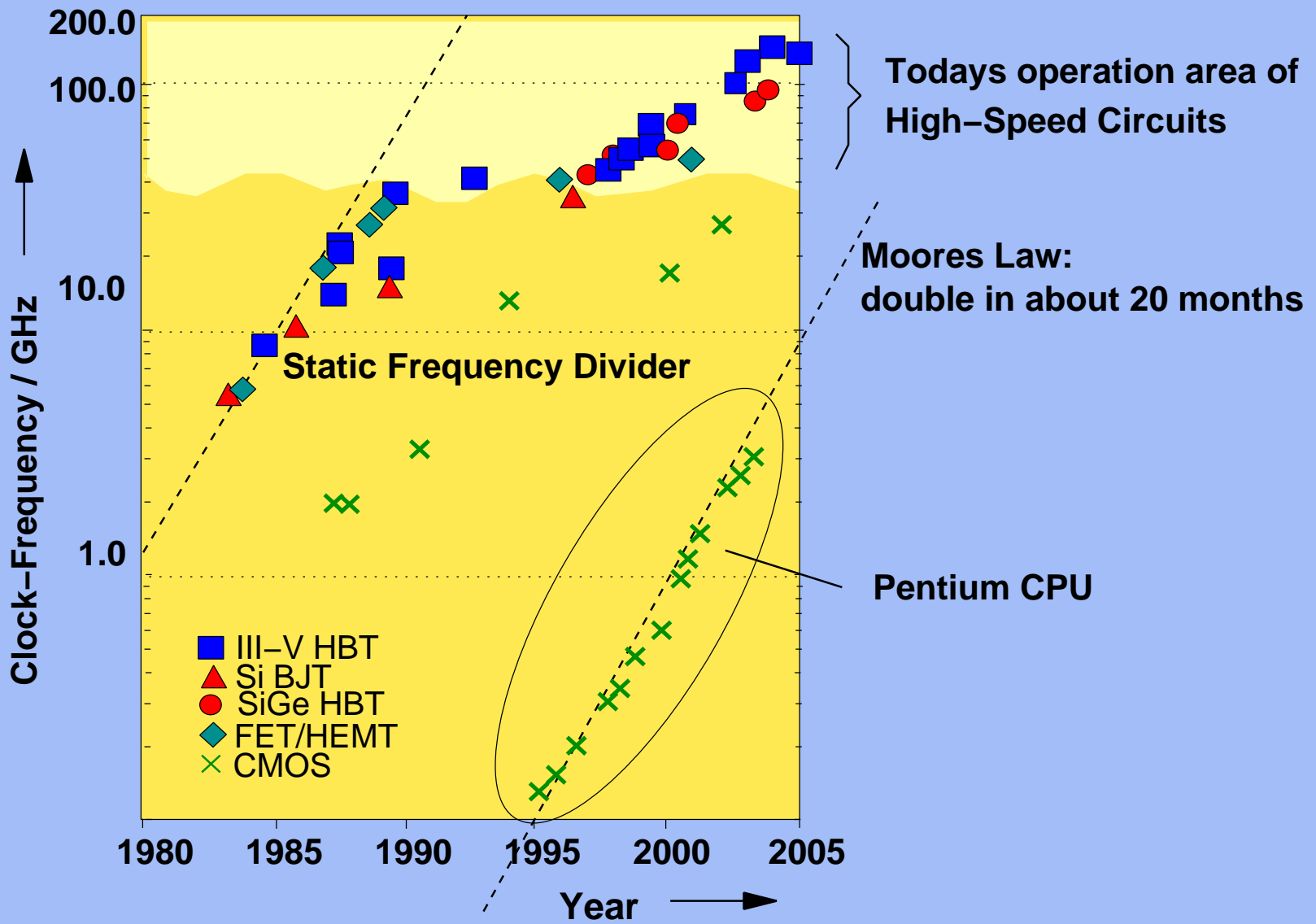


(Why) Does increase in speed slow down?

Fig. 3

Do we need (even) faster Semiconductor-Technologies?

M.Möller, Uni Saarland, MICRAM

 Maximum Static Divider Frequency in Si, SiGe und III/V Bipolar Technologies



Speed does not scale with transistor cut-off frequency – WHY ?

Fig. 4

Outline: Some Speed-Limiting Factors...

... And Ways to Surpass the Limits.





- How fast is the "intrinsic" transistor?
- Troublesome layout parasitics
- High Mismatch – High-Speed
- Borderline design: Speed-Optimisation
- Chip-Assembly – a multidisciplinary challenge
- Measurement setup – the Chicken and the Egg Dilemma
- Some latest 100 Gbit/s Receiver/Transmitter results

"A rough overview from the circuit designers perspective"

Fig. 4

What limits bipolar-transistor speed?

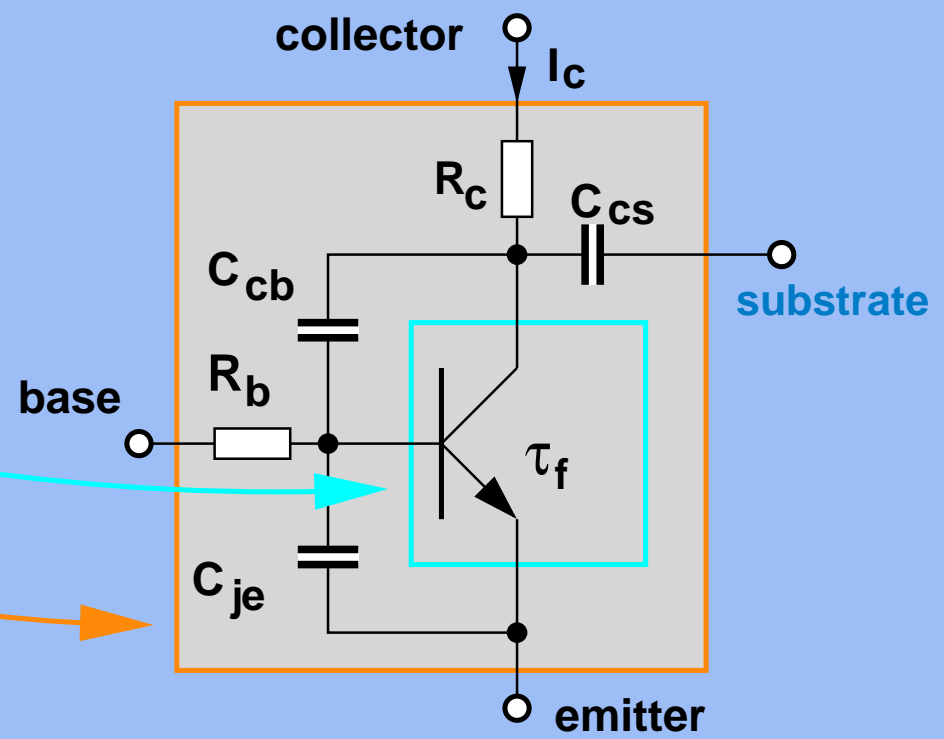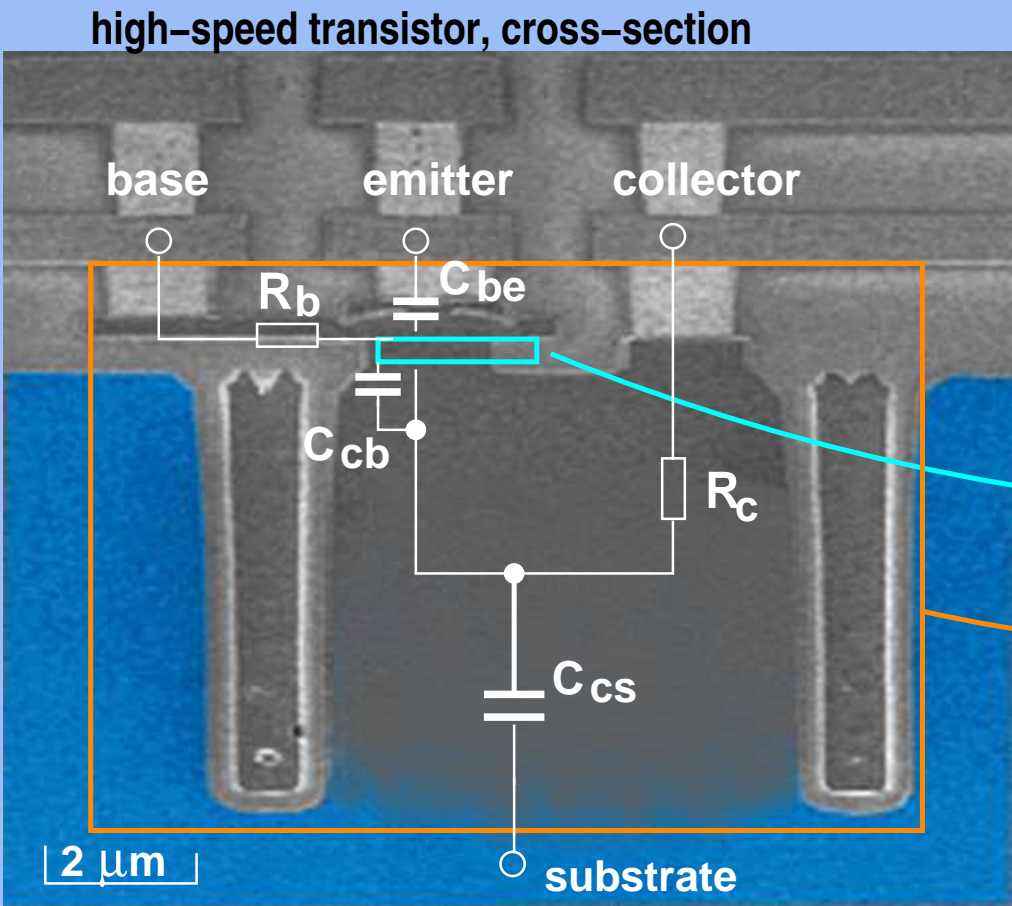

high cut-off frequencies, f_T f_{max} :

$$f_T \sim \frac{1}{\frac{C_{je}}{I_c} u_T + \tau_f + \dots}$$

$$f_{max} = \sqrt{\frac{f_T}{8 \pi R_b C_{cb}}}$$

- small R, C, τ → small transistor size
- high collector current I_c
- ➔ high current density

Higher Speed




Higher Current Density?


Fig. 6

Parasitic Capacitances of Transistor Metallization

M.Möller, Uni Saarland, MICRAM

 

short circuit at increasing frequency:

 

Electromigration determines minimum metal cross-section area

Capacity reduction by:

- lower dielectric constant
- thicker dielectric
- smaller metal width/area (eg. Copper insted of Aluminum)

Technological limit almost exhausted




New Materials/Technology

Fig. 7

Interconnect Parasitics Dominate Transistor Parasitics

M.Möller, Uni Saarland, MICRAM

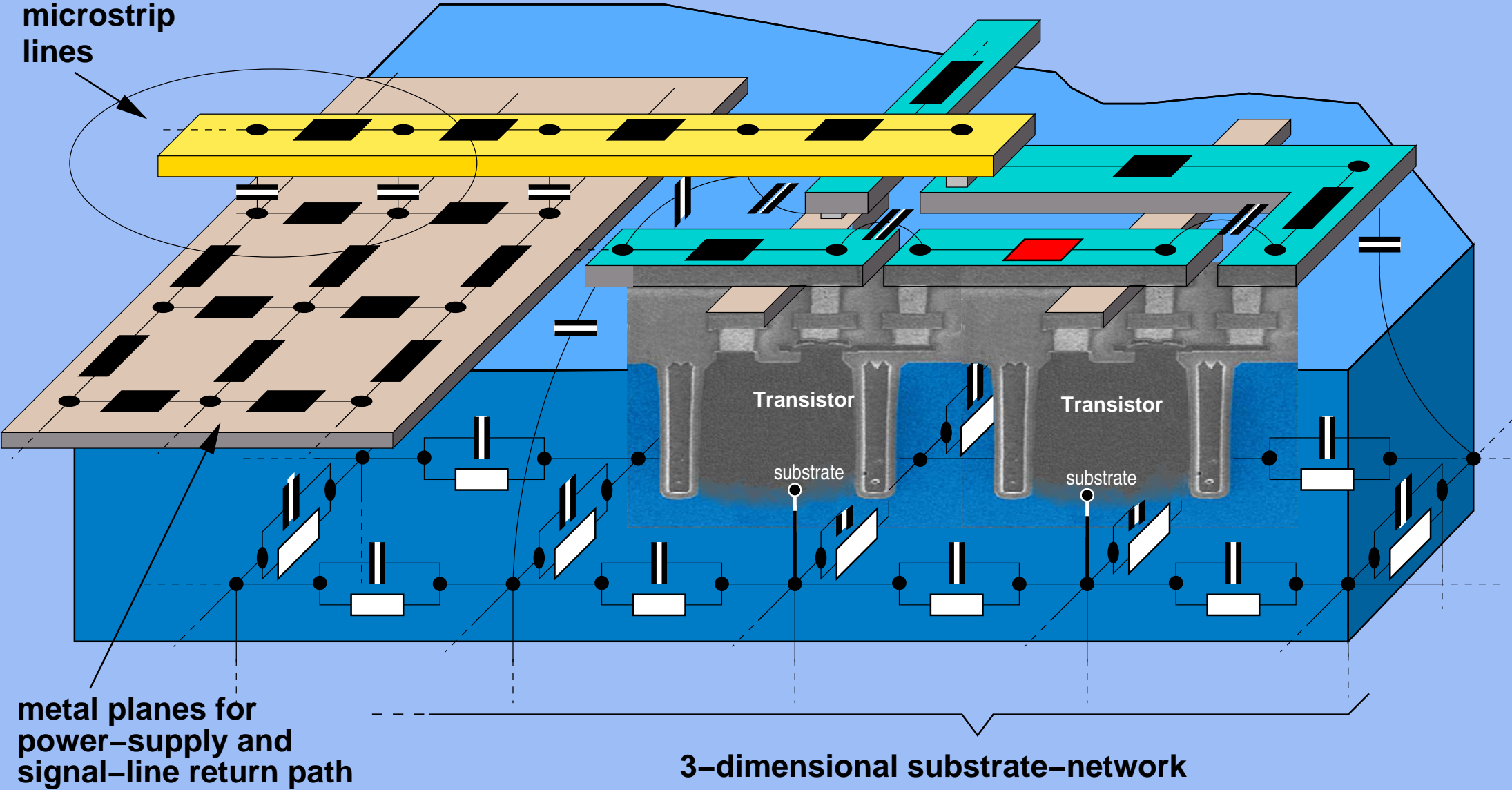


Layout: Very komplex 3-Dim. RLCM Network with major influence on the circuit's speed.

Fig. 8


Layout Determines Speed-Limit

M.Möller, Uni Saarland, MICRAM

 Example: Layout of 1:2 Clock Distribution Amplifier



metal stack:

 


Small parasitic C: small (tall) wires, thick oxide, low dielectric constant

Small parasitic L: broad wires (tradeoff with C), short wires (often not possible) \rightarrow L becomes critical!

Fig. 9

Optimization Goal: Short Wiring

M.Möller, Uni Saarland, MICRAM

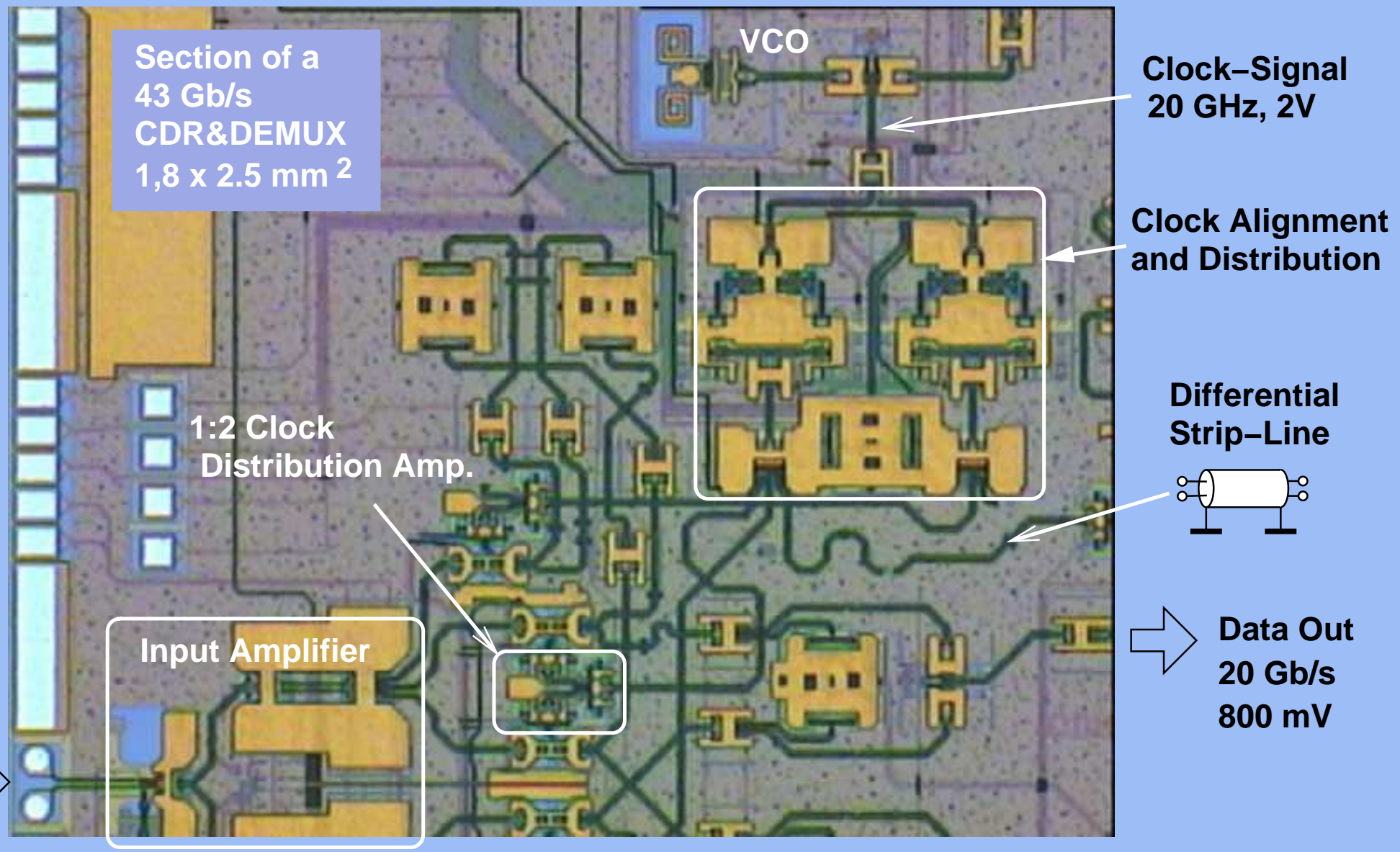

Constraints: Line lengths of dedicated signals must be at the same length

Fig. 10

Design Rules Impact on Speed

M.Möller, Uni Saarland, MICRAM



Optimization-Spiral

Device Size & Design Rules
(Max. Current densities ...
Min. Spacing/width, ...
Overlap, Doughnuts ...
Resistor type, sheet resistance...)

Driver power

Cell Size (L)

Transmission Line Lengths

 
 


High-Speed needs High-Support by Design Rules

Fig. 11

Bridgeover the Distance

  Constraint: Need for global metallization planes (Power supply planes) ➔ **Micro-Strip Lines (Supply plane is current return path)**



Example in Fig.:
 $ZL=50 \Omega \rightarrow 70 \Omega : h=2.2 \mu m \rightarrow 4.4 \mu m$

Line Impedance $ZL \sim \sqrt{\frac{L}{C}}$


- C ~ height "h"
- C ~ epsr
- L ~ 1/ line width ~ 1/C

thick dielectric & low epsr ➔ **high line impedance** ➔ **high bandwidth (speed) & high gain (low power)**

Range of height and epsr limited: $ZL < 80 \text{ Ohm}$

Fig. 12


Concept of Impedance Mismatch

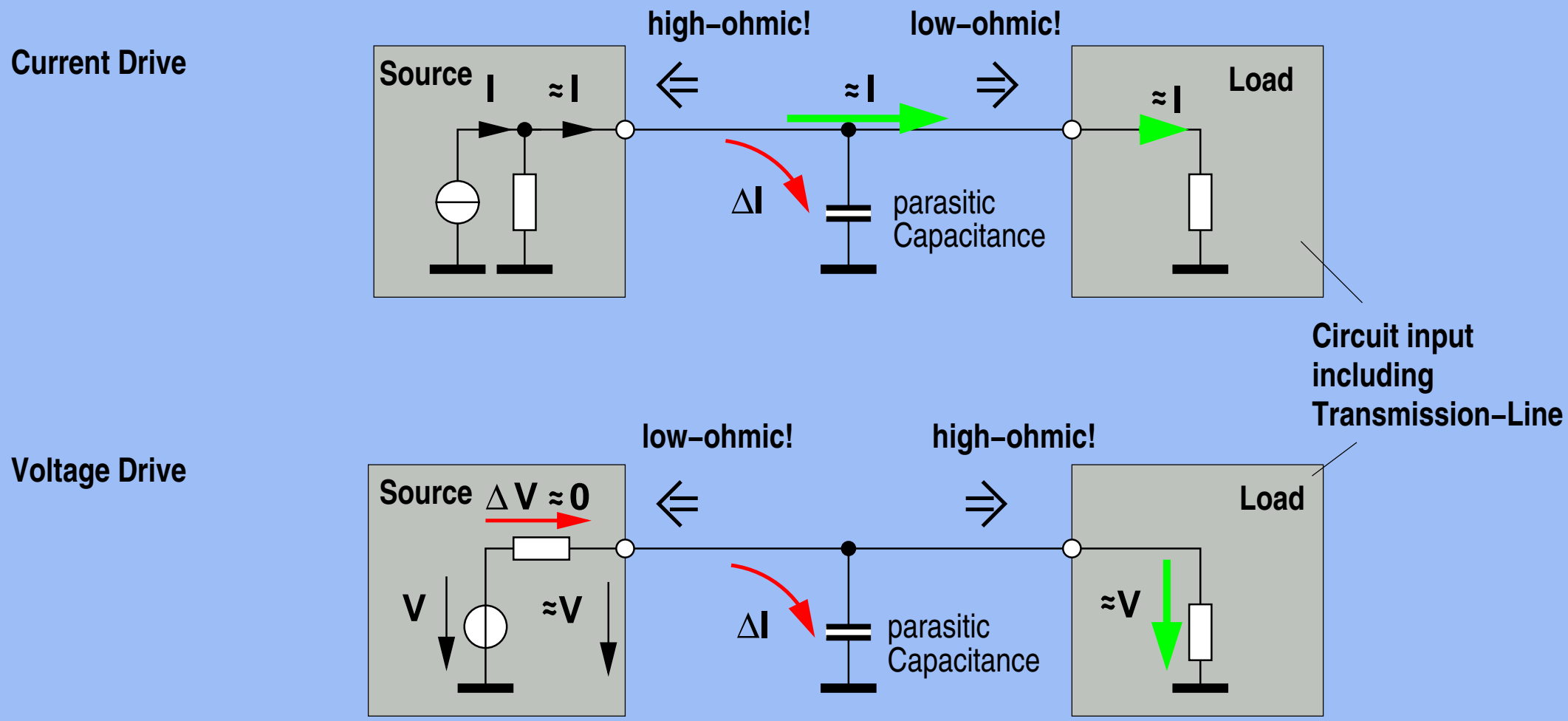

The More Mismatch \rightarrow The More Speed

High-Speed Circuit Topology

Example: Amplifier Stage



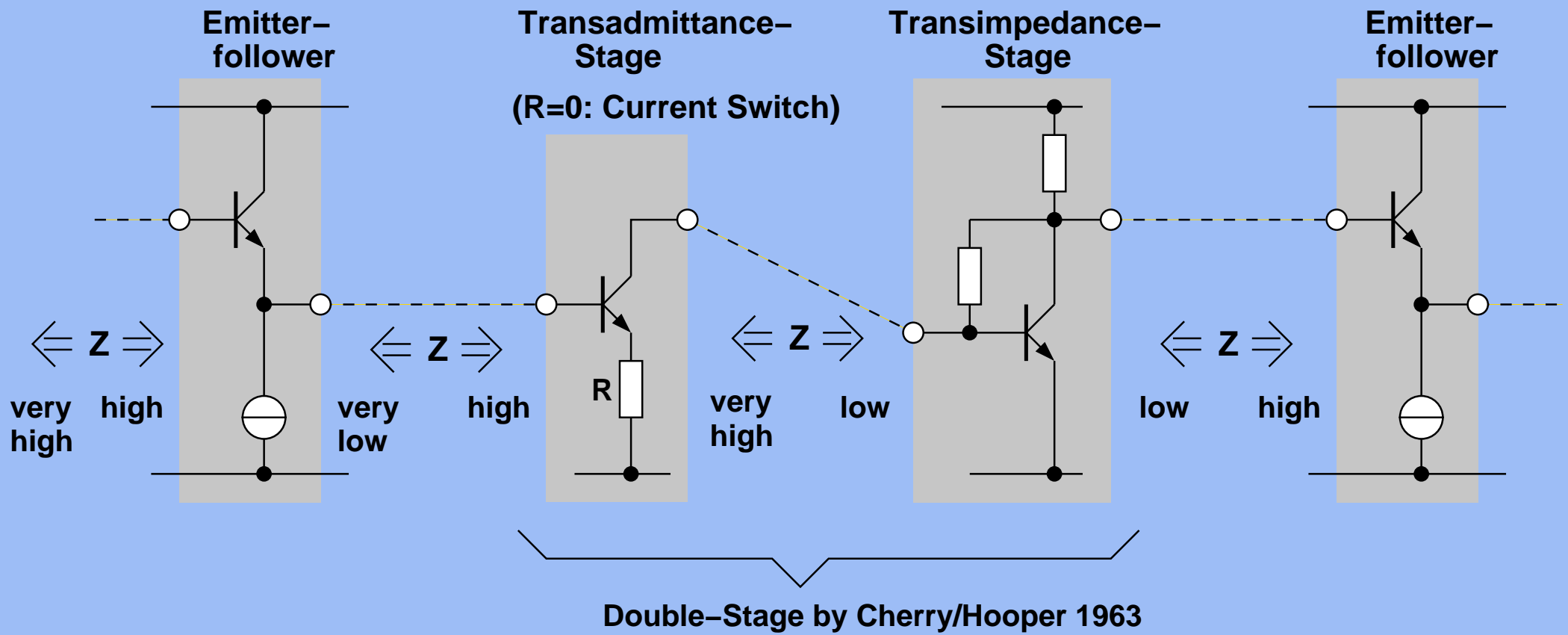


This is the Basic Principle Used in All High-Speed Circuits

Fig. 14

Complex-Conjugate Mismatch

M.Möller, Uni Saarland, MICRAM

 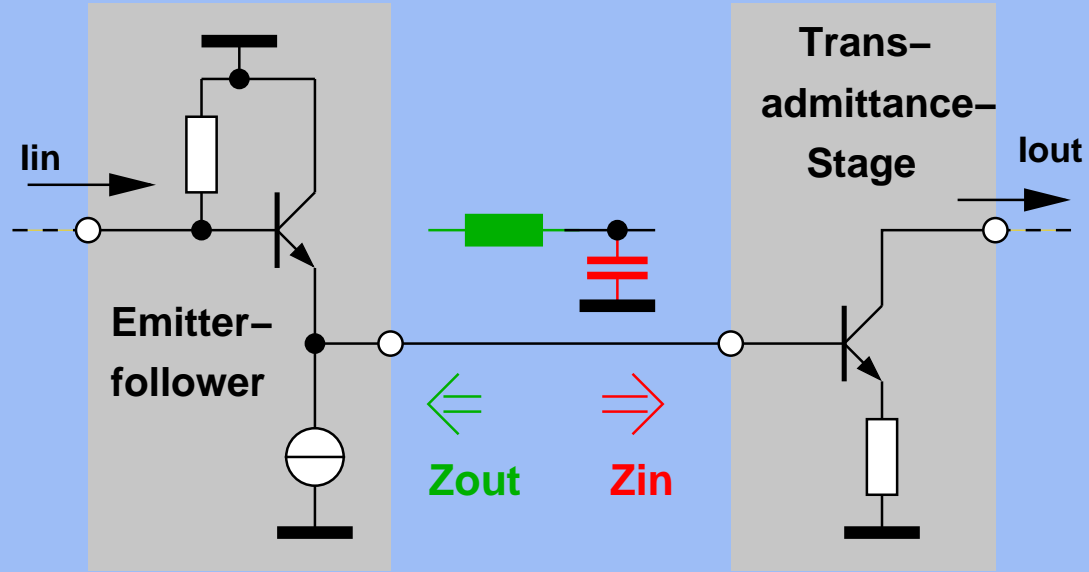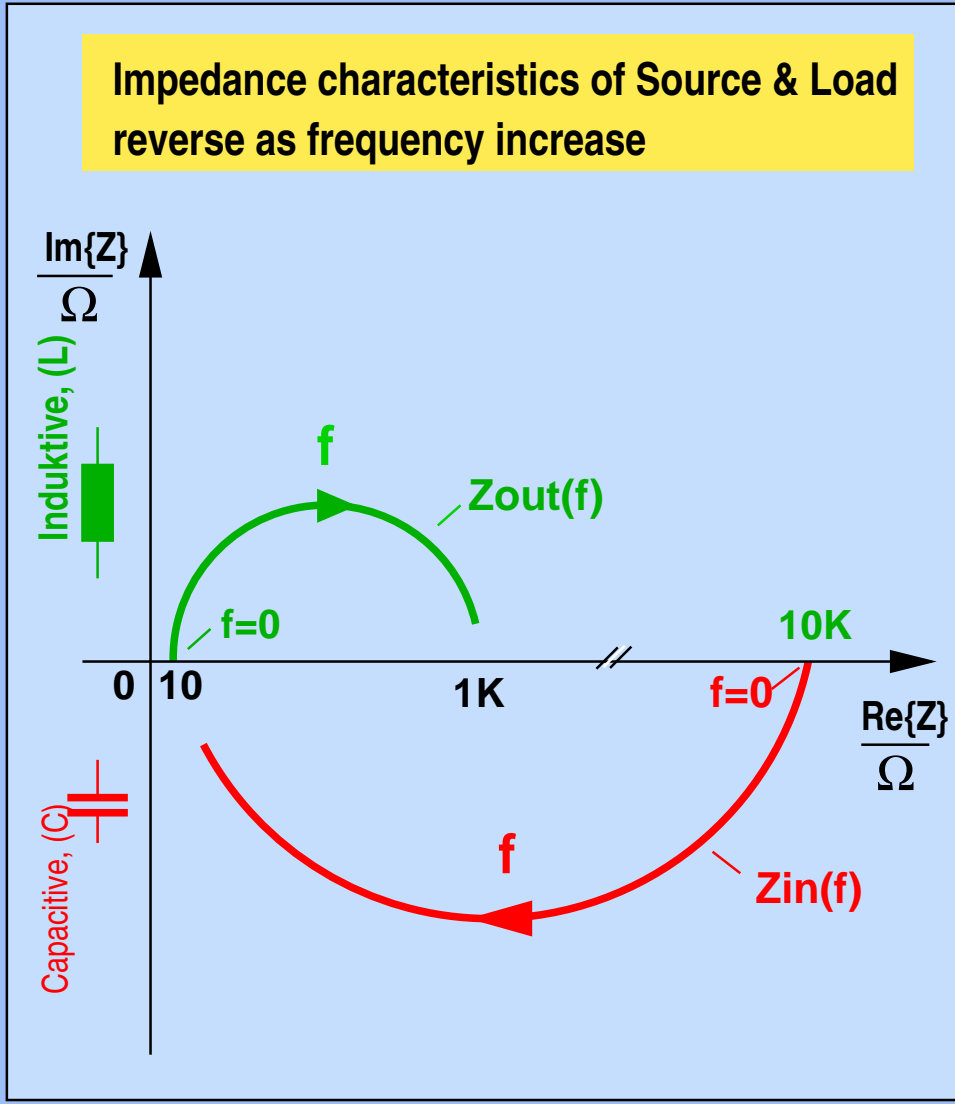

Utilize Complex-Conjugate Mismatch to Increase Speed

Fig. 15

Transistor = Impedance-Transformer




T-Operator:


$$T \approx \frac{f_t}{j \cdot f}$$

Multiplication by T rotates Z by -90° (clockwise)

 Impedances at the Base appear rotated by 90° at the Emitter:



 Impedances at the Emitter appear rotated by -90° at the Base:





Transformation Used to Optimize Pole/Zero Distribution of a Circuit

Fig. 16



Emitter-Follower Chain: A Tunable Resonance Network

M.Möller, Uni Saarland, MICRAM

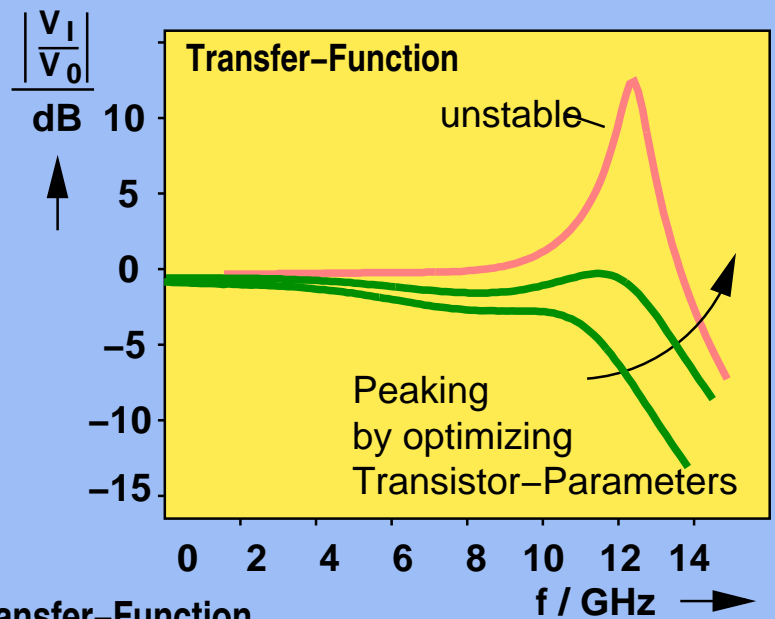 

Shifting Dominating Pole of Transfer-Function by Variation of EF1 Base Resistance

 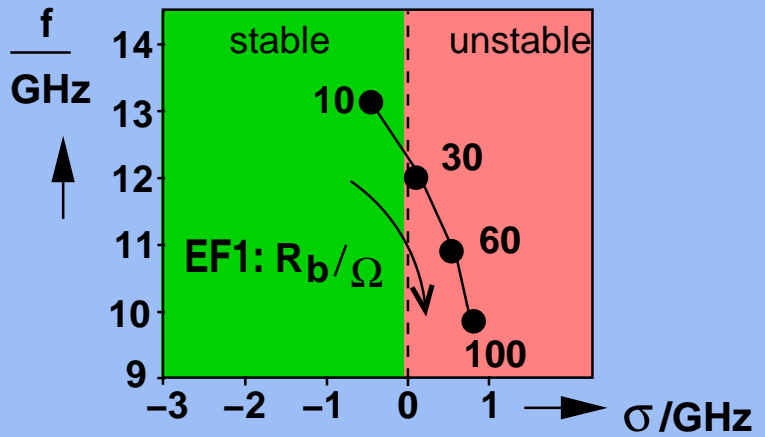Shifting Dominating Pole of Transfer-Function by Variation of EF3 Base Resistance




Great Opportunity to Increase Circuit Speed but ...




Fig. 17

Speed Optimized Circuits are Marginal Stable

M.Möller, Uni Saarland, MICRAM

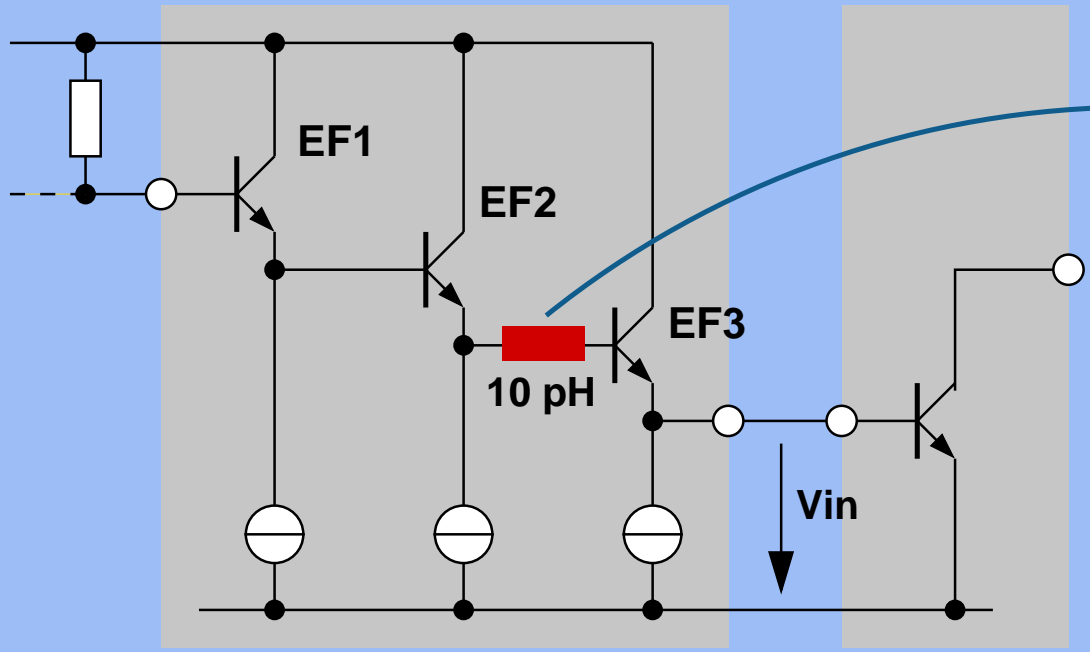

Layout:

 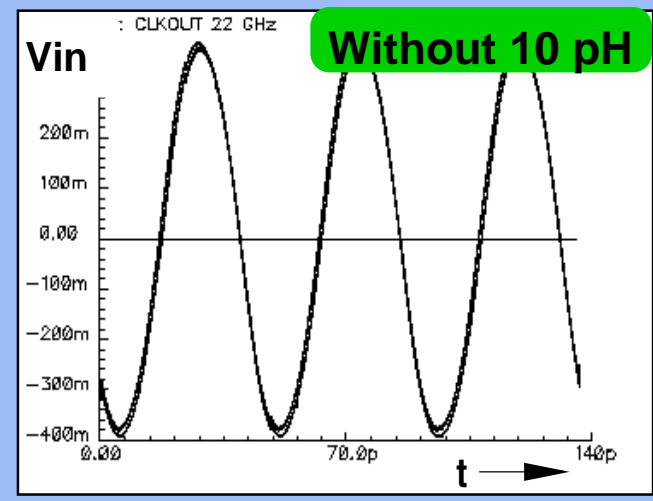 


Proof of Stability: Every Little Piece of Metal is Suspicious!
Feedback Path might be different than Signal Path


Fig. 18

Fast Technology: Low Breakdown Voltage (V_{CE0})

M.Möller, Uni Saarland, MICRAM

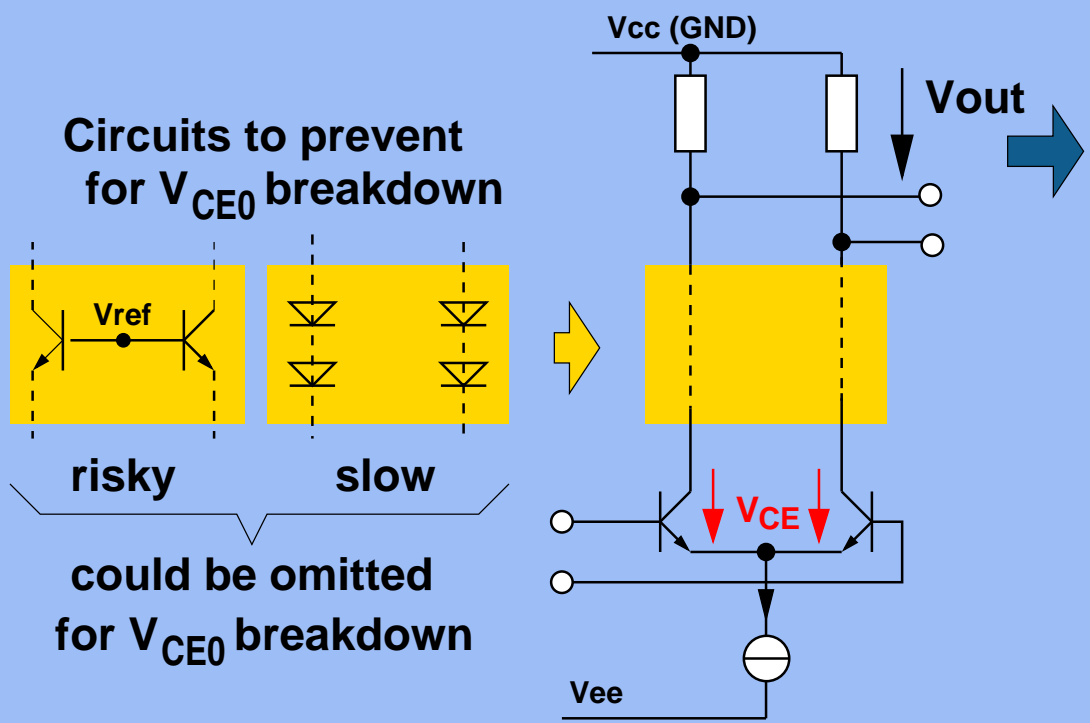

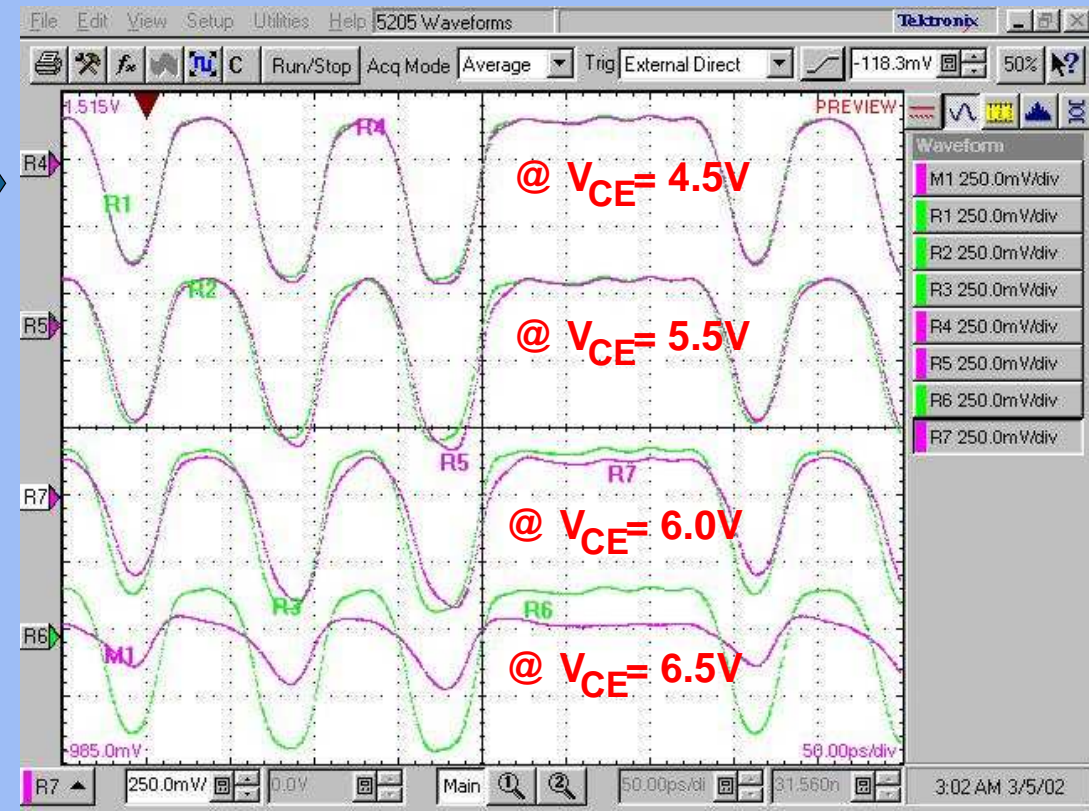Example:
 Limit given by technology $V_{CE0} = 2.5V$




Green trace: Reference Output-Voltage @ $V_{CE0} = 2.5V$

V_{CE0} Limit can be extended up to V_{CBO} by use of adequate Transistor-Models and Circuit Concepts

Fig. 19

Chip Assembly: High-Frequency Meets Precision Mechanics and Heat-Control

M.Möller, Uni Saarland, MICRAM

 

Design Goals: Small Inductances, High Thermal Conductivity

Fig. 20



Using Bondwires to Optimize the Strip-Line to Chip Interface

M.Möller, Uni Saarland, MICRAM

E.g.: Optimization of Refection Coefficient

Optimization goal:

 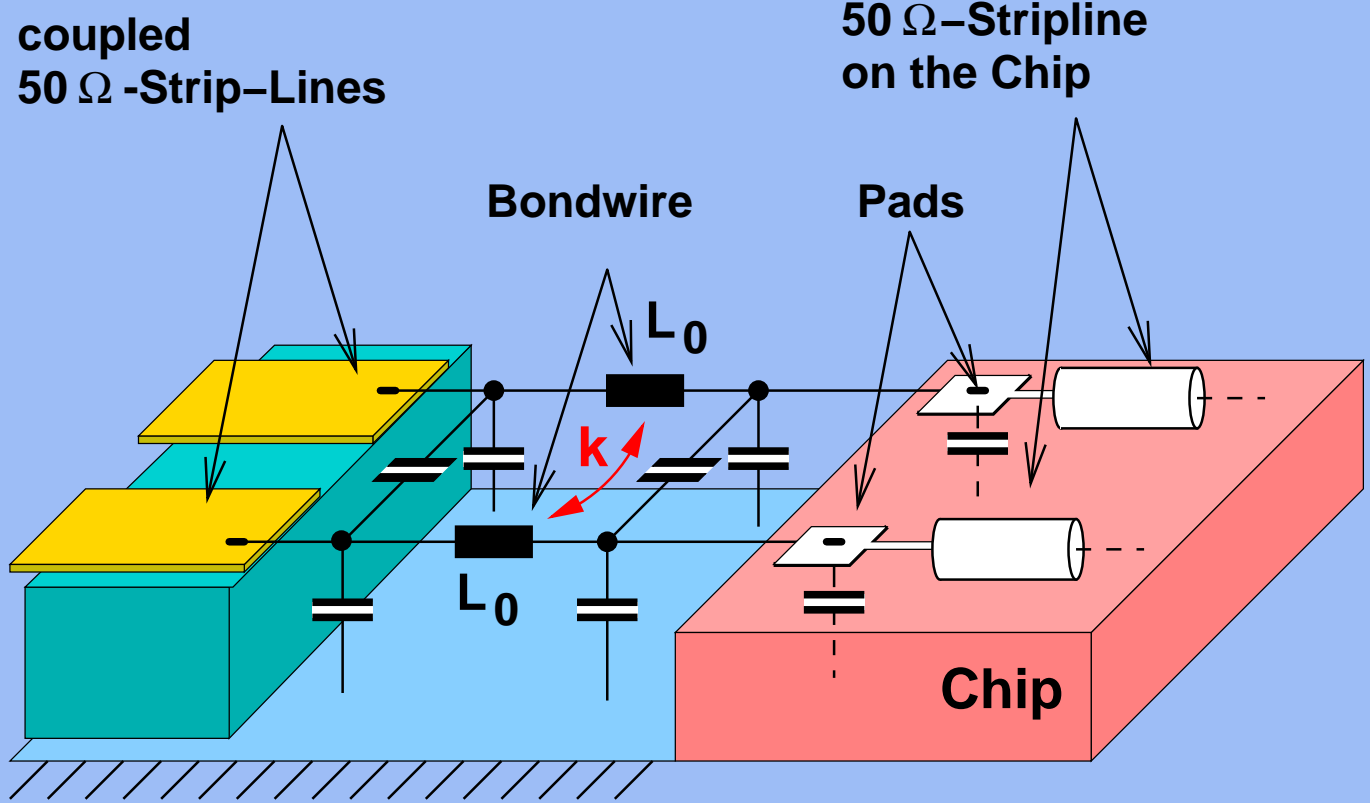
$$z_0^- \approx \sqrt{\frac{L^-}{\Sigma C^-}} \approx 50 \Omega$$



$L^- = (1-k) L_0$ Odd-Mode-Inductance L^- can be adjusted by bondwire spacing

Bondwire can be used also for Noise- and Pulsshape-Optimization

High Speed = High Power Consumption

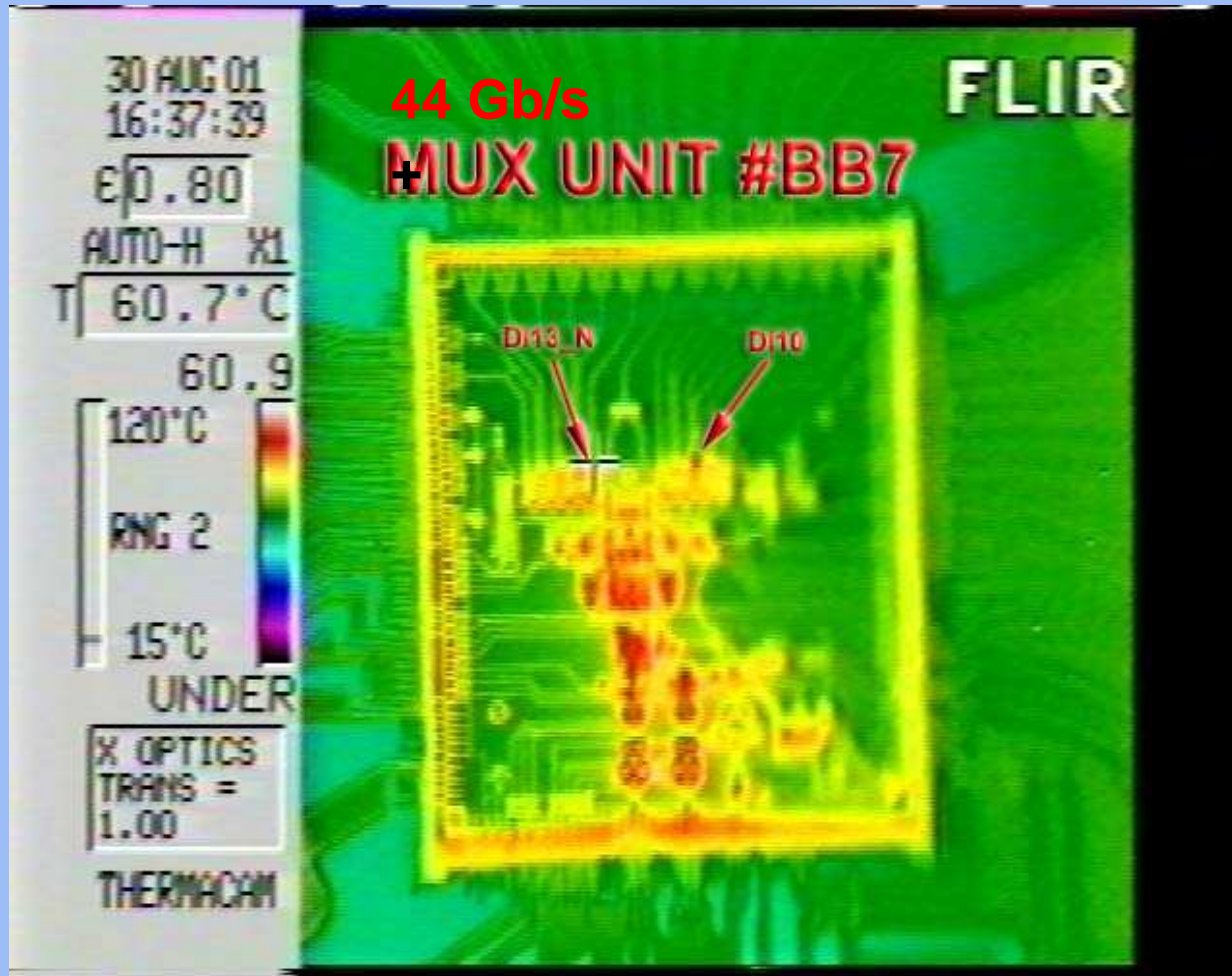

Power Density:

Chip:		Your kitchen hot-plate:
$1 \frac{\text{W}}{\text{mm}^2}$	\Leftrightarrow	$0.01 \frac{\text{W}}{\text{mm}^2}$

"Hot-Spots":

Areas of high power density lead to local heat concentration

"Self-heating"

Transistor heat up due to its own power

Time-constants in the ns-range!

Transistor cut-off frequency drops with increasing temperature:

Omit Hot-Spots \rightarrow Spread Elements / Distribute Power Over Chip Area \rightarrow But: Longer Wiring!

Fig. 23


Measurement of High-Speed Circuits

M.Möller, Uni Saarland, MICRAM

**Actual Example:
Measurement of 100 Gbit/s SerDes ASICs**

Agilent Sampling Scope
70 GHz, <300 fs Jitter

Agilent RF Generator 50 GHz

 

Agilent ParBert
8 Channels @ 12.5 Gbit/s
RZ-Patterns!

Agilent BERT
(12.5 Gbit/s)

Superposing 2 RZ Channels
12,5 Gbit/s → 25 Gbit/s

Testbench
& DUT

The Chicken and the Egg Dilemma

Fig. 24

Measurement of 100 Gbit/s MUX and CDR&DEMUX Modules


M.Möller, Uni Saarland, MICRAM

100 Gbit/s 2:1 MUX with automatic
Clock-to-Data Timing Alignment

100 Gbit/s TIA & DEMUX (& CDR)

Input
4 x 25 Gbit/s

Output
1x12.5 Gbit/s

 

Measurement Concept with Auxiliary Circuits Must be Considered During Circuit Design

Fig. 25

100 Gbit/s Output Eye Diagram of 2:1 MUX Module

M.Möller, Uni Saarland, MICRAM

- **Technologie:**
Infineon B10HF
 $f_T = 225 \text{ GHz}$
 $f_{max} = 300 \text{ GHz}$
- **Outputsignal:**
320 mVpp, single ended
< 400 fs Jitter

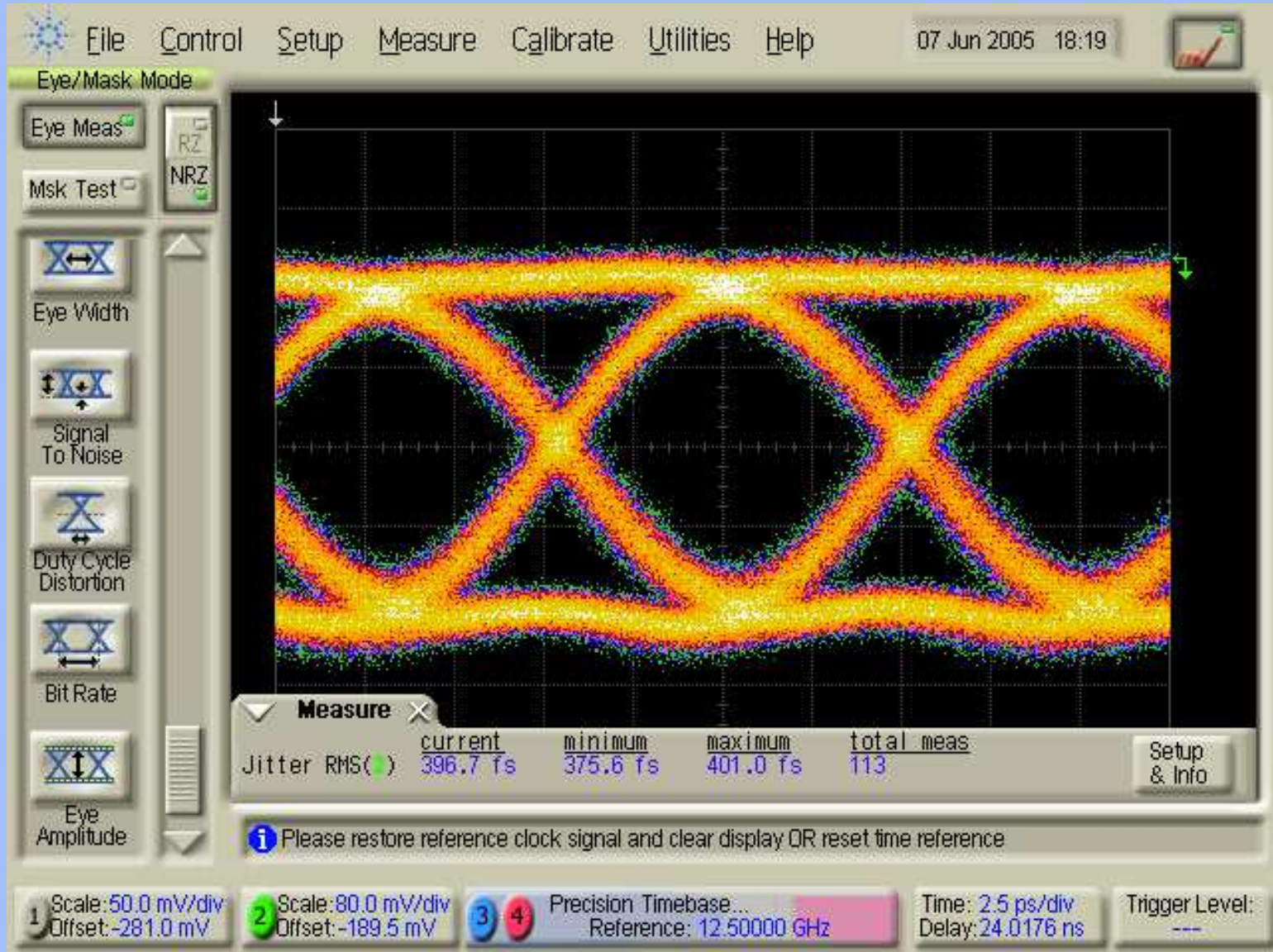


Fig. 26

86 Gbit/s Receiver (TIA, DEMUX, CDR, VCO) with On-Chip PLL


M.Möller, Uni Saarland, MICRAM

- German BMBF-Project:
MultiTeraNet

- Technology:
Infineon B10HF

Measurement Results:

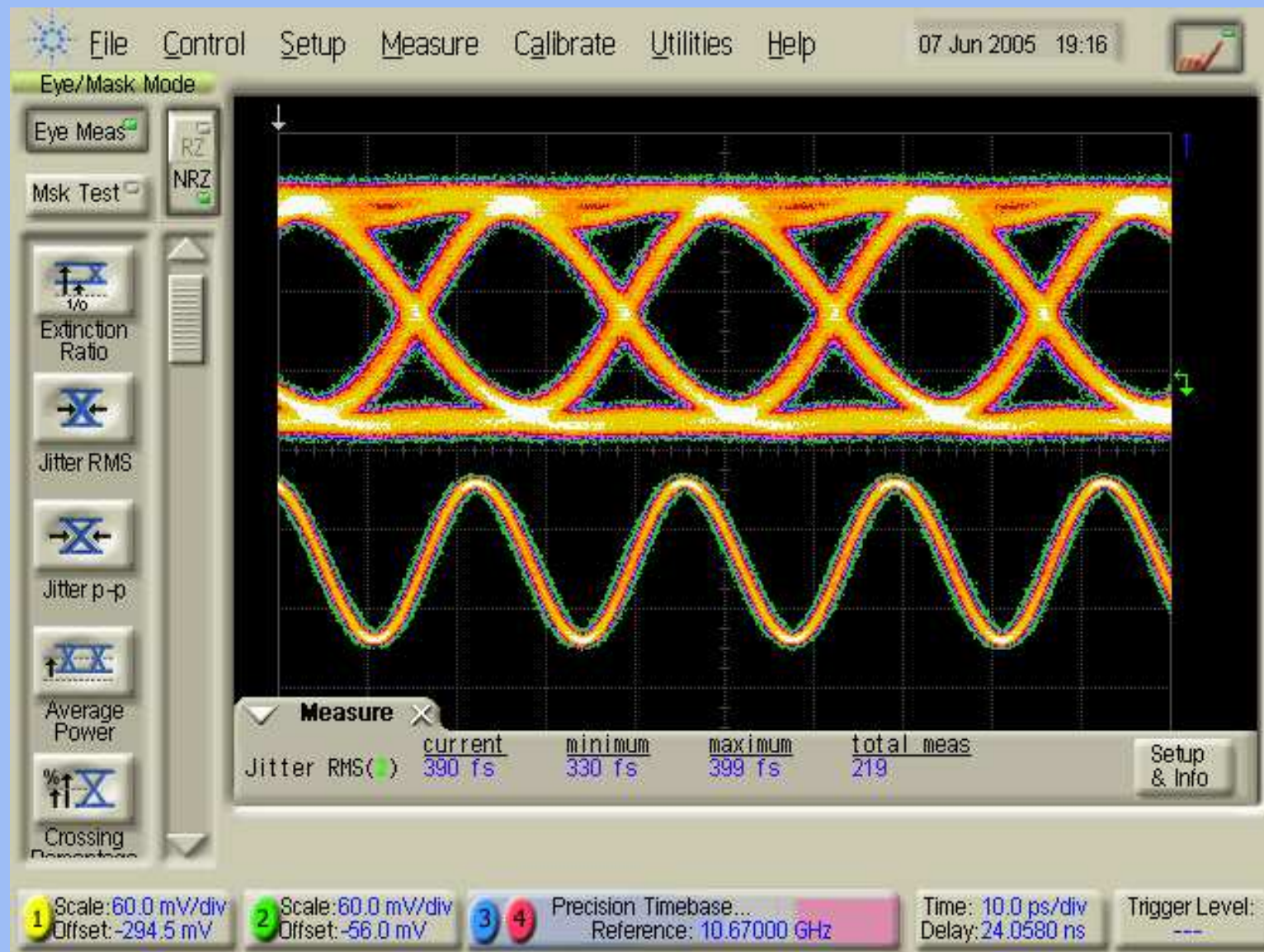- Min. Input Voltage (BER=0):
< 30 mV single ended
- Recovered Clock:
< 400 fs Jitter
- With Exteral VCO (50 GHz):
100 Gbit/s (BER=0)



That's it for Today – Thank You!