
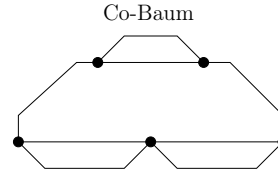


Aufgabe 1

a)


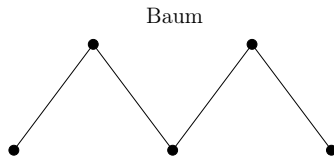


b)


Kobaum: 8 Zweige; 5 Ströme bekannt (Stromquellen) \Rightarrow 3 unabhängige Ströme

c)

umzeichnen:

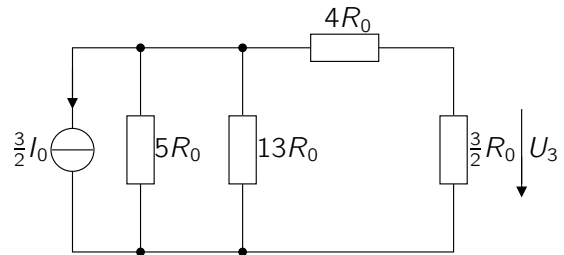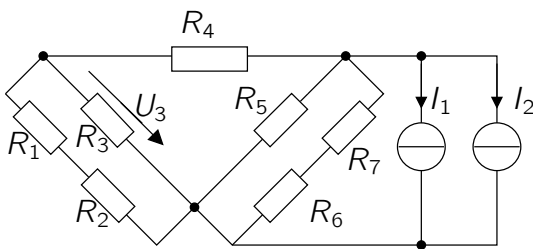
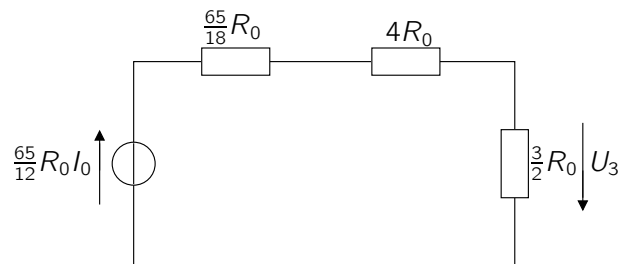
$$\frac{5R_0 13R_0}{5R_0 + 13R_0} = \frac{65}{18} R_0$$



$$\Rightarrow -U_3 = \frac{65}{12} R_0 I_0 \cdot \frac{\cancel{\frac{3}{2} R_0}}{(\frac{65}{18} + 4 + \frac{3}{2}) \cdot R_0} = \frac{65}{12} R_0 I_0 \cdot \frac{27}{65+72+27} = \frac{65}{4 \cdot 12} R_0 I_0 \cdot \frac{27}{164} = \frac{585}{656} R_0 I_0 \Rightarrow a = \frac{-585}{656}$$


Aufgabe 2

a)

$$\underline{Y}_x = j\omega C_k$$





$$\underline{Y}_y = \frac{1}{R_2 + (j\omega L // R_1)} = \frac{1}{R_2 + \frac{j\omega L R_1}{j\omega L + R_1}}$$

b)

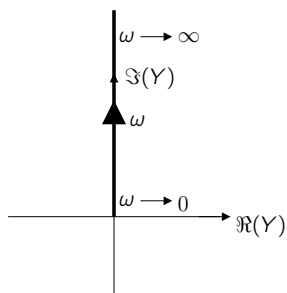

$$\underline{Y}_x(\omega = 0) = 0$$
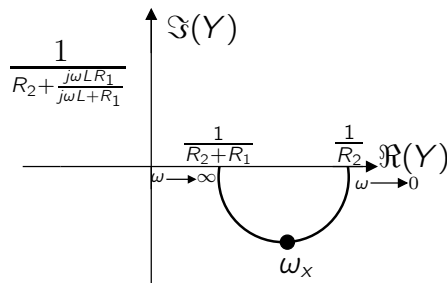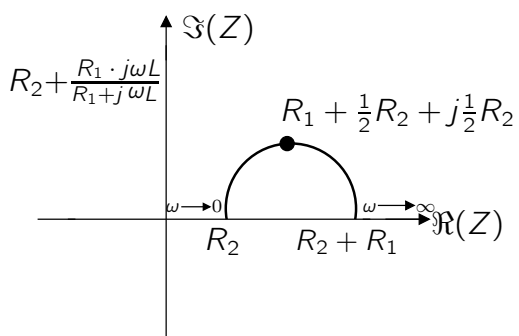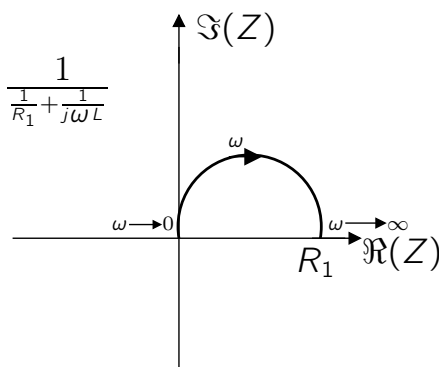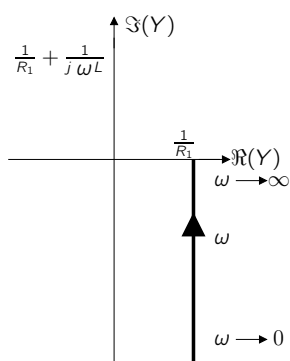
$$\underline{Y}_x(\omega \rightarrow \infty) = j\infty$$



$$\underline{Y}_y(\omega \rightarrow 0) = \frac{1}{R_2}$$

$$\underline{Y}_y(\omega \rightarrow \infty) = \frac{1}{R_2 + R_1}$$

bei ω_x gilt:

$$\Re(Y_y) = \frac{1}{2} \left(\frac{1}{R_1 + R_2} + \frac{1}{R_2} \right)$$

$$\Im(Y_y) = -\frac{1}{2} \left(\frac{1}{R_2} - \frac{1}{R_1 + R_2} \right)$$


c)

$$\omega C_k = -\Im(Y_y) = \frac{1}{2} \left(\frac{1}{R_2} - \frac{1}{R_1 + R_2} \right)$$

$$C_k = \frac{1}{\omega_k} \left(\frac{R_1 + R_2 - R_2}{R_2(R_1 + R_2)} \right) = \frac{1}{\omega_k} \cdot \frac{R_1}{R_2(R_1 + R_2)}$$

Aufgabe 3

a)

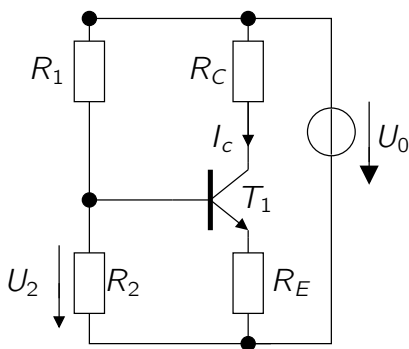

b)

$$R_C I_C = \frac{U_0}{2} = 10U_{BE} \Rightarrow I_C = \frac{10U_{BE}}{R_C}$$


$$U_2 = R_E I_E + U_{BE} \approx R_E I_C + U_{BE} =$$

$$\frac{R_C \cdot 10U_{BE}}{10 R_C} + U_{BE} = 2U_{BE}$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{U_2}{U_0} = \frac{2U_{BE}}{20U_{BE}} = \frac{1}{10}$$

$$\Leftrightarrow 10R_2 = R_1 + R_2 \Leftrightarrow 9R_2 = R_1 \Leftrightarrow R_2 = R_1 \frac{1}{9}$$

c)

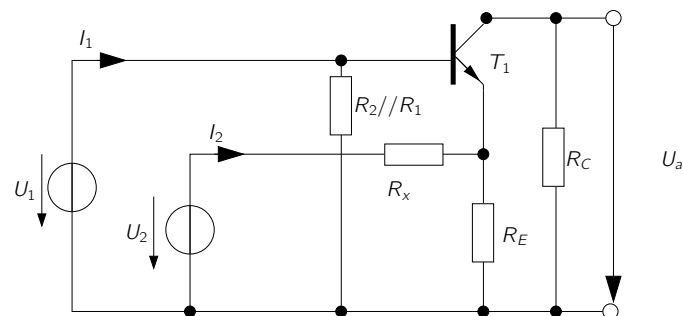


d)

$$U_2 = 0;$$

$$I_E = \frac{U_1}{r_e + R_E // R_x}$$

$$U_a = -I_C R_C = -I_E R_C = -\frac{R_C}{r_e + R_E // R_x} U_1$$

$$\left. \frac{U_a}{U_1} \right|_{U_2=0} = -\frac{R_C}{r_e + R_E // R_x}$$

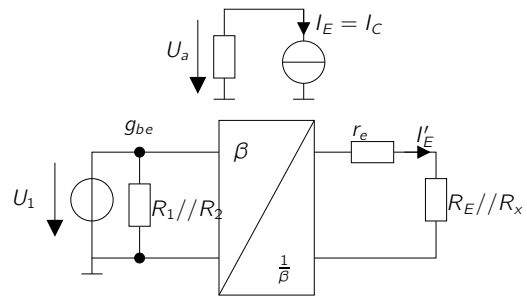

$$U_1 = 0$$


$$I_E = \frac{-\frac{1}{r_e}}{\frac{1}{r_e} + \frac{1}{R_E} + \frac{1}{R_x}} \cdot \frac{U_2}{R_x} = \frac{-1}{1 + \frac{r_e}{R_E} + \frac{r_e}{R_x}} \cdot \frac{U_2}{R_x}$$

$$= \frac{-1}{R_x(1 + \frac{r_e}{R_E}) + r_e} \cdot U_2$$

$$U_a = -I_C R_C = \frac{R_C}{R_x(1 + \frac{r_e}{R_E}) + r_e} \cdot U_2$$

$$\Rightarrow \left. \frac{U_a}{U_2} \right|_{U_1=0} = \frac{R_C}{R_x(1 + \frac{r_e}{R_E}) + r_e}$$
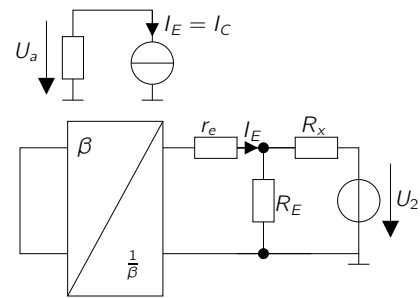
$$\Rightarrow U_a = -\frac{R_C}{r_e + R_E // R_x} U_1 + \frac{R_C}{R_x(1 + \frac{r_e}{R_E}) + r_e} U_2$$



e)

$$\frac{R_C}{r_e + R_E // R_x} \stackrel{!}{=} 1 \quad \frac{R_C}{R_x(1 + \frac{r_e}{R_E}) + r_e} \stackrel{!}{=} 1$$


$$\Rightarrow R_E // R_x = R_x(1 + \frac{r_e}{R_E}) \Rightarrow \frac{R_E}{R_x + R_E} = 1 + \frac{r_e}{R_E}$$

$$R_E \gg R_x, r_e \Rightarrow 1 = 1 \checkmark$$

$$\Rightarrow R_C = r_e + R_x$$

Aufgabe 4

a)

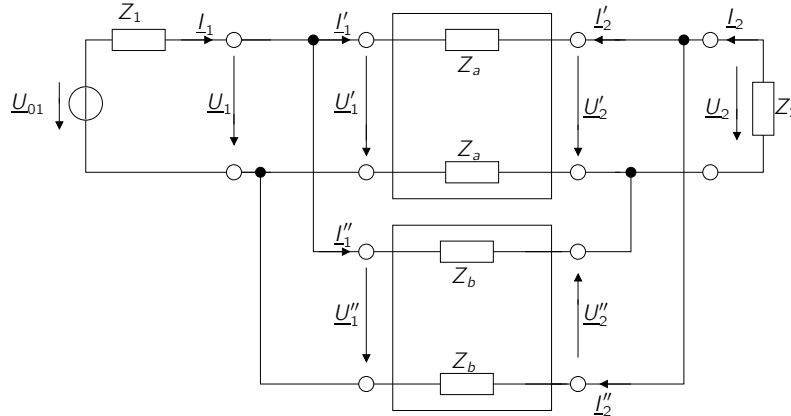

b)

i) PPK

ii) \underline{Y} -Parameter, weil

$$\underline{U}'_1 = \underline{U}''_1 = \underline{U}_1; \quad \underline{U}'_2 = \underline{U}''_2 = \underline{U}_2; \quad I_1 = I'_1 + I''_1; \quad I_2 = I'_2 + I''_2;$$

$$I_1 = Y'_{11} \underline{U}'_1 + Y''_{11} \underline{U}''_1 + Y'_{12} \underline{U}'_2 + Y''_{12} \underline{U}''_2 = Y'_{11} \underline{U}_1 + Y''_{11} \underline{U}_1 + Y'_{12} \underline{U}_2 + Y''_{12} \underline{U}_2 \\ = (Y'_{11} + Y''_{11}) \underline{U}_1 + (Y'_{12} + Y''_{12}) \underline{U}_2$$

$$I_2 = Y'_{21} \underline{U}'_1 + Y''_{21} \underline{U}''_1 + Y'_{22} \underline{U}'_2 + Y''_{22} \underline{U}''_2 = Y'_{21} \underline{U}_1 + Y''_{21} \underline{U}_1 + Y'_{22} \underline{U}_2 + Y''_{22} \underline{U}_2 \\ = (Y'_{21} + Y''_{21}) \underline{U}_1 + (Y'_{22} + Y''_{22}) \underline{U}_2$$

$$\Rightarrow \underline{Y} = \underline{Y}' + \underline{Y}''$$

c)

$$Y'_{11} = \left. \frac{I'_1}{U'_1} \right|_{U'_2=0} = \frac{1}{2Z_a} \quad Y'_{12} = \left. \frac{I'_1}{U'_2} \right|_{U'_1=0} = -\frac{1}{2Z_a} \\ Y'_{21} = \left. \frac{I'_2}{U'_1} \right|_{U'_2=0} = -\frac{1}{2Z_a} \quad Y'_{22} = \left. \frac{I'_2}{U'_2} \right|_{U'_1=0} = \frac{1}{2Z_a}$$

$$\Rightarrow \underline{Y}' = \frac{1}{Z_a} \begin{pmatrix} 1 & -1 \\ -1 & 1 \end{pmatrix}$$

$$\underline{Y}_{11}'' = \left. \frac{I_1''}{U_1''} \right|_{U_2''=0} = \frac{1}{2Z_b} \quad \underline{Y}_{12}'' = \left. \frac{I_1''}{U_2''} \right|_{U_1''=0} = \frac{1}{2Z_b}$$

$$\underline{Y}_{21}'' = \left. \frac{I_2''}{U_1''} \right|_{U_2''=0} = \frac{1}{2Z_b} \quad \underline{Y}_{22}'' = \left. \frac{I_2''}{U_2''} \right|_{U_1''=0} = \frac{1}{2Z_b}$$

$$\Rightarrow \underline{Y}' = \frac{1}{2Z_b} \begin{pmatrix} 1 & 1 \\ 1 & 1 \end{pmatrix}$$

$$\Rightarrow \underline{Y} = \underline{Y}' + \underline{Y}'' = \begin{pmatrix} \frac{1}{2Z_a} + \frac{1}{2Z_b} & \frac{1}{2Z_a} - \frac{1}{2Z_b} \\ \frac{1}{2Z_a} - \frac{1}{2Z_b} & \frac{1}{2Z_a} + \frac{1}{2Z_b} \end{pmatrix}$$

d)

$$I_1 = \underline{Y}_{11}U_1 + \underline{Y}_{12}U_2 = \underline{Y}_{11}U_1 - \underline{Y}_{12}Z_2I_2$$

$$I_2 = \underline{Y}_{21}U_1 + \underline{Y}_{22}U_2 = \underline{Y}_{21}U_1 - \underline{Y}_{22}Z_2I_2 \Rightarrow I_2(1 + \underline{Y}_{22}Z_2) = \underline{Y}_{21}U_1$$

$$\Rightarrow \frac{I_1}{I_2} = \underline{Y}_{11} \frac{(1 + \underline{Y}_{22}Z_2)}{\underline{Y}_{21}} - \underline{Y}_{12}Z_2$$

$$\Rightarrow \underline{E}_I = \frac{I_2}{I_1} = \frac{1}{\underline{Y}_{11} \frac{(1 + \underline{Y}_{22}Z_2)}{\underline{Y}_{21}} - \underline{Y}_{12}Z_2} = \frac{\underline{Y}_{21}}{\underline{Y}_{11}(1 + \underline{Y}_{22}Z_2) - \underline{Y}_{21}\underline{Y}_{12}Z_2}$$

$$\underline{E}_I = 0 \text{ für } \underline{Y}_{21} = 0 \iff \frac{1}{2Z_b} = \frac{1}{2Z_a} \iff Z_a = Z_b$$

Aufgabe 5

a)

$$z(s) = \frac{1}{sC + \frac{1}{R+sL} + \frac{1}{r_x}} = \frac{(R+sL)r_x}{sC(R+sL)r_x + r_x + R+sL}$$

b)

Spannung soll oszillieren \Rightarrow schlieÙe hochomige Last an Oszillator an
 $\Rightarrow \underline{I} \mapsto 0 \quad \underline{U} = \underline{I} \cdot \underline{Z} \neq 0$ für Pole von \underline{Z}

c)

$$\begin{aligned} Z(s) &= \frac{(R+sL)r_x}{sC(R+sL)r_x + r_x + R+sL} \\ &\Rightarrow sCRr_x + s^2CLr_x + r_x + R + sL \stackrel{!}{=} 0 \\ &\Rightarrow s^2CLr_x + s \cdot (CRr_x + L) + r_x + R = 0 \\ &\Rightarrow s^2 + s \frac{CRr_x + L}{CLr_x} + \frac{r_x + R}{CLr_x} = 0 \\ s_{1/2} &= -\frac{1}{2} \cdot \frac{CRr_x + L}{CLr_x} \pm \sqrt{\left(\frac{CRr_x + L}{2CLr_x}\right)^2 - \frac{r_x + R}{CLr_x}} \end{aligned}$$


d)

konstante Amplitude wenn $\Re(s) = 0 = \sigma = \frac{R}{L} + \frac{1}{r_x C} \Rightarrow \frac{1}{r_x} = -\frac{RC}{L} \Rightarrow r_x = -\frac{L}{RC}$

e)

Schwingfrequenz: $s = \sigma + j\omega = 0 + j\sqrt{\frac{r_x+R}{CLr_x}}$ mit $\frac{r_x+R}{CLr_x} > 0 \rightarrow \omega = \sqrt{\frac{1}{CL}\left(1 + \frac{R}{r_x}\right)}$

f)

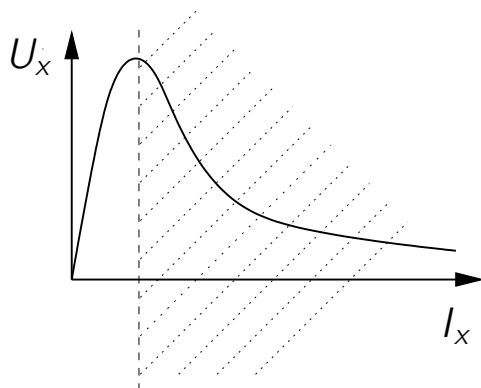

g)

$$\begin{aligned} r_x &= -\frac{L}{CR} = \frac{dU}{dI} \Big|_{AP} = \frac{(1+bl_x^2)a - 2bl_xal_x}{(1+bl_x^2)^2} \\ &\Rightarrow (1+bl_x^2)a - 2abl_x^2 = r_x(1+2bl_x^2 + b^2l_x^4) \\ &\Rightarrow l_x^4 + \left(\frac{2}{b} + \frac{a}{br_x}l_x^2\right) - \frac{a}{b^2r_x} \\ &\Rightarrow l_x^2 = -\left(\frac{1}{b} + \frac{a}{2br_x}\right) \pm \sqrt{\left(\frac{1}{b} + \frac{a}{2br_x}\right)^2 + \frac{a}{b^2r_x}} \\ &\Rightarrow l_x = +\sqrt{-\left(\frac{1}{b} + \frac{a}{2br_x}\right) + \sqrt{\left(\frac{1}{b} + \frac{a}{2br_x}\right)^2 + \frac{a}{b^2r_x}}} \end{aligned}$$


Aufgabe 6

a)

Torpaar 1 : $U_3 = U_4 = 0$



Torpaar 2 : $U_1 = U_2 = 0$
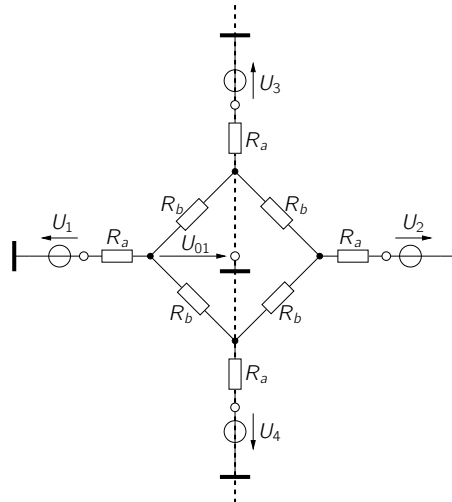
$$\begin{aligned} U_{12}^+ &= \frac{U_1 + U_2}{2} & U_{12}^- &= \frac{U_1 - U_2}{2} \\ U_{34}^+ &= \frac{U_4 + U_3}{2} & U_{43}^- &= \frac{U_4 - U_3}{2} \end{aligned}$$




b)

betrachte Torpaar 1 ,
Gleichtakt:

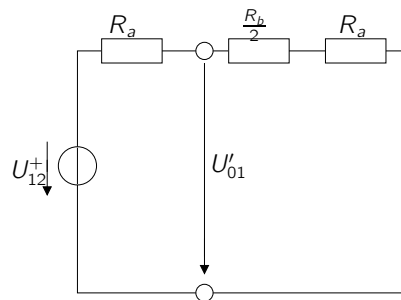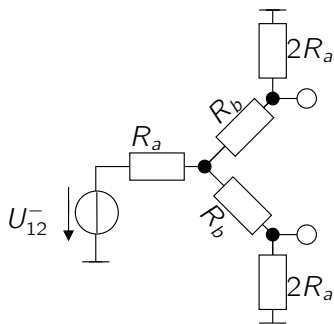


$$\Rightarrow U'_{01} = \underbrace{\frac{\frac{R_b}{2} + R_a}{\frac{R_b}{2} + 2R_a}}_{H_{12}^+} U_{12}^+$$

Gegentakt:

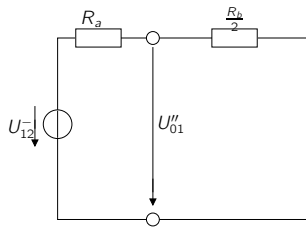


$$\Rightarrow U_{01}'' = \underbrace{\frac{R_b}{2R_a + R_b}}_{H_{12}^-} U_{12}^-$$

betrachte Torpaar 2,
Gleichtakt:

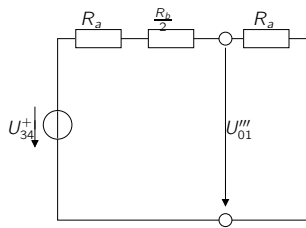

$$\Rightarrow U_{01}''' = \underbrace{\frac{R_a}{\frac{R_b}{2} + 2R_a}}_{H_{34}^+} U_{34}^+$$

Gegentakt:

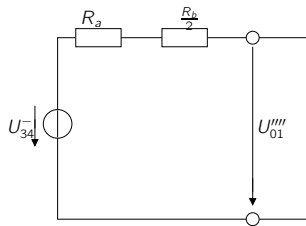

$$\Rightarrow U_{01}'''' = \underbrace{0}_{H_{34}^-}$$

$$\begin{aligned} \Rightarrow U_{01} &= H_{12}^+ U_{12}^+ + H_{12}^- U_{12}^- + H_{34}^+ U_{34}^+ + 0 \\ &= \frac{H_{12}^+ + H_{12}^-}{2} U_1 + \frac{H_{12}^+ - H_{12}^-}{2} U_2 + \frac{H_{34}^+ U_3}{2} + \frac{H_{34}^+ U_4}{2} \\ &= \left(\frac{\frac{R_b}{2} + R_a}{\frac{R_b}{2} + 2R_a} + \frac{R_b}{2R_a + R_b} \right) U_1 + \left(\frac{\frac{R_b}{2} + R_a}{\frac{R_b}{2} + 2R_a} - \frac{R_b}{2R_a + R_b} \right) U_2 + \frac{R_a}{\frac{R_b}{2} + 2R_a} U_3 + \frac{R_a}{\frac{R_b}{2} + 2R_a} U_4 \end{aligned}$$

Aufgabe 7

a)

$$\frac{U_p}{U_1} = \frac{Z_2}{Z_1 + Z_2}$$

$$U_p = U_d + U_e \Leftrightarrow U_d = U_p - U_e$$

$$U_2 = v_u U_d \frac{Z_e}{R_a + Z_e} \Leftrightarrow U_2 = v_u (U_p - U_e) \frac{Z_e}{R_a + Z_e}$$

$$\Rightarrow U_2 (1 + v_u \frac{Z_e}{R_a + Z_e}) = U_p v_u \frac{Z_e}{R_a + Z_e}$$

$$\frac{U_2}{U_p} = \frac{v_u \frac{Z_e}{R_a + Z_e}}{1 + v_u \frac{Z_e}{R_a + Z_e}}$$

$$\Rightarrow F = \frac{U_p}{U_1} \frac{U_2}{U_p} = \frac{Z_2}{Z_1 + Z_2} \cdot \frac{v_u \frac{Z_e}{R_a + Z_e}}{1 + v_u \frac{Z_e}{R_a + Z_e}}$$

c)

$$\Rightarrow F_k = \frac{\alpha R_1 \gg R_a}{(1+\alpha)^2} \frac{j\omega R_2 C_1}{(1+j\omega R_2 C_1)(j\omega R_1 C_2 + 1)}$$

$$\Rightarrow R_2 C_1 = \frac{10}{\omega_0} \quad R_2 C_1 = \frac{1}{10\omega_0}$$

b)

$$F_k = \frac{Z'_2}{Z'_1 + Z'_2} \frac{v'_u \frac{Z'_e}{R_a + Z'_e}}{1 + v'_u \frac{Z'_e}{R_a + Z'_e}} \cdot \frac{Z''_2}{Z''_1 + Z''_2} \frac{v''_u \frac{Z''_e}{R_a + Z''_e}}{1 + v''_u \frac{Z''_e}{R_a + Z''_e}}$$

$$Z'_1 = \frac{1}{j\omega C_1}; Z'_2 = R_2; Z''_1 = R_1; Z''_2 = \frac{1}{j\omega C_2}; |Z_e| \mapsto \infty;$$

$$Z'_e = Z''_1 + Z''_2 = R_1 + \frac{1}{j\omega C_2};$$

$$v'_u = v''_u = \alpha \in \mathbb{R}, \alpha \gg 1$$

$$F_k \stackrel{|Z_e| \mapsto \infty}{\approx} \frac{R_2}{R_2 + \frac{1}{j\omega C_1}} \frac{\alpha \frac{R_1 + \frac{1}{j\omega C_2}}{R_a + R_1 + \frac{1}{j\omega C_2}}}{1 + \alpha \frac{R_1 + \frac{1}{j\omega C_2}}{R_a + R_1 + \frac{1}{j\omega C_2}}} \cdot \frac{\frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_2}} \frac{\alpha}{1 + \alpha}$$

$$= \frac{j\omega R_2 C_1}{1 + j\omega R_2 C_1} \frac{\alpha (R_1 + \frac{1}{j\omega C_2})}{R_a + (1 + \alpha)(R_1 + \frac{1}{j\omega C_2})} \frac{1}{1 + j\omega R_1 C_2} \frac{\alpha}{1 + \alpha}$$

$$= \frac{j\omega R_2 C_1}{1 + j\omega R_2 C_1} \frac{\alpha (R_1 + \frac{1}{j\omega C_2}) j\omega C_2}{(1 + \alpha) [(R_1 + \frac{R_a}{1 + \alpha}) j\omega C_2 + 1]} \frac{1}{1 + j\omega R_1 C_2} \frac{\alpha}{1 + \alpha}$$

$$= \frac{\alpha^2}{(1 + \alpha)^2} \frac{j\omega R_2 C_1}{1 + j\omega R_2 C_1} \frac{1 + j\omega R_1 C_2}{j\omega (R_1 + \frac{R_a}{1 + \alpha}) C_2 + 1} \frac{1}{1 + j\omega R_1 C_2}$$

$$= \frac{\alpha^2}{(1 + \alpha)^2} \frac{j\omega R_2 C_1}{(1 + j\omega R_2 C_1) [j\omega (R_1 + \frac{R_a}{1 + \alpha}) C_2 + 1]}$$

d)

