
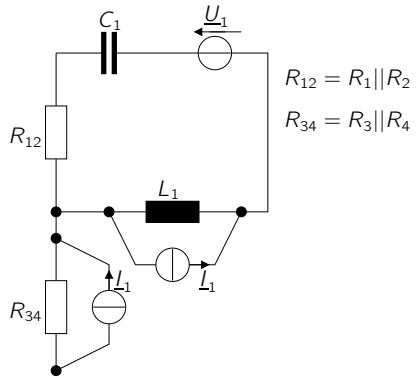


Aufgabe 1

a)

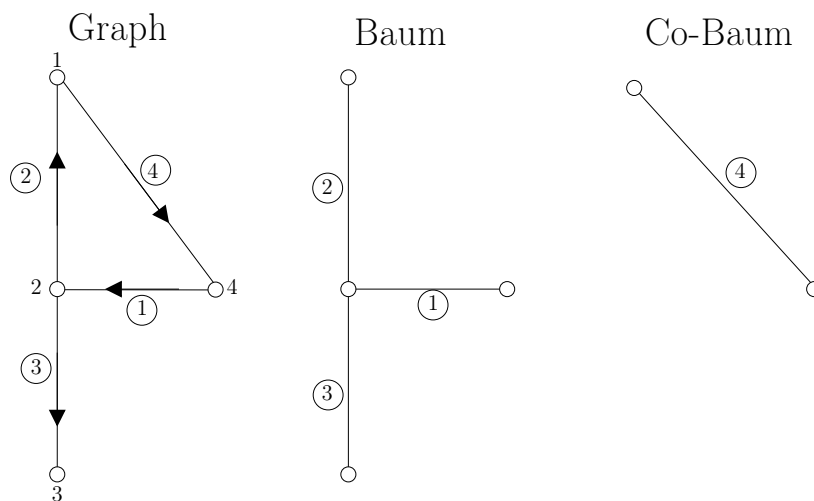

b)



c)

$$Y = \begin{pmatrix} \frac{1}{sL_1} & 0 & 0 & 0 \\ 0 & \frac{1}{R_{12}} & 0 & 0 \\ 0 & 0 & \frac{1}{R_{34}} & 0 \\ 0 & 0 & 0 & sC \end{pmatrix}$$

d)

$$A = \underset{\substack{1 \\ 2 \\ 3 \\ 4}}{K} \underset{\substack{1 \\ 2 \\ 3 \\ 4}}{Z} \begin{pmatrix} 1 & 2 & 3 & 4 \\ 0 & -1 & 0 & 1 \\ -1 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix}$$

Knoten 2 als Bezugsknoten \rightarrow Streichen 2. Zeile:

$$\Rightarrow A = \begin{pmatrix} 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix}$$

d)

$$\begin{aligned} Y_n = AY A^T &= \begin{pmatrix} 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix} \begin{pmatrix} \frac{1}{sL_1} & 0 & 0 & 0 \\ 0 & \frac{1}{R_{12}} & 0 & 0 \\ 0 & 0 & \frac{1}{R_{34}} & 0 \\ 0 & 0 & 0 & sC \end{pmatrix} \begin{pmatrix} 0 & 0 & 1 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 1 & 0 & -1 \end{pmatrix} \\ &= \begin{pmatrix} 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix} \begin{pmatrix} 0 & 0 & \frac{1}{sL_1} \\ -\frac{1}{R_{12}} & 0 & 0 \\ 0 & \frac{1}{R_{34}} & 0 \\ sC & 0 & -sC \end{pmatrix} = \begin{pmatrix} \frac{1}{R_{12}} + sC & 0 & -sC \\ 0 & \frac{1}{R_{34}} & 0 \\ -sC & 0 & \frac{1}{sL_1} + sC \end{pmatrix} \end{aligned}$$

$$\begin{aligned} I_{qn} = A(I_g - Y U_g) &= \begin{pmatrix} 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix} \left[\begin{pmatrix} I_1 \\ 0 \\ I_1 \\ 0 \end{pmatrix} - \begin{pmatrix} \frac{1}{sL_1} & 0 & 0 & 0 \\ 0 & \frac{1}{R_{12}} & 0 & 0 \\ 0 & 0 & \frac{1}{R_{34}} & 0 \\ 0 & 0 & 0 & sC \end{pmatrix} \begin{pmatrix} 0 \\ 0 \\ 0 \\ U_1 \end{pmatrix} \right] \\ &= \begin{pmatrix} 0 & -1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix} \begin{pmatrix} I_1 \\ 0 \\ I_1 \\ -sC \cdot U_1 \end{pmatrix} = \begin{pmatrix} -sC \cdot U_1 \\ I_1 \\ I_1 + sC \cdot U_1 \end{pmatrix} \end{aligned}$$

$$\begin{matrix} Y_n & U_n & = & I_{qn} \\ \begin{pmatrix} \frac{1}{R_{12}} + sC & 0 & -sC \\ 0 & \frac{1}{R_{34}} & 0 \\ -sC & 0 & \frac{1}{sL_1} + sC \end{pmatrix} & \begin{pmatrix} U_{n1} \\ U_{n3} \\ U_{n4} \end{pmatrix} & = & \begin{pmatrix} -sC \cdot U_1 \\ I_1 \\ I_1 + sC \cdot U_1 \end{pmatrix} \end{matrix}$$

 U_{n3} ist entkoppelt \Rightarrow streichen 2. Zeile und 2. Spalte:

$$\begin{pmatrix} \frac{1}{R_{12}} + sC & -sC \\ -sC & \frac{1}{sL_1} + sC \end{pmatrix} \begin{pmatrix} U_{n1} \\ U_{n4} \end{pmatrix} = \begin{pmatrix} -sC \cdot U_1 \\ I_1 + sC \cdot U_1 \end{pmatrix}$$

$$U_x = -U_{n1}$$

$$U_{n1} = \frac{\begin{vmatrix} -sC \cdot U & -sC \\ I_1 + sC \cdot U & \frac{1}{sL_1} + sC \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_{12}} + sC & -sC \\ -sC & \frac{1}{sL_1} + sC \end{vmatrix}}$$


Aufgabe 2

a)

$$\underline{Y}_1 = \frac{1}{R_1 + j\omega L_1}$$

$$\underline{Y}_2 = \frac{1}{R_2 + j\omega L_2 + \frac{1}{j\omega C_2}} = \frac{1}{R_2 + j\left(\omega L_2 - \frac{1}{\omega C_2}\right)}$$

b)

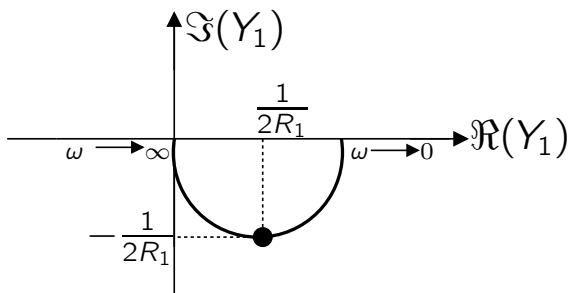


$$\max\{\Im\{\underline{Y}_1\}\} : \rightarrow \Re\{\underline{Y}_1\} = \frac{1}{2R_1}$$

$$\Im\{\underline{Y}_1\} = \frac{-\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

$$\Re\{\underline{Y}_1\} = \frac{R_1}{R_1^2 + \omega^2 L_1^2} \stackrel{!}{=} \frac{1}{2R_1}$$


$$\Leftrightarrow \omega^2 L_1^2 = R_1^2 \Leftrightarrow \omega = \frac{R_1}{L_1}$$
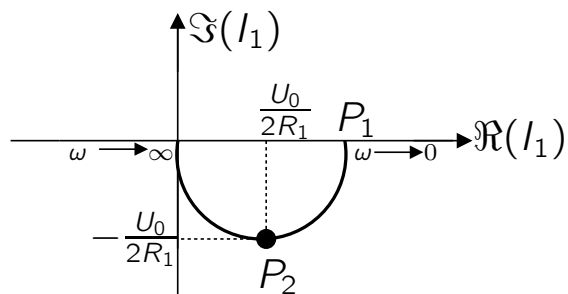
$$\Im\left\{\underline{Y}_1\left\{\frac{R_1}{L_1}\right\}\right\} = \frac{-R_1}{R_1^2 + R_1^2} = -\frac{1}{2R_1}$$



$$P_1 : I_1 = \frac{U_0}{R_1}$$
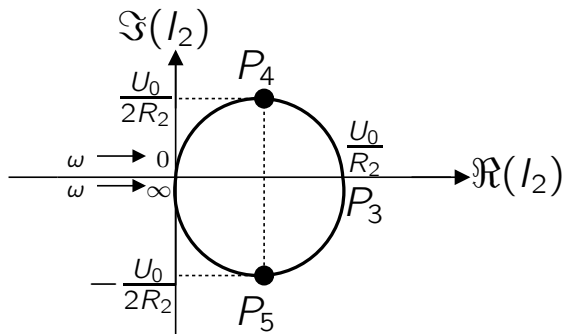
$$P_2 : I_1 = \frac{U_0}{2R_1} - j \frac{U_0}{2R_1}$$



$$P_3 : I_2 = \frac{U_0}{R_2}$$


$$P_4 : I_2 = \frac{U_0}{2R_2} + j \frac{U_0}{2R_2}$$

$$P_5 : I_2 = \frac{U_0}{2R_2} - j \frac{U_0}{2R_2}$$

c)

$$\frac{U_0}{R_1} \stackrel{!}{=} \frac{U_0}{R_2} \Leftrightarrow R_1 = R_2$$

d)

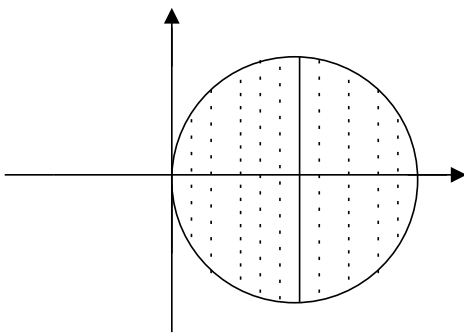

$$I_{\Delta} = I_1 - I_2$$

⇒ Verbindung muss senkrecht verlaufen, damit :

$$\Re\{I_1 - I_2\} = 0 \Leftrightarrow \Re\{T_1\{\omega_x\}\} = \Re\{I_2\{\omega_x\}\}$$

⇒ $|\Im(I_{\Delta}(\omega_x))|$ möglichst groß ⇒ in der Mitte

$$\Rightarrow I_1\{\omega_x\} = \frac{U_0}{2R_1} - j \frac{U_0}{2R_2} ; I_2\{\omega_x\} = \frac{U_0}{2R_1} + j \frac{U_0}{2R_2}$$

$$\Rightarrow I_{\Delta}\{\omega_x\} = -j \frac{U_0}{R_2}$$

$$\Rightarrow I_1 = Y_1 \cdot U_0 = \frac{1}{R_0 + j\omega L_1} U_0 = \frac{R_0 - j\omega L_1}{R_0^2 + \omega^2 L_1^2} U_0$$

$$\Re I_1(\omega_x) = -\Im I_1(\omega_x) \Leftrightarrow R_0 = j\omega L_1 \Leftrightarrow \omega_x = \frac{R_0}{L_1}$$

$$I_2 = Y_2 \cdot U_0 = \frac{1}{R_2 + j\omega - xL_2 + \frac{1}{j\omega C_2}} \cdot U_0 = \frac{j\omega_x C_2}{1 - \omega_x^2 C_2 L_2 + j\omega R_0 C_2} \cdot U_0$$

$$= \frac{j\omega_x C_2 (1 - \omega_x^2 C_2 L_2 + j\omega R_0 C_2)}{(1 - \omega_x^2 C_2 L_2)^2 + (\omega R_0 C_2)^2} U_0$$


$$\Re I_2(\omega_x) = \Im I_2(\omega_x) \Leftrightarrow \omega_x^2 R_0 C_2^2 = \omega_x C_2 (1 - \omega_x^2 C_2 L_2) \rightsquigarrow 1 - \omega_x^2 C_2 L_2 - \omega_x^2 R_0 C_2 = 0$$

$$\rightsquigarrow 1 - \frac{R_0^2}{L_1^2} C_2 L_2 - \frac{R_0^2 C_2}{L_1} = 0$$

$$\Rightarrow L_2 = \frac{1 - \frac{R_0^2 C_2}{L_1}}{\frac{R_0^2 C_2}{L_1^2}} = \frac{L_1^2}{R_0^2 C_2} - L_1 = L_1 \left(\frac{L_1}{R_0^2 C_2} - 1 \right)$$

Aufgabe 3

a)

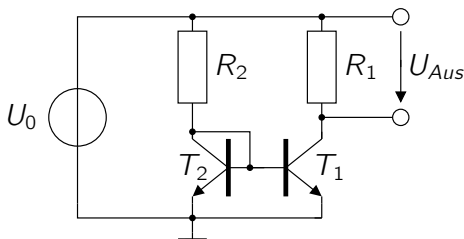

b)

Normalaktiver Bereich für T1 : $U_{CE,1} \geq U_{BE}$

$$U_{aus,min} = 0 ; U_{aus,max} = U_0 - U_{BE,0}$$


$$U_{aus,0} = \frac{1}{2} (U_{aus,max} + U_{aus,min}) = \frac{U_0 - U_{BE,0}}{2}$$

$$I_{C1,0} = \frac{U_{aus,0}}{R_1} = \frac{U_0 - U_{BE,0}}{2R_1}$$


c)

$$I_{C2,0} = I_{C1,0} ; R_2 I_{C2,0} + U_{BE,2} = U_0 \Rightarrow R_2 = \frac{U_0 - U_{BE,0}}{I_{C2,0}} = 2R_1$$

d)

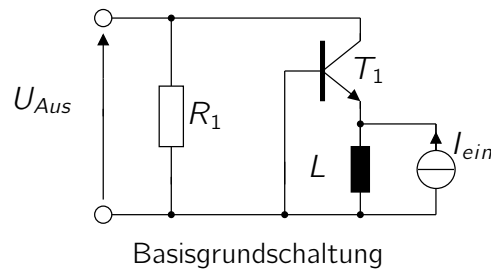

e)

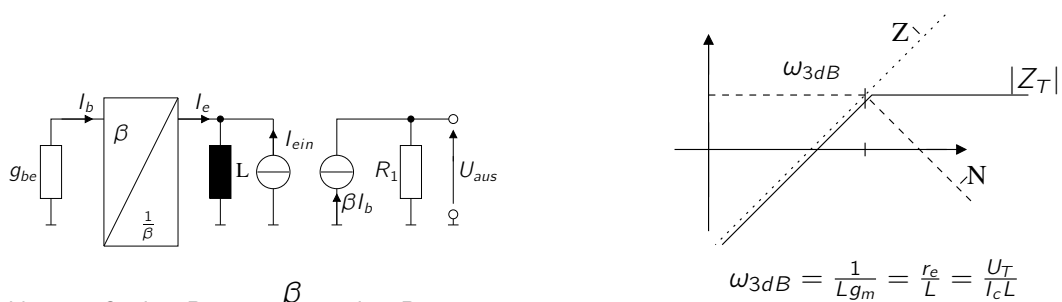

$$\begin{aligned}
 U_{aus} &= \beta \cdot I_b \cdot R_1 = \frac{\beta}{\beta + 1} \cdot I_e \cdot R_1 \\
 &= \frac{\beta}{\beta + 1} \cdot (-I_{ein}) \cdot \frac{j\omega L}{\frac{1}{\beta} \frac{1}{g_{be}} + j\omega L} \cdot R_1 \\
 &= -\frac{\beta}{\beta + 1} \cdot R_1 \cdot \frac{j\omega L g_m}{1 + j\omega L g_m} \cdot I_{ein} \\
 \Rightarrow |Z_T| &= \frac{\beta}{\beta + 1} \cdot R_1 \cdot \left| \frac{j\omega L g_m}{1 + j\omega L g_m} \right|
 \end{aligned}$$


$$\omega_{3dB} = \frac{1}{Lg_m} = \frac{r_e}{L} = \frac{U_T}{I_c L}$$

$$Z = j\omega L g_m \quad (\text{Zähler})$$

$$N = 1 + j\omega L g_m \quad (\text{Nenner})$$

Aufgabe 4

a)

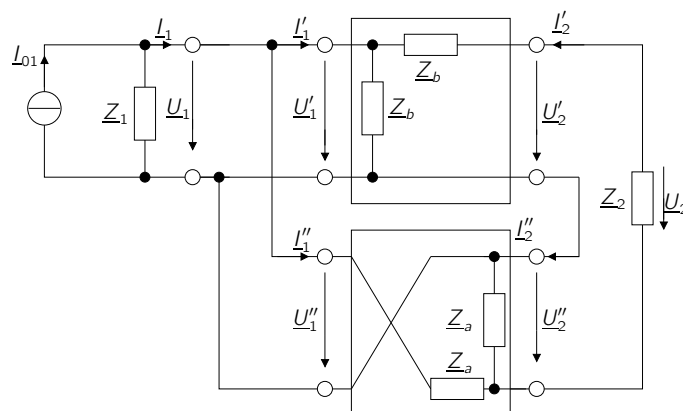

b)

i) PSK

ii) \underline{G} -Parameter, weil:

$$\underline{U}'_1 = \underline{U}''_1 = \underline{U}_1; \quad \underline{I}_2 = \underline{I}'_2 + \underline{I}''_2;$$

$$\underline{I}_1 = \underline{G}'_{11}\underline{U}'_1 + \underline{G}'_{12}\underline{I}'_2 + \underline{G}''_{11}\underline{U}''_1 + \underline{G}''_{12}\underline{I}''_2 = (\underline{G}'_{11} + \underline{G}''_{11})\underline{U}_1 + (\underline{G}'_{12} + \underline{G}''_{12})\underline{I}_2$$

$$\underline{U}_2 = \underline{G}'_{21}\underline{U}'_1 + \underline{G}'_{22}\underline{I}'_2 + \underline{G}''_{21}\underline{U}''_1 + \underline{G}''_{22}\underline{I}''_2 = (\underline{G}'_{21} + \underline{G}''_{21})\underline{U}_1 + (\underline{G}'_{22} + \underline{G}''_{22})\underline{I}_2$$

$$\Rightarrow \underline{G} = \underline{G}' + \underline{G}''$$

c)

$$\underline{G}'_{11} = \left. \frac{I'_1}{U'_1} \right|_{I'_2=0} = \frac{1}{Z_b} \quad \underline{G}'_{12} = \left. \frac{I'_1}{I'_2} \right|_{U'_1=0} = -1$$

$$\underline{G}'_{21} = \left. \frac{U'_2}{U'_1} \right|_{I'_2=0} = 1 \quad \underline{G}'_{22} = \left. \frac{U'_2}{I'_2} \right|_{U'_1=0} = Z_b$$

$$\Rightarrow \underline{G}' = \begin{pmatrix} \frac{1}{Z_b} & -1 \\ 1 & Z_b \end{pmatrix}$$

$$\underline{G}''_{11} = \left. \frac{I''_1}{U''_1} \right|_{I''_2=0} = \frac{1}{2Z_a} \quad \underline{G}''_{12} = \left. \frac{I''_1}{I''_2} \right|_{U''_1=0} = \frac{1}{2}$$

$$\underline{G}''_{21} = \left. \frac{U''_2}{U''_1} \right|_{I''_2=0} = -\frac{1}{2} \quad \underline{G}''_{22} = \left. \frac{U''_2}{I''_2} \right|_{U''_1=0} = \frac{Z_a}{2}$$

$$\Rightarrow \underline{G}'' = \begin{pmatrix} \frac{1}{2Z_a} & \frac{1}{2} \\ -\frac{1}{2} & \frac{Z_a}{2} \end{pmatrix}$$


$$\Rightarrow \underline{G} = \underline{G}' + \underline{G}'' = \begin{pmatrix} \frac{1}{Z_b} + \frac{1}{2Z_a} & -\frac{1}{2} \\ \frac{1}{2} & Z_b + \frac{Z_a}{2} \end{pmatrix}$$

d)

$$\begin{aligned} U_2 &= -Z_2 I_2 \Leftrightarrow I_2 = -\frac{U_2}{Z_2} \\ U_2 &= G_{21} U_1 + G_{22} I_2 = U_1 G_{21} - \frac{G_{22}}{Z_2} U_2 \\ \Leftrightarrow U_2 \left(1 + \frac{G_{22}}{Z_2} \right) &= G_{21} U_1 \\ \Rightarrow \underline{F}_U = \frac{U_2}{U_1} &= \frac{G_{21}}{1 + \frac{G_{22}}{Z_2}} = \frac{\frac{1}{2}}{1 + \frac{Z_b + \frac{Z_a}{2}}{Z_2}} = \frac{Z_2}{2Z_2 + 2Z_b + Z_a} \end{aligned}$$

$$\underline{F}_U = 0 \text{ für } |Z_a|, |Z_b| \rightarrow \infty$$

Aufgabe 5

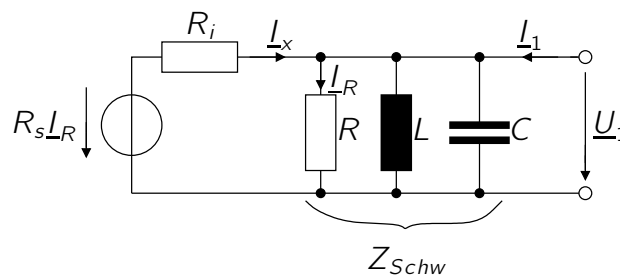

a)

$$\begin{aligned} \underline{Z}(s) &= \frac{U_1}{I_1} \\ U_1 &= (I_1 + I_x) \cdot Z_{Schw} \quad I_R = \frac{U_1}{R} \quad I_x = \frac{R_s I_R - U_1}{R_i} = \frac{R_s \frac{U_1}{R} - U_1}{R_i} = \frac{U_1}{R_i} \left(\frac{R_s}{R} - 1 \right) \\ U_1 &= \left(I_1 + \frac{U_1}{R_i} \left(\frac{R_s}{R} - 1 \right) \right) Z_{Schw} \Leftrightarrow U_1 \cdot \left(1 - \frac{\left(\frac{R_s}{R} - 1 \right) Z_{Schw}}{R_i} \right) = I_1 \cdot Z_{Schw} \\ \underline{Z}(s) &= \frac{U_1}{I_1} = \frac{I_1 \cdot Z_{Schw}}{1 - \frac{\left(\frac{R_s}{R} - 1 \right) Z_{Schw}}{R_i}} = \frac{\frac{1}{\frac{1}{R} + \frac{1}{sL} + sC}}{1 - \left(\frac{R_s}{R} - 1 \right) \cdot \frac{1}{R_i} \cdot \frac{1}{\left(\frac{1}{R} + \frac{1}{sL} + sC \right)}} \\ &= \frac{1}{\frac{1}{R} + \frac{1}{sL} + sC - \left(\frac{R_s}{R} - 1 \right) \cdot \frac{1}{R_i}} = \frac{1}{sL \cdot R_i + R_i R + s^2 \cdot CL \cdot R_i R - (R_s - R) sL} \end{aligned}$$

b)

Spannung soll oszillieren \Rightarrow schlieÙe hochomige Last an Oszillator an
 $\Rightarrow \underline{I} \mapsto 0 \quad \underline{U} = \underline{I} \cdot \underline{Z} \neq 0$ für Pole von \underline{Z}

c)

$$s^2 \cdot R_i R \cdot CL + sL \cdot (R_i - R_s + R) + R_i R \stackrel{!}{=} 0 \Leftrightarrow s^2 + s \cdot \frac{R_i - R_s + R}{R_i R \cdot C} + \frac{1}{CL} = 0$$

$$s_{1,2} = -\frac{R_i - R_s + R}{2R_i RC} \pm \sqrt{\left(\frac{R_i - R_s + R}{2R_i RC}\right)^2 - \frac{1}{LC}}$$

Schwingkreis entdämpft für $\sigma > 0$

$$\sigma = -\frac{R_i - R_s + R}{2R_i RC}, \quad R > 0, R_i > 0, C > 0 \Rightarrow \sigma > 0 \quad \text{für } R_s > R_i + R$$

d)

$$\begin{aligned} j\omega &= \sqrt{\underbrace{\left(\frac{R_i - R_s + R}{2R_i RC}\right)^2 - \frac{1}{LC}}_{<0}} = \sqrt{\left(\frac{R - 4R + R}{2R^2 C}\right)^2 - \frac{1}{LC}} = \sqrt{\left(\frac{-2R}{2R^2 C}\right)^2 - \frac{1}{LC}} \\ &= \sqrt{\left(\frac{R - 4R + R}{2R^2 C}\right)^2 - \frac{1}{LC}} = \sqrt{\underbrace{\frac{1}{R^2 C^2} - \frac{1}{LC}}_{<0}} \Rightarrow \omega = \sqrt{\frac{1}{LC} - \frac{1}{R^2 C^2}} \\ &\Rightarrow \frac{1}{LC} > \frac{1}{R^2 C^2} \rightarrow L < R^2 C \rightarrow \frac{L}{C} < R^2 \end{aligned}$$

e)

$$\delta(t) \circ \bullet 1$$


$$\begin{aligned} \Rightarrow \underline{U}_1(s) &= 1 \cdot \underline{Z}(s) = 1 \cdot \frac{sL \cdot R^2}{sL \cdot R + R^2 + s^2 \cdot CL \cdot R^2 - (4R - R)sL} \\ &= 1 \cdot \frac{sL \cdot R^2}{CL \cdot R^2 \cdot (s^2 - 2\frac{s}{CR} + \frac{1}{CL})} = \frac{1}{C} \cdot \frac{s}{(s - s_1)(s - s_2)} \end{aligned}$$

$$\text{Heavisidscher Entwicklungssatz: } u_1(t) = \sum_{s_1, s_2} \frac{\underline{Z}(s)}{N'(s)} \cdot e^{st} \Big|_{s=s_j} = \frac{1}{C} \left(\frac{s_1}{s_1 - s_2} \cdot e^{s_1 t} - \frac{s_2}{s_2 - s_1} \cdot e^{s_2 t} \right)$$

mit s_1, s_2 aus Aufgabenteil c)

Aufgabe 6

a)



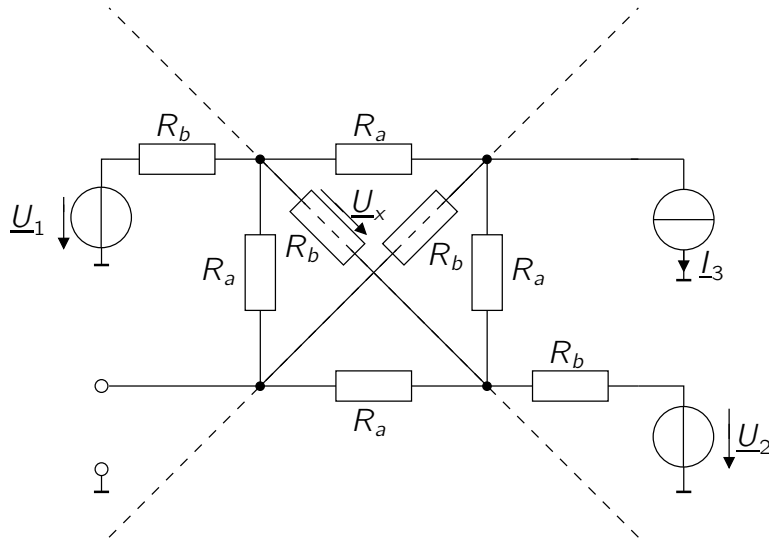


1)

$$U_1 = U_2 = 0$$

$$I_4 = I^+ + I^- = 0 \quad , \quad I_3 = I^+ - I^-$$
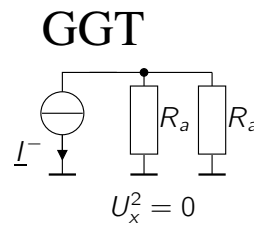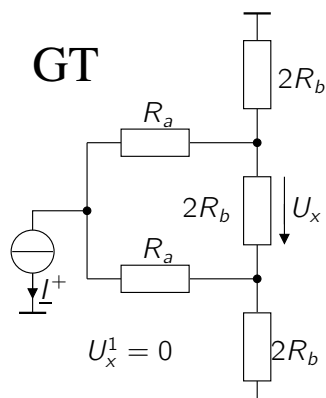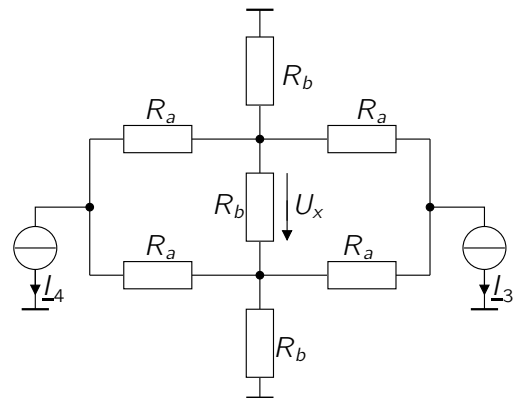
$$I^+ = \frac{I_3 + I_4}{2} = \frac{I_3}{2} \quad , \quad I^- = \frac{I_4 - I_3}{2} = -\frac{I_3}{2}$$






2)

$$I_3 = 0$$

$$\underline{U}_1 = \underline{U}^+ + \underline{U}^- \quad , \quad \underline{U}_2 = \underline{U}^+ - \underline{U}^-$$
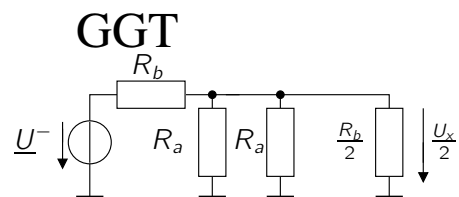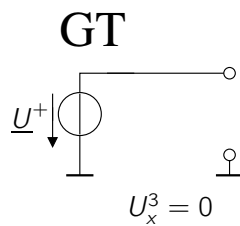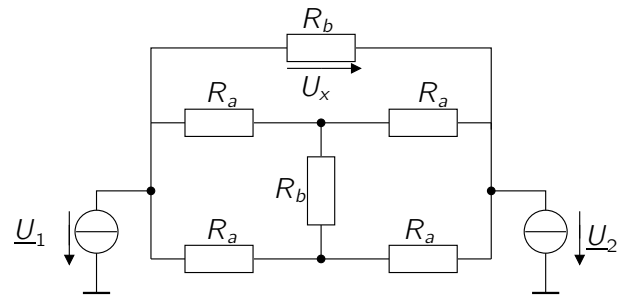
$$\underline{U}^+ = \frac{\underline{U}_2 + \underline{U}_1}{2} \quad , \quad \underline{U}^- = \frac{\underline{U}_1 - \underline{U}_2}{2}$$



b)

$$\frac{U_x}{2} = \underline{U}^- \cdot \frac{R_a \parallel R_a \parallel \frac{R_b}{2}}{R_b + (R_a \parallel R_a \parallel \frac{R_b}{2})} \stackrel{(*)}{=} \frac{\frac{1}{2} R_a R_b}{R_b(R_a + R_b) + \frac{1}{2} R_a R_b} \underline{U}^-$$

$$\Rightarrow \underline{U}_x = \frac{R_a}{\frac{3}{2} R_a + R_b} \cdot (\underline{U}_1 - \underline{U}_2)$$

$$(*) \quad R_a \parallel R_a \parallel \frac{R_b}{2} = \frac{\frac{R_a R_a}{2} \cdot \frac{R_b}{2}}{\frac{R_a}{2} + \frac{R_a}{2} + \frac{R_b}{2}} = \frac{1}{2} \frac{R_a R_b}{R_a + R_b}$$

Aufgabe 7

a)


$$F = \frac{U_2}{U_1} \quad \underline{U}_2 = v_u \underline{U}_d$$

$$\underline{U}_d = k_F \underline{U}_1 - k_R \underline{U}_2 \quad \frac{\underline{U}_2}{U_1} = \frac{v_u k_F}{1 + v_u k_R}$$

$$k_F = \left. \frac{\underline{U}_d}{U_1} \right|_{U_2=0} = \frac{z_2}{z_1 + z_2} \quad k_R = - \left. \frac{\underline{U}_d}{U_2} \right|_{U_1=0} = - \frac{z_1}{z_1 + z_2}$$

$$\Rightarrow \frac{U_2}{U_1} = \frac{v_u \frac{z_2}{z_1 + z_2}}{1 - v_u \frac{z_1}{z_1 + z_2}}$$

b)

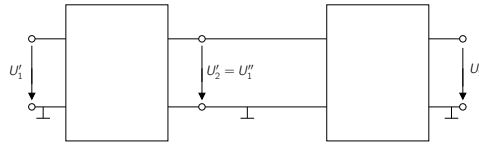

$$\begin{aligned}
 \frac{U_2''}{U_1'} &= \frac{U_2'}{U_1'} \cdot \frac{U_2''}{U_2'} = \frac{\alpha \frac{z_2'}{z_1' + z_2'}}{1 - \alpha \frac{z_1'}{z_1' + z_2'}} \cdot \frac{\alpha \frac{z_2''}{z_1'' + z_2''}}{1 - \alpha \frac{z_1''}{z_1'' + z_2''}} = \frac{\alpha \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}}}{1 - \alpha \frac{\frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}}} \cdot \frac{\alpha \frac{R_2 + \frac{1}{j\omega C_2}}{R_2 + R_2 + \frac{1}{j\omega C_2}}}{1 - \alpha \frac{R_2}{R_2 + R_2 + \frac{1}{j\omega C_2}}} \\
 &= \frac{\alpha R_1}{(1 - \alpha) \frac{1}{j\omega C_1} + R_1} \cdot \frac{\alpha (R_2 + \frac{1}{j\omega C_2})}{(1 - \alpha) R_2 + R_2 + \frac{1}{j\omega C_2}} = \frac{j\omega R_1 C_1}{(\frac{1}{\alpha} - 1) + \frac{j\omega R_1 C_1}{\alpha}} \cdot \frac{1 + j\omega R_2 C_2}{(\frac{1}{\alpha} - 1) j\omega R_2 C_2 + \frac{1 + j\omega R_2 C_2}{\alpha}} \\
 \stackrel{\alpha \rightarrow \infty}{=} & -j\omega R_1 C_1 \cdot \frac{1 + j\omega R_2 C_2}{-j\omega R_2 C_2} \Rightarrow \underline{E}_k = j \frac{\omega}{\omega_1} \cdot \frac{1 + j \frac{\omega}{\omega_2}}{j \frac{\omega}{\omega_2}}
 \end{aligned}$$

c)

$$\omega_1 = \omega_2 = \omega_0 \quad \Rightarrow \quad R_1 C_1 = R_2 C_2 \quad \Rightarrow \quad \underline{E}_k = 1 + j \frac{\omega}{\omega_0}$$

d)

