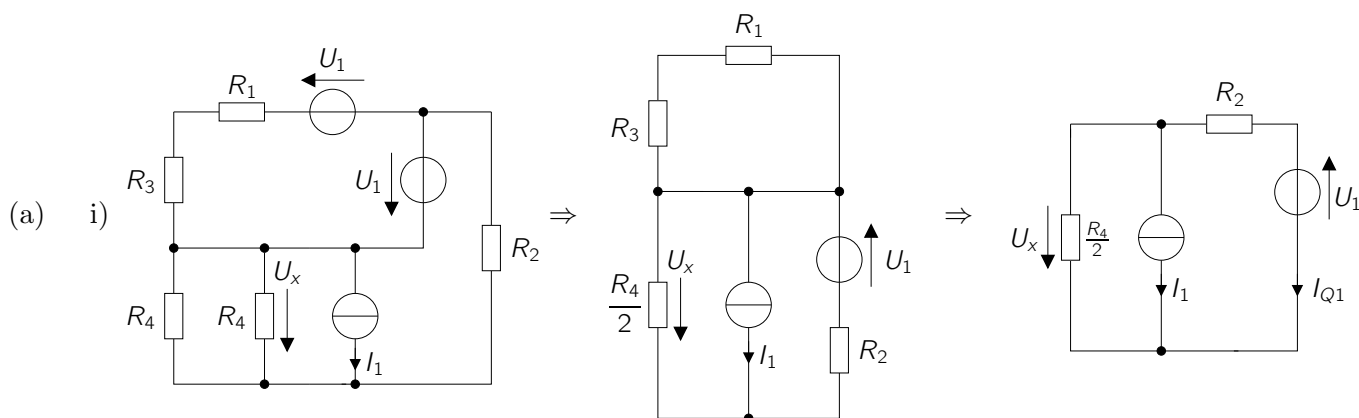


Aufgabe 1



Superposition

$$U_1 = 0 \Rightarrow U'_x = -I_1 \left(\frac{R_4}{2} \parallel R_2 \right) = -I_1 \left(\frac{\frac{R_4}{2} R_2}{\frac{R_4}{2} + R_2} \right)$$

$$I_1 = 0 \Rightarrow U''_x = -U_1 \frac{\frac{R_4}{2}}{\frac{R_4}{2} + R_2}$$

$$\text{Gesamt: } U_x = U'_x + U''_x = -I_1 \left(\frac{\frac{R_4}{2} R_2}{\frac{R_4}{2} + R_2} \right) - U_1 \frac{\frac{R_4}{2}}{\frac{R_4}{2} + R_2}$$

ii) Gesamtlösung: Summe der Leistungen an den Quellen:


$$\begin{aligned} P_\Sigma &= P_{\text{Stromquelle}} + P_{\text{Spannungsquelle}} \\ &= -I_1 U_x + U_1 I_{Q1} = I_1 U_x + U_1 \left(\frac{U_x}{\frac{R_4}{2}} + I_1 \right) \end{aligned}$$


(b)

$$\begin{aligned} \underline{U}_1 &= j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2 & | + j\omega M \underline{I}_1 - j\omega M \underline{I}_1 \\ \underline{U}_2 &= j\omega M \underline{I}_1 + j\omega L_2 \underline{I}_2 & | + j\omega M \underline{I}_2 - j\omega M \underline{I}_2 \end{aligned}$$

$$\Leftrightarrow \underline{U}_1 = j\omega(L_1 - M)\underline{I}_1 + j\omega M(\underline{I}_2 + \underline{I}_1)$$

$$\Leftrightarrow \underline{U}_2 = j\omega M(\underline{I}_1 + \underline{I}_2) + j\omega(L_2 - M)\underline{I}_2$$

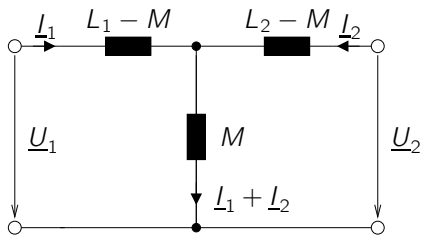

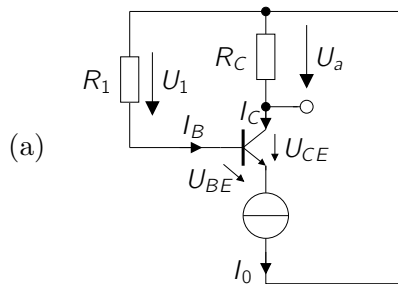Aufgabe 2

(b)

$$U_{CE} = 10U_{BE}$$

$$U_a = 5U_{BE}$$

$$I_E = I_0 = I_C + I_B = I_B B + I_B = I_B (B + 1) \quad I_B > 0 \quad \text{für normal aktiv}$$



$$\Leftrightarrow I_0 = I_C \left(1 + \frac{1}{B} \right) \Rightarrow I_C = \frac{I_0 B}{B + 1}$$

$$U_a = I_C R_C \Leftrightarrow R_C = \frac{U_a}{I_C} = \frac{5U_{BE}(B + 1)}{I_0 B}$$

$$U_1 = R_1 I_B = R_1 \frac{I_0}{B + 1}$$

$$U_{BE} + U_1 = U_a + U_{CE} \Leftrightarrow U_1 = U_a + U_{CE} - U_{BE} = 14U_{BE}$$
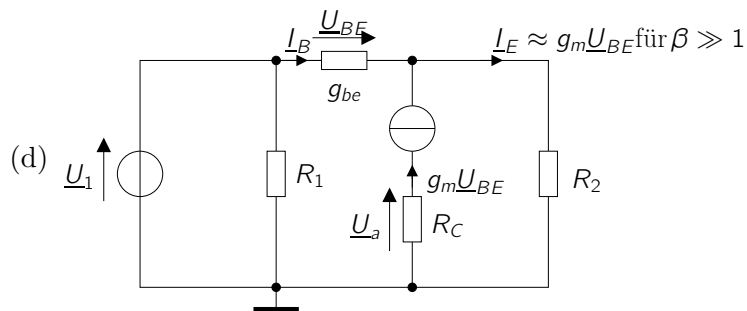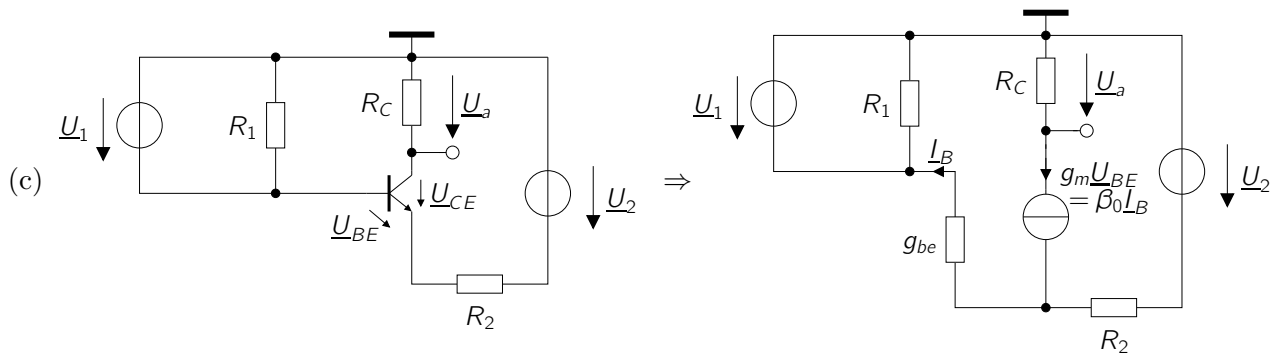
$$\Rightarrow R_1 = \frac{B + 1}{I_0} U_1 = \frac{B + 1}{I_0} 14U_{BE}$$



Für $U_2 = 0$ gilt:

$$U_a = g_m U_{BE} R_C = \beta_0 I_B R_C$$


$$I_C \approx I_E \quad \text{für } \beta \gg 1$$

$$U_1 = -I_B \frac{1}{g_{be}} - \beta_0 I_B R_2$$

$$\Leftrightarrow I_B = -\frac{U_1}{\frac{1}{g_{be}} + \beta_0 R_2}$$

$$\Rightarrow U_a = -\beta_0 \frac{R_C U_1}{\frac{1}{g_{be}} + \beta_0 R_2}$$

$$\left. \frac{U_a}{U_1} \right|_{U_2=0} = -\frac{\beta_0 R_C}{\frac{1}{g_{be}} + \beta_0 R_2} = -\frac{R_C}{\frac{1}{g_m} + R_2}$$

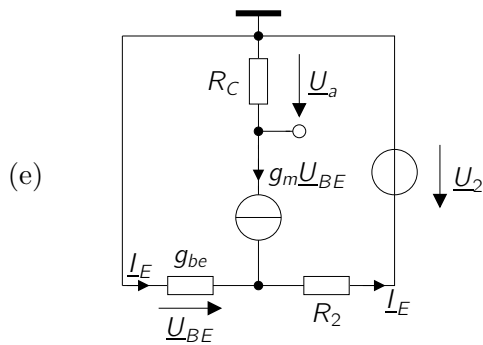

Für $U_1 = 0$ gilt:

$$\underline{U}_a = \beta_0 \underline{I}_B R_C = g_m \underline{U}_{BE} R_C$$

$$\underline{U}_2 = \underline{I}_B \frac{1}{g_{be}} + \beta_0 \underline{I}_B R_2 \quad |\beta \gg 1 \Rightarrow \underline{I}_E \approx \underline{I}_C$$

$$\underline{I}_B = \frac{\underline{U}_2}{\frac{1}{g_{be}} + \beta_0 R_2}$$

$$\left. \frac{\underline{U}_a}{\underline{U}_2} \right|_{\underline{U}_1=0} = \beta_0 R_C \frac{\underline{U}_2}{\frac{1}{g_{be}} + \beta_0 R_2} = \frac{\beta_0 R_C}{\frac{1}{g_{be}} + \beta_0 R_2} = \frac{R_C}{\frac{1}{g_m} + R_2}$$

$$\underline{U}_{a,ges} = \left. \frac{\underline{U}_a}{\underline{U}_1} \right|_{\underline{U}_2=0} + \left. \frac{\underline{U}_a}{\underline{U}_2} \right|_{\underline{U}_1=0} = -\frac{R_C}{\frac{1}{g_m} + R_2} \underline{U}_1 + \frac{R_C}{\frac{1}{g_m} + R_2} \underline{U}_2 = \frac{R_C}{\frac{1}{g_m} + R_2} (\underline{U}_2 - \underline{U}_1)$$

Aufgabe 3

(a) i)

Fall 1:

$$I_C = 0$$

$$\Rightarrow U_{CE} = U_0 = 1,2 \text{ V}$$

Fall 2:

$$U_{CE} = 0$$

$$\frac{U_0}{R_C} = I_C = \frac{1,2 \text{ V}}{40 \Omega} = 30 \text{ mA}$$

ii)

$$I_B \geq 100 \mu\text{A}$$

bzw.

$$I_B \leq 25 \mu\text{A}$$

um Bedingung zu erfüllen

(b) Graphische Bestimmung des Arbeitspunktes: $U_D \approx 0,82 \text{ V}$ und $I_D \approx 2,9 \text{ mA}$ Fall 1: $I_D = 0$

$$\Rightarrow U_D = I_0 R_1 = 14 \text{ mA} \cdot 100 \Omega = 1,4 \text{ V}$$

Fall 2: $U_D = 0$

$$I_D = I_0 \frac{R_2}{R_1 + R_2} = 14 \text{ mA} \cdot 0,5 = 7 \text{ mA}$$

Aufgabe 4(a) $0 \leq t \leq DT$

$$u_{out}(t) = -C R \frac{du_{out}(t)}{dt}$$

$$i_C = C \frac{du_{out}(t)}{dt}$$

$$u_{out}(t) = -C R \dot{u}$$

$$i_R = \frac{u_{out}(t)}{R}$$

$$-i_C = i_R$$

 $DT \leq t < T$

$$I_0 = i_C$$

$$I_0 = C \frac{du_{out}(t)}{dt}$$

$$I_0 = C \dot{u}_{out}(t)$$

(b)

$$0 \leq t \leq DT$$

$$u_{out}(t) = -CR \frac{du_{out}(t)}{dt} \quad |\text{Ansatz} \rightarrow e^{\lambda t}$$

$$e^{\lambda t} = -CR \lambda e^{\lambda t}$$

$$1 = -CR \lambda$$

$$\lambda = -\frac{1}{RC}$$

Lösung: $0 \leq t \leq DT$

$$\begin{aligned} u_{out}(t) &= k_1 e^{-\frac{t}{RC}} & k_1 \text{ ist Anfangsbedingung} \\ &= u_{out}(0) e^{-\frac{t}{RC}} & k_1 = u_{out}(t=0) = u_{out,max} \end{aligned}$$

$$DT \leq t < T$$

$$I_0 = C \frac{du_{out}(t)}{dt} \quad \Big| \int_{DT}^T dt$$

$$\int_{DT}^T I_0 dt = C \int_{DT}^T \frac{du_{out}(t)}{dt} dt = C \int_{DT}^T du_{out}(t) \quad | I_0 \text{ ist konstant}$$

$$I_0 (T - DT) = C [u_{out}(T) - u_{out}(DT)]$$

(c)

$$0 \leq t \leq DT$$

$$u_{out}(t) = u_{out}(0) e^{-\frac{t}{RC}} \quad |e^x \approx (1+x) \parallel RC \ll \frac{1}{T}$$

$$u_{out}(t) = u_{out}(0) \left(1 - \frac{t}{RC}\right) \quad |t = DT$$

$$u_{out}(DT) = u_{out}(0) \left(1 - \frac{DT}{RC}\right)$$

$$u_{out}(DT) = u_{out}(0) - u_{out}(0) \frac{DT}{RC}$$

$$\underbrace{u_{out}(DT) - u_{out}(0)}_{\Delta u'_{out}(t)} = -u_{out}(0) \frac{DT}{RC}$$

$$DT \leq t < T$$

$$I_0(T - DT) = C \underbrace{[u_{out}(T) - u_{out}(DT)]}_{\Delta u''_{out}(t)} = C \Delta u''_{out}(t)$$

$$\Rightarrow \Delta u''_{out}(t) = -\Delta u'_{out}(t)$$

$$\frac{I_0}{C} T (1 - D) = \frac{DT}{RC} u_{out}(0)$$

$$\Leftrightarrow u_{out}(0) = \frac{RI_0}{D} (1 - D) = RI_0 \frac{(1 - D)}{D} = u_{out,max}$$

(d)

$$\begin{aligned}\overline{u_{out}} &= u_{out,max} - \frac{|\Delta u'_{out}(t)|}{2} \\ &= u_{out}(0) - u_{out}(0) \frac{DT}{2RC} = u_{out}(0) \left(1 - \frac{DT}{2RC}\right)\end{aligned}$$