

## Aufgabe 1

a)




b)

4 Co-Baum-Ströme und unabhängig davon 2 bekannte Ströme (Stromquellen)  
 $\Rightarrow$  2 unbekannte Ströme

c)

umzeichnen:

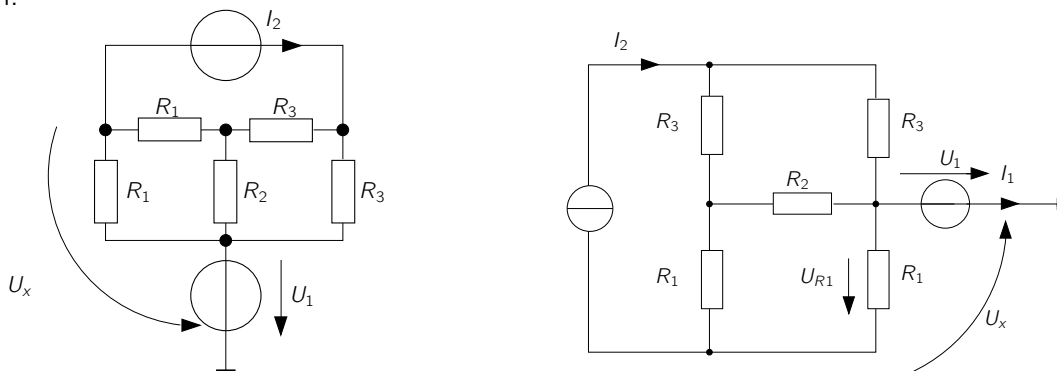

$$U_{R1} = \frac{R_1 I_2}{2} \text{ (symmetrie)}$$

$$U_x = U_1 - U_{R1} = U_1 - \frac{R_1 I_2}{2} = 2R_0 I_2 - \frac{R_1 I_2}{2} = \frac{3}{2} R_0 I_2 = \frac{3}{4} U_1$$

d)

$$I_1 = 0 \Rightarrow U_1 I_1 = 0$$

$$U_2 = \frac{I_2}{2} (R_1 + R_2) = \frac{U_1}{4R_0} = U_1$$


$$\Rightarrow P = 0 + I_2 U_1 = \frac{U_1}{2R_0} U_1 = \frac{1}{2} \frac{U_1^2}{R_0}$$

## Aufgabe 2

a)

$$\begin{aligned}
 Y_x &= \frac{1}{j\omega L_k} = -j \frac{1}{\omega L_k} \\
 Y_y &= \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2 + \frac{1}{j\omega C}}} \right)^{-1} = \left( \frac{R_1 + (R_2 + \frac{1}{j\omega C})}{R_1 + R_2 + \frac{1}{j\omega C}} \right)^{-1} \\
 &= \frac{R_1 + R_2 + \frac{1}{j\omega C}}{R_1 R_2 + \frac{R_1}{j\omega C}} = \frac{(R_1 + R_2)j\omega C + 1}{R_1 R_2 j\omega C + R_1}
 \end{aligned}$$

b)

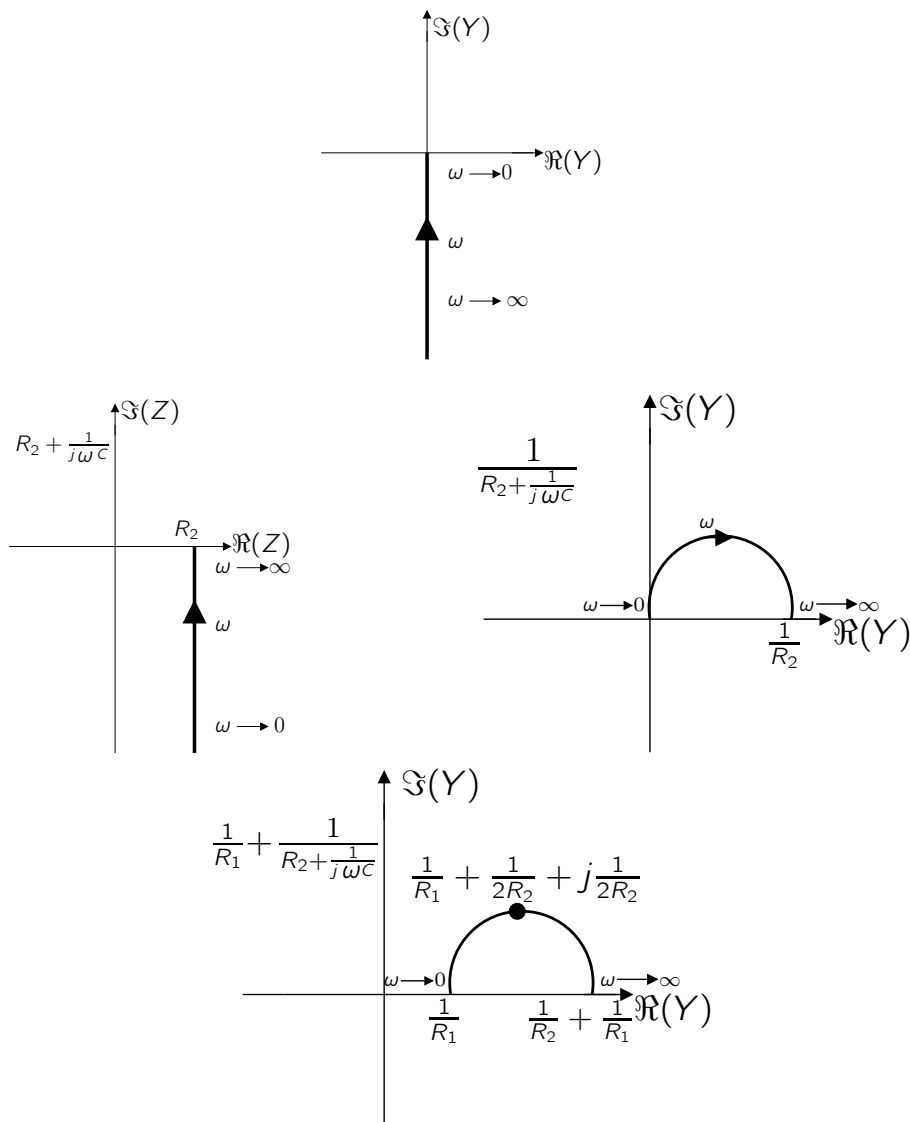


c)

$$\text{Im}(Y_x) = -\text{Im}(Y_y)$$

$$\frac{1}{\omega L_R} = \frac{1}{2R_2} \Leftrightarrow L_R = \frac{2R_2}{\omega} \Rightarrow L_k = \frac{2R_2}{\omega_x}$$

### Aufgabe 3

a)

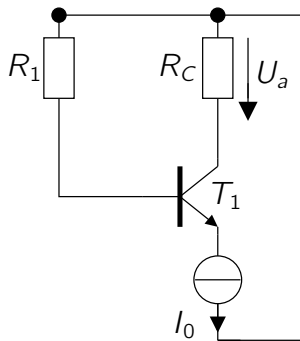


b)

Dimensioniere

$$U_{CE} = 10U_{BE}, U_a = 5U_{BE}$$



- 1.)  $I_B R_1 = U_a + U_{CB} = U_a + 9U_{BE} = 5U_{BE} + 10U_{BE} - U_{BE} = 14U_{BE}$
- 2.)  $I_C = \beta I_B = \frac{\beta}{\beta + 1} I_E = \frac{\beta}{\beta + 1} I_0$   
 $\Rightarrow R_1 = 14U_{BE} \frac{\beta + 1}{I_0}$
- 3.)  $R_a = \frac{U_a}{I_C} = 5U_{BE} \frac{\beta + 1}{\beta I_0}$

c)

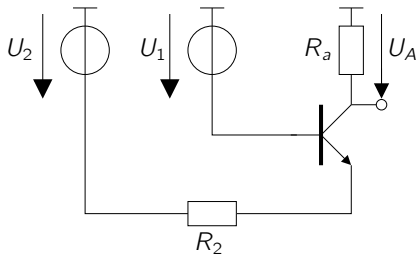

d)


$$U_1 = 0;$$

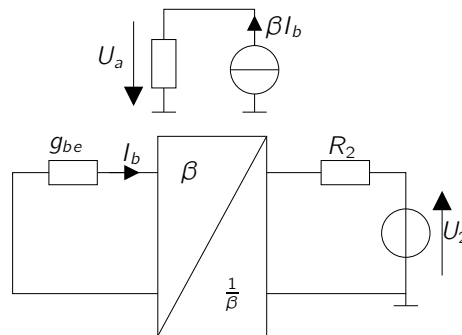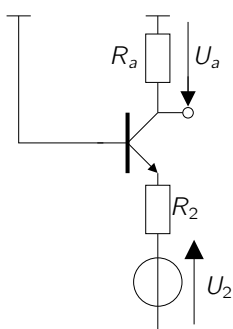

$$U_a = \beta I_b R_a = \beta \frac{U_2}{\frac{1}{g_{be}} + \beta R_2} R_a$$

$$\left. \frac{U_a}{U_2} \right|_{U_1=0} = \frac{\beta R_a}{\frac{1}{g_{be}} + \beta R_2} = \frac{R_a}{\frac{1}{\beta g_{be}} + R_2} = \frac{R_a}{\frac{1}{g_m} + R_2} = \frac{R_a}{r_e + R_2}$$

$U_2 = 0$

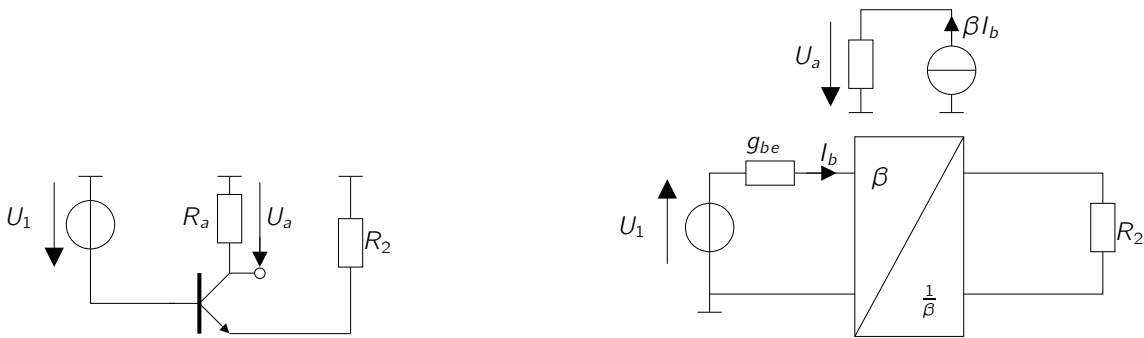

$$U_a = \beta I_b R_a = \beta \cdot \left( -\frac{U_1}{\frac{1}{g_{be}} + \beta R_2} \right) R_a$$

$$\left. \frac{U_a}{U_1} \right|_{U_2=0} = \frac{\beta R_a}{\frac{1}{g_{be}} + \beta R_2} = \frac{R_a}{r_e + R_2} \quad (\text{s.o.})$$

$$\Rightarrow U_a = \frac{\beta R_a}{\frac{1}{g_{be}} + \beta R_2} (U_2 - U_1)$$

e)

$$\frac{\beta R_a}{\frac{\beta}{g_{be}} + \beta R_2} = \frac{R_a}{\frac{1}{g_m} + R_2} \stackrel{!}{=} 1$$


$$\Rightarrow R_a = R_2 + \frac{1}{g_m} = R_2 + \frac{U_T}{I_c} \Rightarrow \frac{U_a}{I_c} = R_2 + \frac{U_T}{I_c}$$

$$\Rightarrow U_a = I_c R_2 + U_T \Rightarrow 5U_{BE} = I_0 \frac{B}{B+1} R_2 + U_T$$

$$\Rightarrow I_0 = \frac{5U_{BE} - U_T}{\frac{B}{B+1} R_2}$$

### Aufgabe 4

a)

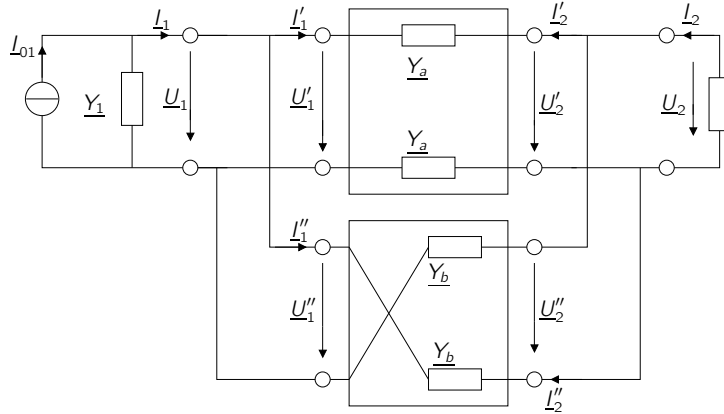

b)

i) PPK

ii)  $\underline{Y}$ -Parameter, weil

$$\underline{U}'_1 = \underline{U}''_1 = \underline{U}_1; \quad \underline{U}'_2 = \underline{U}''_2 = \underline{U}_2; \quad \underline{I}_1 = \underline{I}'_1 + \underline{I}''_1; \quad \underline{I}_2 = \underline{I}'_2 + \underline{I}''_2;$$

$$\begin{aligned} \underline{I}_1 &= \underline{Y}'_{11}\underline{U}'_1 + \underline{Y}''_{11}\underline{U}''_1 + \underline{Y}'_{12}\underline{U}'_2 + \underline{Y}''_{12}\underline{U}''_2 = \underline{Y}'_{11}\underline{U}_1 + \underline{Y}''_{11}\underline{U}_1 + \underline{Y}'_{12}\underline{U}_2 + \underline{Y}''_{12}\underline{U}_2 \\ &= (\underline{Y}'_{11} + \underline{Y}''_{11})\underline{U}_1 + (\underline{Y}'_{12} + \underline{Y}''_{12})\underline{U}_2 \end{aligned}$$

$$\begin{aligned} \underline{I}_2 &= \underline{Y}'_{21}\underline{U}'_1 + \underline{Y}''_{21}\underline{U}''_1 + \underline{Y}'_{22}\underline{U}'_2 + \underline{Y}''_{22}\underline{U}''_2 = \underline{Y}'_{21}\underline{U}_1 + \underline{Y}''_{21}\underline{U}_1 + \underline{Y}'_{22}\underline{U}_2 + \underline{Y}''_{22}\underline{U}_2 \\ &= (\underline{Y}'_{21} + \underline{Y}''_{21})\underline{U}_1 + (\underline{Y}'_{22} + \underline{Y}''_{22})\underline{U}_2 \end{aligned}$$

$$\Rightarrow \underline{Y} = \underline{Y}' + \underline{Y}''$$

c)

$$\underline{Y}'_{11} = \left. \frac{\underline{I}'_1}{\underline{U}'_1} \right|_{\underline{U}'_2=0} = \frac{\underline{Y}_a}{2} \quad \underline{Y}'_{12} = \left. \frac{\underline{I}'_1}{\underline{U}'_2} \right|_{\underline{U}'_1=0} = -\frac{\underline{Y}_a}{2}$$

$$\underline{Y}'_{21} = \left. \frac{\underline{I}'_2}{\underline{U}'_1} \right|_{\underline{U}'_2=0} = -\frac{\underline{Y}_a}{2} \quad \underline{Y}'_{22} = \left. \frac{\underline{I}'_2}{\underline{U}'_2} \right|_{\underline{U}'_1=0} = \frac{\underline{Y}_a}{2}$$

$$\Rightarrow \underline{Y}' = \begin{pmatrix} \frac{\underline{Y}_a}{2} & -\frac{\underline{Y}_a}{2} \\ -\frac{\underline{Y}_a}{2} & \frac{\underline{Y}_a}{2} \end{pmatrix}$$

$$\underline{Y}_{11}'' = \left. \frac{I_1''}{U_1''} \right|_{U_2''=0} = \frac{Y_b}{2} \quad \underline{Y}_{12}'' = \left. \frac{I_1''}{U_2''} \right|_{U_1''=0} = \frac{Y_b}{2}$$

$$\underline{Y}_{21}'' = \left. \frac{I_2''}{U_1''} \right|_{U_2''=0} = \frac{Y_b}{2} \quad \underline{Y}_{22}'' = \left. \frac{I_2''}{U_2''} \right|_{U_1''=0} = \frac{Y_b}{2}$$

$$\Rightarrow \underline{Y}' = \begin{pmatrix} \frac{Y_b}{2} & \frac{Y_b}{2} \\ \frac{Y_b}{2} & \frac{Y_b}{2} \end{pmatrix}$$

$$\Rightarrow \underline{Y} = \underline{Y}' + \underline{Y}'' = \begin{pmatrix} \frac{Y_b+Y_a}{2} & \frac{Y_b-Y_a}{2} \\ \frac{Y_b-Y_a}{2} & \frac{Y_b+Y_a}{2} \end{pmatrix}$$

d)

$$U_2 = -\frac{I_2}{Y_2}$$

$$I_1 = Y_{11}U_1 + Y_{12}U_2 = Y_{11}U_1 - \frac{Y_{12}}{Y_2}I_2 \iff U_1 = \frac{1}{Y_{11}}I_1 + \frac{Y_{12}}{Y_2 Y_{11}}I_2$$

$$\Rightarrow I_2 = Y_{21}U_1 + Y_{22}U_2 = \frac{Y_{21}}{Y_{11}}I_1 + \frac{Y_{12}Y_{21}}{Y_{11}Y_2}I_2 - \frac{Y_{22}}{Y_2}I_2$$

$$\iff I_2 \left(1 - \frac{Y_{12}Y_{21}}{Y_{11}Y_2} + \frac{Y_{22}}{Y_2}\right) = \frac{Y_{21}}{Y_{11}}I_1$$

$$\iff I_2 \frac{Y_{11}Y_2 - Y_{12}Y_{21} + Y_{22}Y_{11}}{Y_{11}Y_2} = \frac{Y_{21}}{Y_{11}}I_1$$

$$\iff F_I = \frac{I_2}{I_1} = \frac{Y_{21}Y_2}{Y_{11}Y_2 - Y_{12}Y_{21} + Y_{22}Y_{11}}$$

$$F_I = 0 \text{ für } Y_{21} = 0 \iff \frac{Y_b - Y_a}{2} = 0 \iff Y_a = Y_b$$

## Aufgabe 5

a)

$$Y_{out} = \frac{1}{\left(\frac{1}{sC} + \frac{RsL}{R+sL} + r_x\right)}$$

b)

Oszillation:

Stromfluss muss möglich sein,  
Anregung mit Spannungsquelle die mit  $t \mapsto \infty$  verschwindet.

$$Y = \frac{I}{U} \Big|_{U \rightarrow \infty}$$

c)

$$\begin{aligned} Y_{out} &= \frac{1}{\frac{1}{sC} + \frac{RsL}{R+sL} + r_x} = \frac{sC(R+sL)}{R+sL + RsLsC + r_x sC(R+sL)} \\ &\Rightarrow s^2(LCr_x + RCL) + s(L + RCr_x) + R \stackrel{!}{=} 0 \\ &\Rightarrow s^2 + s \cdot \frac{L + RCr_x}{LC(R+r_x)} + \frac{R}{LC(R+r_x)} = 0 \\ s_{1,2} &= -\frac{1}{2} \cdot \frac{L + RCr_x}{LC(R+r_x)} \pm \sqrt{\left(\frac{L + RCr_x}{2LC(R+r_x)}\right)^2 - \frac{R}{LC(R+r_x)}} \end{aligned}$$


d)

konstante Amplitude wenn  $\Re(s) = 0 = \sigma \Rightarrow r_x = -\frac{L}{RC}$

e)

Schwingfrequenz:  $s = \sigma + j\omega = 0 + j\sqrt{\frac{R}{LC(R + (-\frac{L}{RC})})}$  mit  $R - \frac{L}{RC} > 0 \rightarrow R^2 > \frac{L}{C}$

f)

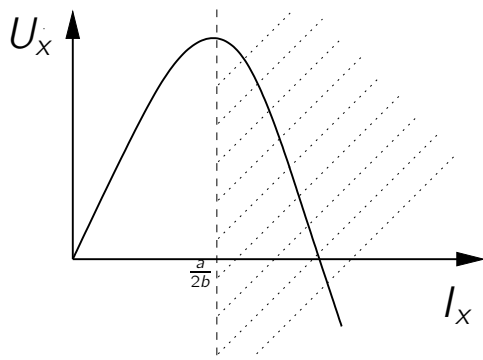

g)

$$\begin{aligned} U &= aI - bI^2 \\ \frac{dU}{dI} \Big|_{AP} &= r_x = a - 2bI \\ \Rightarrow \cdot) r_x < 0 &\Leftrightarrow a - 2bI < 0 \rightarrow I > \frac{a}{2b} \\ \cdot) r_x &\stackrel{!}{=} -\frac{L}{RC} \\ \Leftrightarrow a - 2bI &= -\frac{L}{RC} \rightarrow I = +\frac{1}{2b} \left( \frac{L}{RC} + a \right) \end{aligned}$$


### Aufgabe 6

a)

Torpaar 1 :  $I_1, I_4$

Torpaar 2 :  $I_2, I_3$


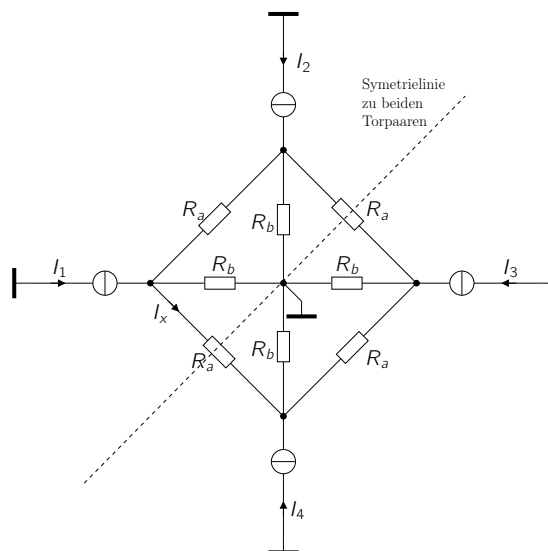
$$\begin{aligned} I_{14}^+ &= \frac{I_1 + I_4}{2} & I_{14}^- &= \frac{I_1 - I_4}{2} \\ I_{23}^+ &= \frac{I_2 + I_3}{2} & I_{23}^- &= \frac{I_2 - I_3}{2} \end{aligned}$$



b)

betrachte Torpaar 1 ,  $I_2 = I_3 = 0$   
Gleichtakt:  $I_x = 0$  ("freies Ende" bei  $\frac{R_a}{2}$ )

Gegentakt:

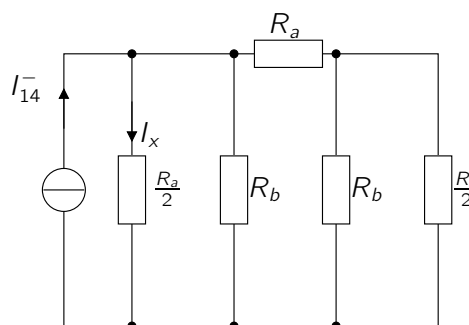
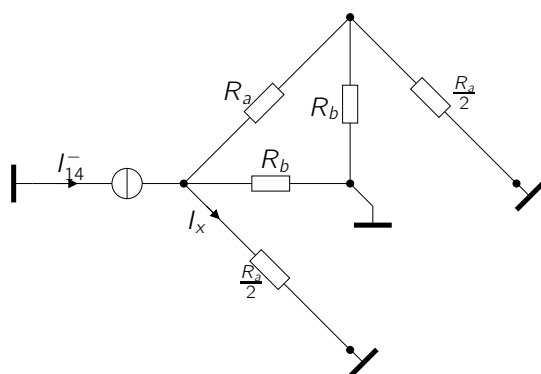


$$\frac{I_x}{I_{14}^-} = \frac{\frac{2}{R_a}}{\frac{2}{R_a} + \frac{1}{R_b} + \frac{1}{R_a + \frac{\frac{R_a R_b}{2}}{\frac{R_a}{2} + R_b}}} = \frac{\frac{2}{R_a}}{\frac{2}{R_a} + \frac{1}{R_b} + \frac{1}{R_a + \frac{R_a R_b}{R_a + 2R_b}}} = H_{14}$$



betrachte Torpaar 2,  $I_1 = I_4 = 0$   
 Gleichtakt:  $I_x = 0$  (s.o.)

Gegentakt:

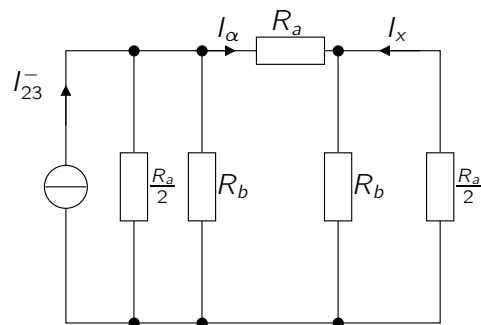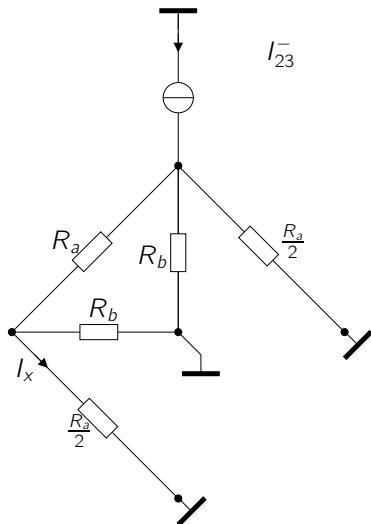

$$\frac{I_\alpha}{I_{23}^-} = -\frac{\frac{R_a}{2} // R_b}{R_a + 2(R_a // R_b)} \quad \frac{I_x}{I_\alpha} = \frac{R_b}{\frac{R_a}{2} + R_b} = \frac{2R_b}{2R_b + R_a}$$

$$\Rightarrow \frac{I_x}{I_{23}^-} = \frac{\frac{R_a}{2} // R_b}{R_a + 2(\frac{R_a}{2} // R_b)} \cdot \frac{2R_b}{2R_b + R_a} = H_{23}$$

$$I_x = H_{14}I_{14}^- + H_{23}I_{23}^- = \frac{H_{14}}{2}(I_1 - I_4) + \frac{H_{23}}{2}(I_2 - I_3)$$

## Aufgabe 7

a)

$$\frac{U_p}{U_1} = \frac{Z_2}{Z_1 + Z_2}$$

$$U_p = U_d + U_e \Leftrightarrow U_d = U_p - U_e$$

$$U_2 = v_u U_d \frac{Z_e}{R_a + Z_e} \Leftrightarrow U_2 = v_u (U_p - U_e) \frac{Z_e}{R_a + Z_e}$$

$$\Rightarrow U_2 (1 + v_u \frac{Z_e}{R_a + Z_e}) = U_p v_u \frac{Z_e}{R_a + Z_e}$$

$$\frac{U_2}{U_p} = \frac{v_u \frac{Z_e}{R_a + Z_e}}{1 + v_u \frac{Z_e}{R_a + Z_e}}$$

$$\Rightarrow F = \frac{U_p}{U_1} \frac{U_2}{U_p} = \frac{Z_2}{Z_1 + Z_2} \cdot \frac{v_u \frac{Z_e}{R_a + Z_e}}{1 + v_u \frac{Z_e}{R_a + Z_e}}$$

c)

$$\alpha R_1 \gg R_a \Rightarrow \tilde{\omega} = \frac{1}{\frac{1}{\omega_2} + 0} = \omega_2$$

$$F_k = \frac{1}{1 + j\frac{\omega}{\omega_1}} \cdot \underbrace{\frac{\alpha(1 + j\frac{\omega}{\omega_2})}{(1 + \alpha)(1 + j\frac{\omega}{\omega_2})}}_{\approx \frac{\alpha}{\alpha} \approx 0} \cdot \frac{j\frac{\omega}{\omega_2}}{1 + j\frac{\omega}{\omega_2}}$$

$$= \frac{j\frac{\omega}{\omega_2}}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2})}$$

$$\omega_1 = 10\omega_0 = \frac{R_1}{L_1}; \quad \omega_2 = \frac{\omega_0}{10} = \frac{R_2}{L_1}$$

b)

$$F_k = \frac{Z_2'}{Z_1' + Z_2'} \frac{v_u' \frac{Z_e'}{R_a + Z_e'}}{1 + v_u' \frac{Z_e'}{R_a + Z_e'}} \cdot \frac{Z_2''}{Z_1'' + Z_2''} \frac{v_u'' \frac{Z_e''}{R_a + Z_e''}}{1 + v_u'' \frac{Z_e''}{R_a + Z_e''}}$$

$$\underline{Z}_1' = R_1; \underline{Z}_2' = j\omega L_2; \underline{Z}_1'' = j\omega L_1; \underline{Z}_2'' = R_2; |\underline{Z}_e| \mapsto \infty;$$

$$\underline{Z}_e' = \underline{Z}_1'' + \underline{Z}_2'' = R_2 + j\omega L_1; v_u' = v_u'' = \alpha \in \mathbb{R}, \alpha \gg 1$$

$$F_k = \frac{j\omega L_2}{R_1 + j\omega L_2} \frac{\alpha \frac{R_2 + j\omega L_1}{R_a + R_2 + j\omega L_1}}{1 + \alpha \frac{R_2 + j\omega L_1}{R_a + R_2 + j\omega L_1}} \cdot \frac{R_2}{R_2 + j\omega L_1} \frac{\alpha}{1 + \alpha}$$

$$\underset{|\underline{Z}_e| \mapsto \infty}{\approx} \frac{1}{1 + j\frac{L_2}{R_1}} \cdot \frac{\alpha(1 + j\frac{L_1}{R_2})}{(1 + \alpha)(1 + j\frac{L_1}{R_2} + \frac{R_a}{(1 + \alpha)R_2})} \cdot \frac{j\omega \frac{L_1}{R_2}}{1 + j\omega \frac{L_1}{R_2}} \cdot \frac{\alpha}{1 + \alpha}$$

$$= \frac{1}{1 + j\frac{\omega}{\omega_1}} \cdot \frac{\alpha(1 + j\frac{\omega}{\omega_2})}{(1 + \alpha)(1 + j\frac{\omega}{\tilde{\omega}})} \cdot \frac{j\frac{\omega}{\omega_2}}{1 + j\frac{\omega}{\omega_2}}$$

$$\omega_1 = \frac{R_1}{L_2}; \quad \omega_2 = \frac{R_2}{L_1};$$

$$\tilde{\omega} = \frac{1}{\frac{L_1}{R_2} + \frac{1}{\omega(1 + \alpha)R_2}} = \frac{1}{\frac{1}{\omega_2} + \frac{1}{\omega(1 + \alpha)R_2}}$$

d)

