 


Chapter 4

Basis of analog MOS circuit

- Inverter circuit
- Differential amplifier
- Current mirror

Characteristics of differential amplifier



$$U_{out} = A \cdot (U_{in1} - U_{in2})$$

(The gain A -> infinite)

U_{out} is saturated high at U_{DD} and low at U_{SS}

$$I_{in1} = I_{in2} = 0$$


With a proper feedback, U_{out} can ensure that $U_{in1} = U_{in2}$

There is no current in the inputs of the differential amplifier


The buffer circuit

$$A = \frac{U_{out}}{U_{in}} = 1$$

Purpose: U_{in} is unloaded

 

Design of differential input

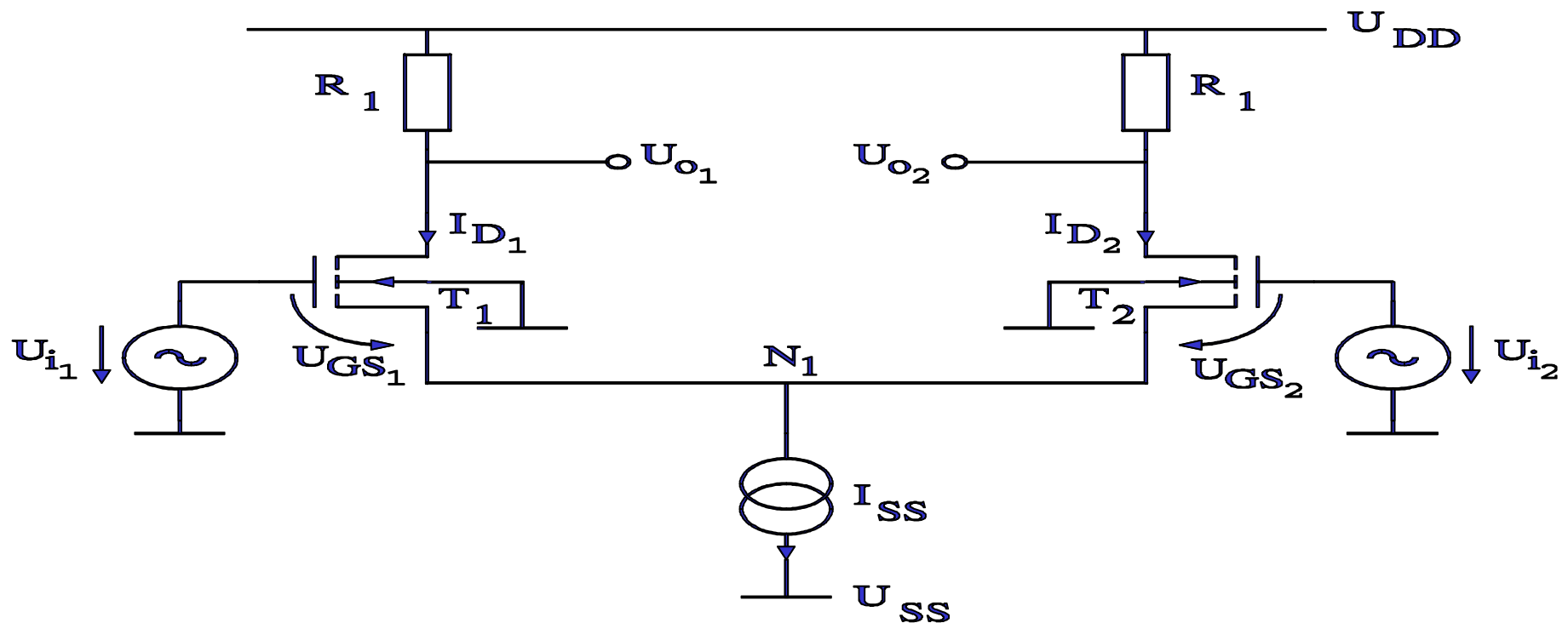

For currents:

$$I_{D1} + I_{D2} = I_{SS}$$


At common mode:

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

with
$$I_D = \frac{I_{SS}}{2} = \frac{W}{2 \cdot L} \cdot \beta_0 \cdot (U_{GS} - U_T)^2$$

Operation range (quasi- linear)

Large signal behaviour

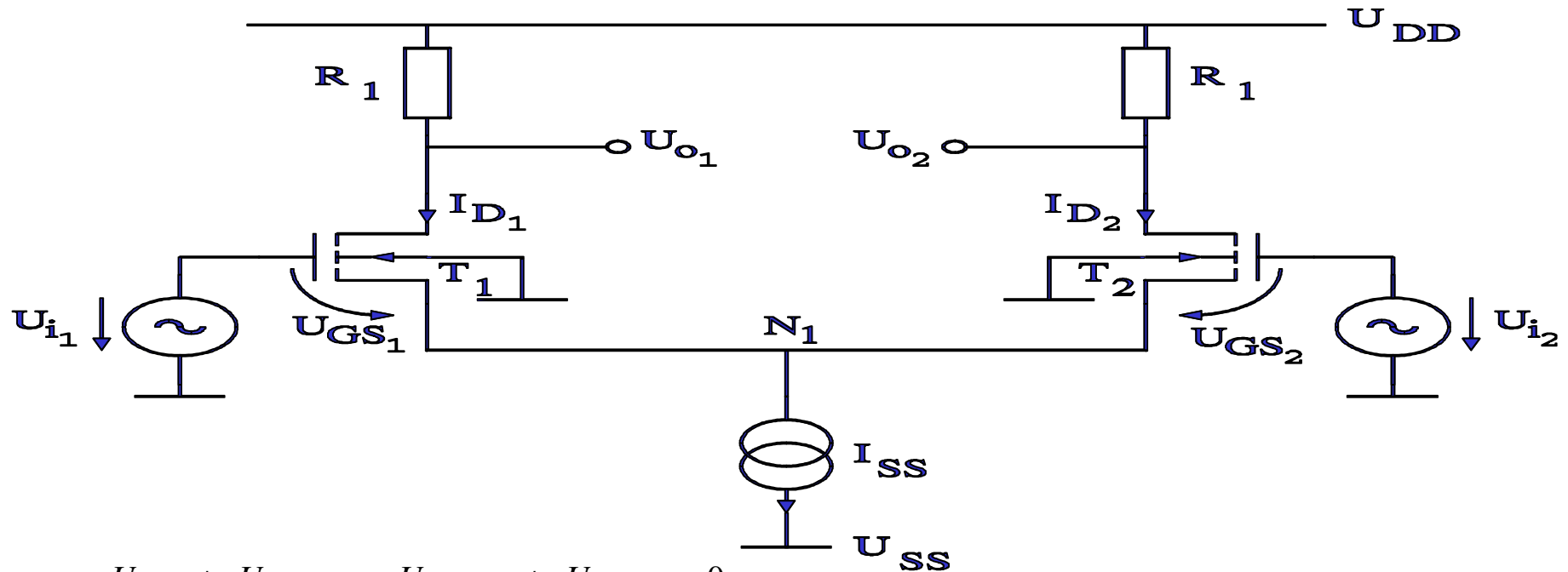

$$-U_{i1} + U_{GS1} - U_{GS2} + U_{i2} = 0$$

$$\underbrace{U_{i1} - U_{i2}}_{\Delta U_i} = U_{GS1} - U_{GS2}$$

$$I_D = \frac{\beta}{2} \cdot (U_{GS} - U_T)^2 \quad \Rightarrow \quad U_{GS} = \sqrt{\frac{2 \cdot I_D}{\beta}} + U_T$$

with $U_{T1} = U_{T2} = U_T$ & $\beta_1 = \beta_2 = \beta$


$$\Delta U_i = U_{GS1} - U_{GS2} = \sqrt{\frac{2 \cdot I_{D1}}{\beta}} - \sqrt{\frac{2 \cdot I_{D2}}{\beta}}$$

Operation range (quasi- linear)

Large signal behaviour

$$\Delta U_i = U_{GS1} - U_{GS2} = \sqrt{\frac{2 \cdot I_{D1}}{\beta}} - \sqrt{\frac{2 \cdot I_{D2}}{\beta}}$$

 mit $I_{D1} + I_{D2} = I_{SS}$ wird $I_{D1} = f(I_{SS}, \Delta U_i)$



Operation range (quasi- linear)

Large signal behaviour

1) Differential voltage

$$\Delta U_i = 0 \quad I_D = \frac{I_{SS}}{2}$$

$$U_{GS_{1,2o}} = \sqrt{\frac{I_{SS}}{\beta}} + U_T$$

$$\Rightarrow U_{GS_{eff} \ 1,2o} = \sqrt{\frac{I_{SS}}{\beta}}$$

a) Differential input voltage = 0 (common mode)

$$U_{GS} = \sqrt{\frac{2 \cdot I_D}{\beta}} + U_T$$

$$U_{GS_{eff}} = U_{GS} - U_T$$

Operation range (quasi- linear)

Large signal behaviour

1) Differential voltage

b) Differential input voltage < 0

Assumption: T_1 is off, 100% of the current I_{SS} through T_2


$$U_{GS1} \approx U_T$$

$$U_{GS2} = U_{GS_{eff}2} + U_T$$

$$\Delta U_i \gg 0 \quad I_{D2} = I_{SS} \quad U_{GS2} = \sqrt{\frac{2 \cdot I_{SS}}{\beta}} + U_T$$

$$\Rightarrow \Delta U_{i \max} = U_{GS2} - U_{GS1} = U_{GS_{eff}2}$$
 
$$= \sqrt{\frac{2 \cdot I_{SS}}{\beta}} = \sqrt{2} \cdot U_{GS_{eff}1,2o}$$



Operation range (quasi- linear)

Large signal behaviour


2) Common Mode Voltage

a) Maximum common mode input voltage,
so that transistors are in saturation

$$U_{DS} \geq U_{GS} - U_T(U_{SB})$$

Limit of the saturation :

$$\Rightarrow U_D = U_G - U_T(U_{SB})$$

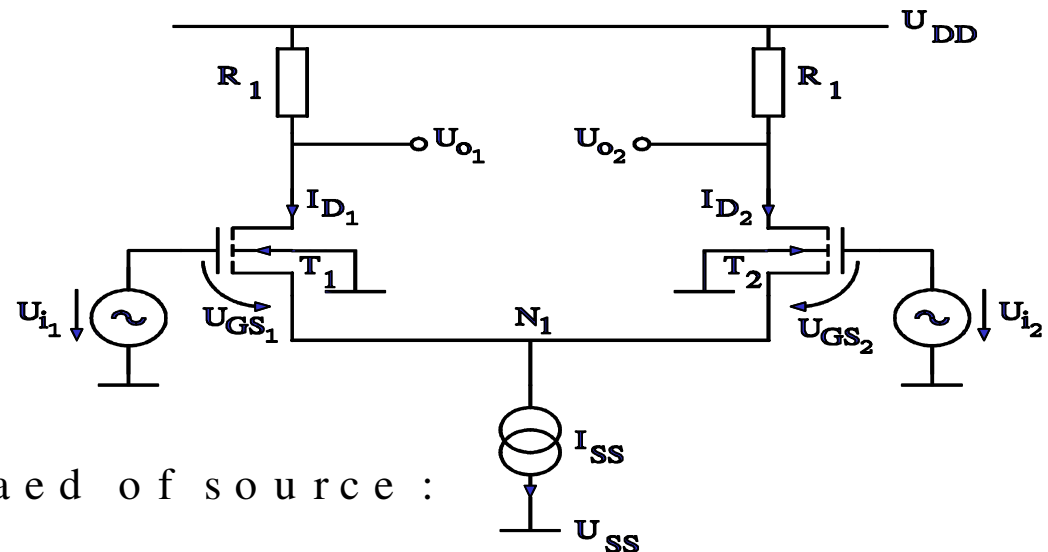

Referred to Ground instead of source :

$$U_G = U_{in} \text{ and } U_D = U_{DD} - I_D \cdot R$$

$$U_{in \max} = U_{DD} - \frac{I_{SS}}{2} \cdot R + U_T(U_{SB} > 0)$$

$$U_{SB} = U_{N1} = U_{DD} - \frac{I_{SS}}{2} \cdot R - U_{GS \text{ eff } 1,2 o}$$


Operation range (quasi- linear)

Large signal behaviour

2) Common Mode

b) Maximum common mode input voltage,
so that transistors are in saturation

Numerical example:

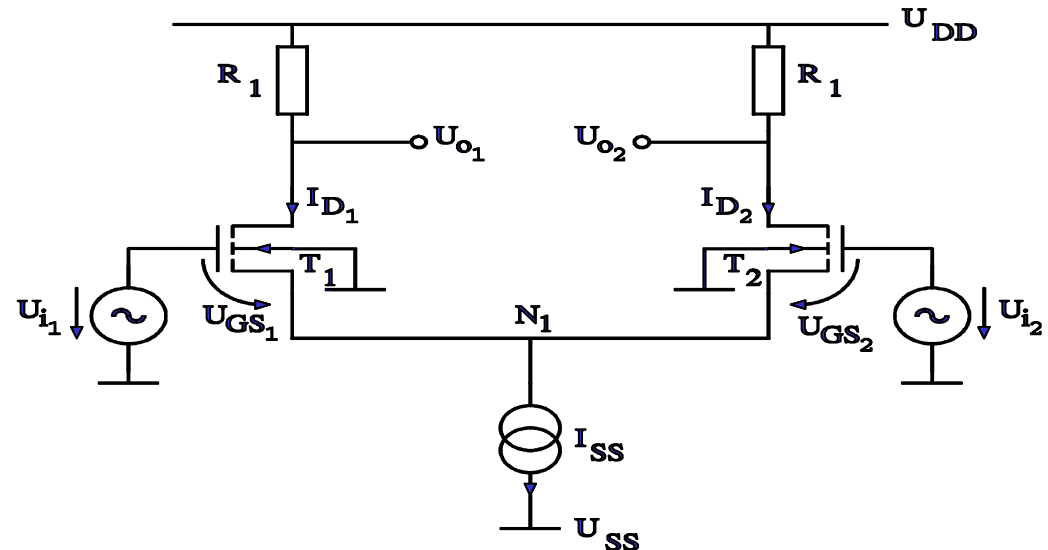

Transistor parameters:

$$\beta_0 = 93,2 \mu A / V^2; U_T = 1V; \gamma = 1 \sqrt{V}; \Phi_D = 0,7V$$

Circuit parameters:

$$I_{SS} = 100 \mu A; R = 10 k\Omega; W/L = 10, U_{DD} = 5V$$

Calculated operating parameters:

$$U_{GS_{eff1,2o}} = 0,33V;$$

$$U_{SB} = 5V - 100 \mu A \cdot 10 k\Omega / 2 - 0,33V = 4,17V, U_T = 2,18V$$

maximum constant input voltage:

$$U_{in_{max}} = 5V - 100 \mu A \cdot 10 k\Omega / 2 + 2,18V = 6,68V$$

Operation range (quasi- linear)

Large signal behaviour

2) Common Mode

b) minimum common mode input voltage,
so that current I_{SS} can flow

$$U_{GS_{1,2}} = \sqrt{\frac{I_{SS}}{\beta}} + U_T(U_{SB})$$

Node potential U_{N1} minimum $U_{SS} \rightarrow U_{SB}=0$

$$U_{in\ min} = \sqrt{\frac{I_{SS}}{\beta}} + U_T + U_{SS} \quad \text{mit} \quad U_{SB} \approx 0$$

Numerical example:

Transistor parameters:

$$\beta_0 = 93,2 \mu A / V^2; U_T = 1V; \gamma = 1 \sqrt{V}; \Phi_D = 0,7V$$

Circuit parameters:

$$I_{SS} = 100 \mu A; R = 10 k\Omega; W/L = 10, U_{DD} = 5V$$

$$U_{in\ min} = 1,33V \text{ above } U_{SS}$$


$$U_{in\ max} - U_{in\ min} = 6,68V - 1,33V = 5,35V \approx U_{DD} - U_{SS}$$

Operation range (quasi- linear)

Common Mode Input


$$U_{in \max} = U_{DD} - \frac{I_{SS}}{2} \cdot R + U_T \quad (U_{SB} > 0)$$
 
$$U_{in \min} = \sqrt{\frac{I_{SS}}{\beta}} + U_T$$



Maximum input difference: $\sqrt{\frac{2 \cdot I_{SS}}{\beta}}$

Small signal behaviour

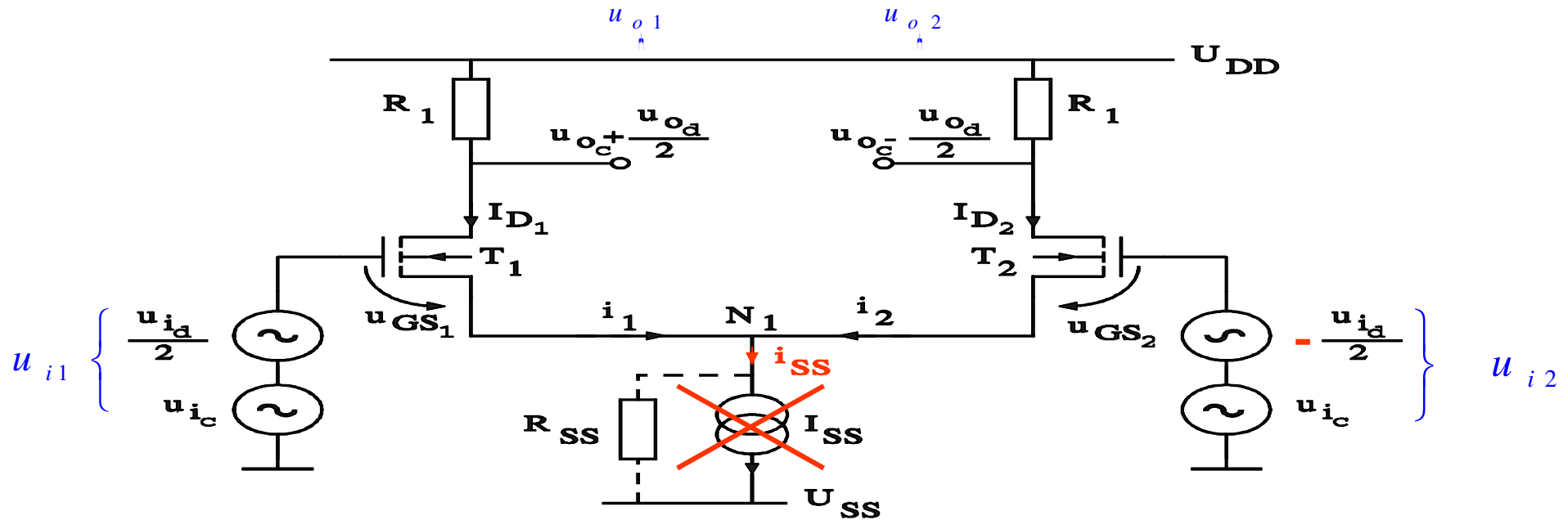

Splitting into common mode and differential voltage

$$u_{id} = u_{i1} - u_{i2}$$

$$u_{od} = u_{o1} - u_{o2}$$

$$u_{ic} = \frac{u_{i1} + u_{i2}}{2}$$

$$u_{oc} = \frac{u_{o1} + u_{o2}}{2}$$


$$u_{i1} = u_{ic} + \frac{1}{2} \cdot u_{id}$$

$$u_{o1} = u_{oc} + \frac{1}{2} \cdot u_{od}$$

$$u_{i2} = u_{ic} - \frac{1}{2} \cdot u_{id}$$

$$u_{o2} = u_{oc} - \frac{1}{2} \cdot u_{od}$$

Small signal behaviour

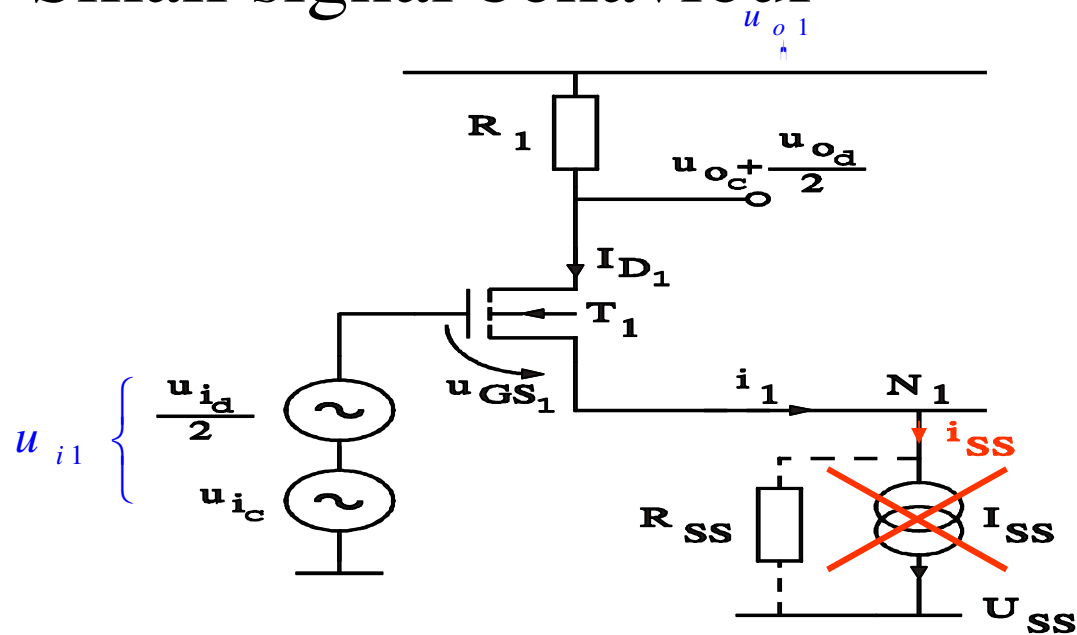

Differential Mode

$$u_{i1} = u_{ic} + \frac{1}{2} \cdot u_{id} \qquad u_{i2} = u_{ic} - \frac{1}{2} \cdot u_{id}$$


$$u_{ic} = 0 \quad \Rightarrow \quad u_{oc} = 0$$

$$\frac{1}{2} \cdot u_{id} = \left| -\frac{1}{2} \cdot u_{id} \right| \quad \Rightarrow \quad i_1 = -i_2 \quad \Rightarrow \quad i_{ss} = 0$$

=> N1 is in small signal domain behaviour ground!

Equivalent circuit diagram for differential mode

(Small signal behaviour)

 


$$\frac{1}{2} \cdot u_{od} = A_{VDM} \cdot \frac{1}{2} \cdot u_{id}$$

$$A_{VDM} = -g \cdot r_{out}$$

$$= -g_{m1} \cdot (R_1 \parallel r_{DS1})$$



$$\approx -g_{m1} \cdot R_1$$

 


$$g = \left. \frac{i_{out}}{u_{in}} \right|_{u_{out}=0} = \frac{g_m \cdot \frac{1}{2} \cdot u_{id}}{\frac{1}{2} \cdot u_{id}} = g_m$$

$$r_{out} = \left. \frac{u_{out}}{i_{out}} \right|_{u_{in}=0} = r_{DS1} \parallel R_1 = \frac{1}{\frac{1}{R_1} + \frac{1}{r_{DS1}}}$$

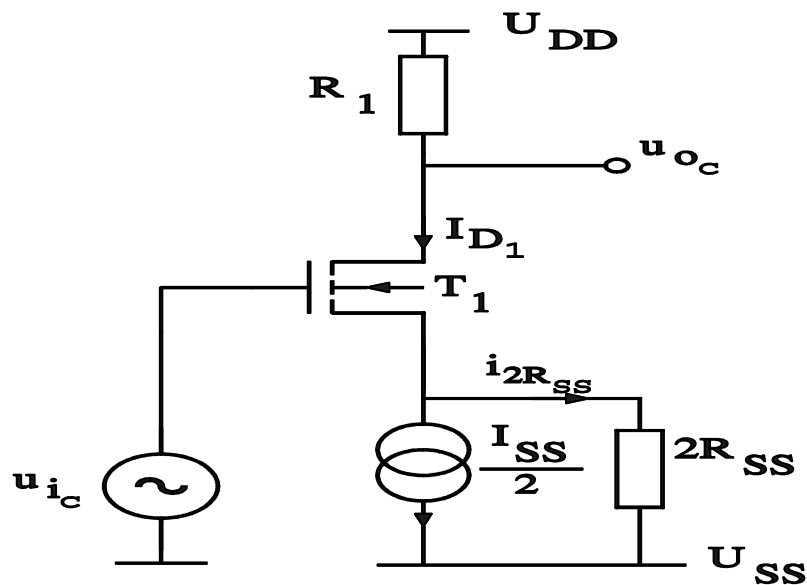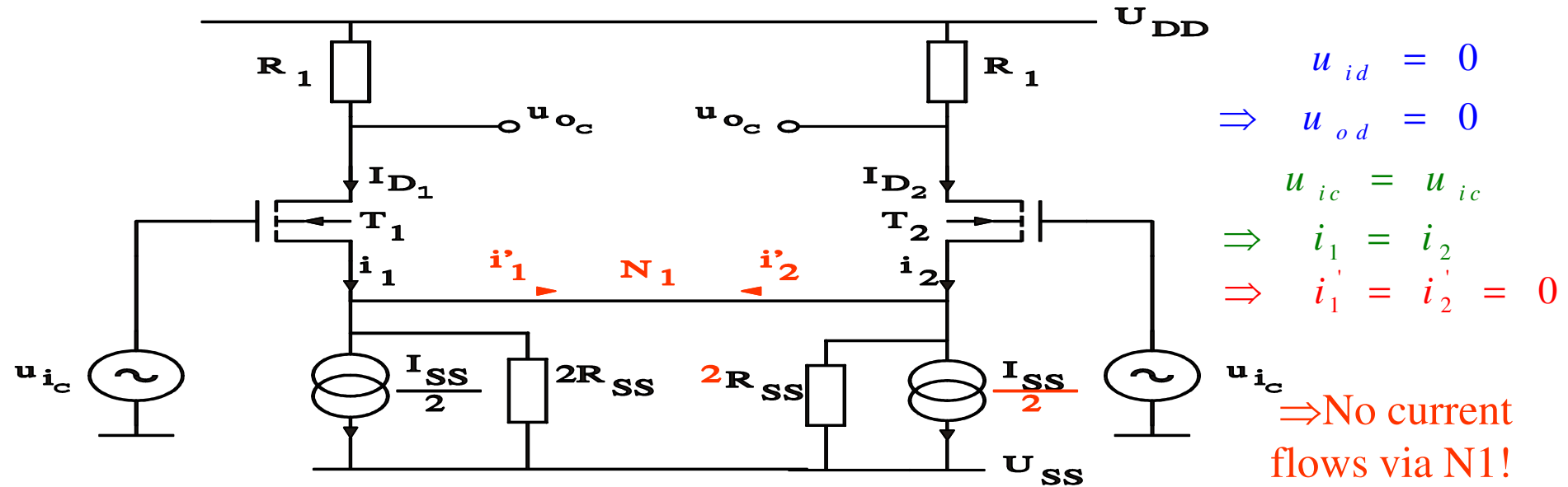Equivalent circuit diagram for common mode (Small signal behaviour)



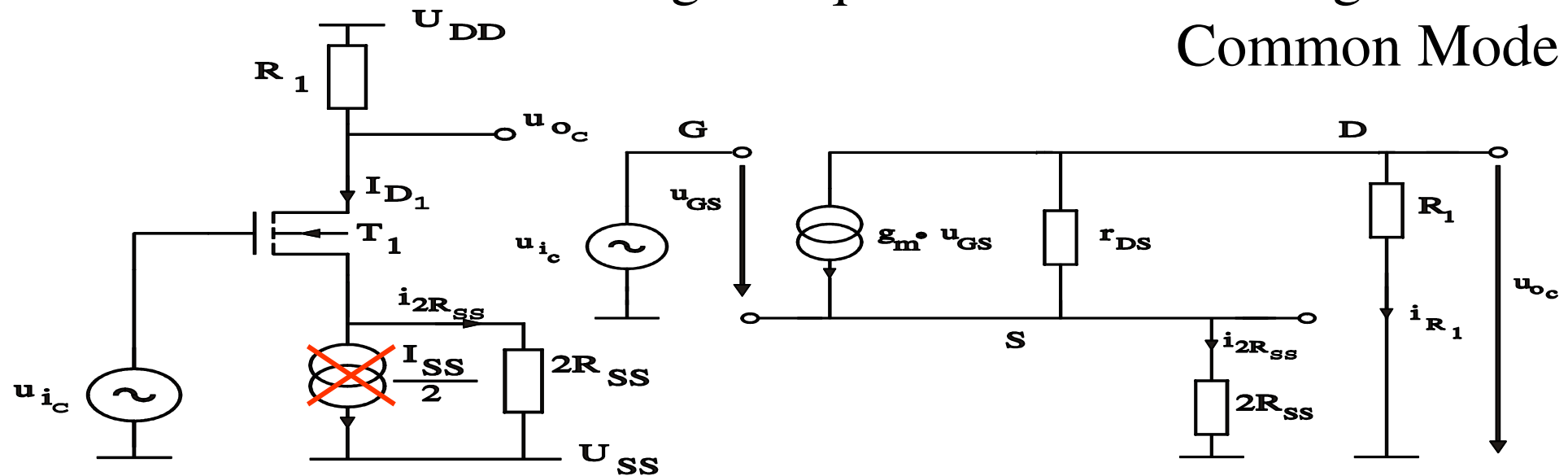Small signal equivalent circuit diagram for Common Mode



$$u_{ic} = u_{GS} + i_{2RSS} \cdot 2 \cdot R_{SS}$$

$$u_{oc} = -i_{2RSS} \cdot R_1$$

$$u_{oc} = i_{2RSS} \cdot 2 \cdot R_{SS} + (i_{2RSS} - g_m \cdot u_{GS}) \cdot r_{DS}$$

$$\left. \begin{aligned} \frac{i_{out}}{u_{out}} \Big|_{u_{ic}=0} &= ? \Rightarrow r_{out} \\ \frac{i_{out}}{u_{in}} \Big|_{u_{oc}=0} &= ? \Rightarrow g \end{aligned} \right\}$$

$$A_{VCM} = \frac{U_{oc}}{U_{ic}} = \frac{-g_m}{\frac{1}{r_{DS}} + \frac{1}{R_1} + \frac{2 \cdot R_{SS}}{R_1} \cdot \left(\frac{1}{r_{DS}} + g_m \right)} = \frac{-g_m}{\frac{1}{R_1} \cdot (1 + 2 \cdot R_{SS} \cdot g_m)}$$

mit $r_{DS} \gg R_1$, $g_m \gg g_{DS} = \frac{1}{r_{DS}}$ und $2 \cdot R_{SS} \cdot g_m \gg 1$

$$A_{VCM} \approx - \frac{R_1}{2 \cdot R_{SS}}$$

Common Mode Rejection Ratio: CMRR

$$A_{VDM} \approx -g_{m1} \cdot R_1$$

$$A_{VCM} \approx -\frac{R_1}{2 \cdot R_{SS}}$$

$$CMRR = \frac{A_{VDM}}{A_{VCM}} = 2 \cdot g_{m1} \cdot R_{SS}$$

For a good differential amplifier:

- R1 uncritical
- high Gm
- high Rss

By now:

$$A_{INV} \approx A_{VDM} \approx -g_{m1} \cdot R_1$$

$$C_{MRR} = \frac{A_{VDM}}{A_{VCM}} = 2 \cdot g_{m1} \cdot R_{SS}$$

What next?


How to realize a high g_m ?

$$\begin{aligned} g_m &= \frac{dI_D}{dU_{GS}} & I_D &= \frac{\beta}{2} \cdot (U_{GS} - U_T)^2 \\ g_m &= \beta \cdot (U_{GS} - U_T) \\ &= \beta \cdot U_{GSeff} & &= \sqrt{2 \cdot I_D \cdot \beta} & &= \frac{2 \cdot I_D}{U_{GSeff}} \end{aligned}$$

and

How to realize high resistances R_{SS} ?

Transistors as resistor

 

$$\frac{dI_D}{dU_{DS}} = g_{DS} = \frac{1}{r_{DS}}$$

$$G = \frac{1}{R} = \frac{I_D}{U_{DS}}$$

Small signal resistance

Large signal resistance

$$g_{DS} = I_D \cdot \lambda \Rightarrow g_{DS} = 9,3 \mu S$$



$$r_{DS} = 110 k \Omega$$

$$\Rightarrow R_{DS} = 20 k \Omega$$

Fixed potential (U_{GS}) necessary: other solution?

1) Transistor in „Diode circuit“

a) n-channel transistor

  

$$U_{DS} = U_{GS}$$

$$\Rightarrow U_{DS} > U_{GS} - U_T$$



$$\Rightarrow \text{Sättigung}$$

$$\Rightarrow I_D = \frac{\beta}{2} (U_{GS} - U_T)^2$$

$$r_{out} = \frac{u_{out}}{i_{out}} = \frac{u_{DS}}{i_{out}}$$


$$i_{out} = g_m \cdot u_{DS} + g_{DS} \cdot u_{DS}$$
  
$$r_{out} = \frac{1}{g_m + g_{DS}} \approx \frac{1}{g_m} \quad (\approx 1 \text{ k}\Omega)$$



Two-terminal-device „Diode“

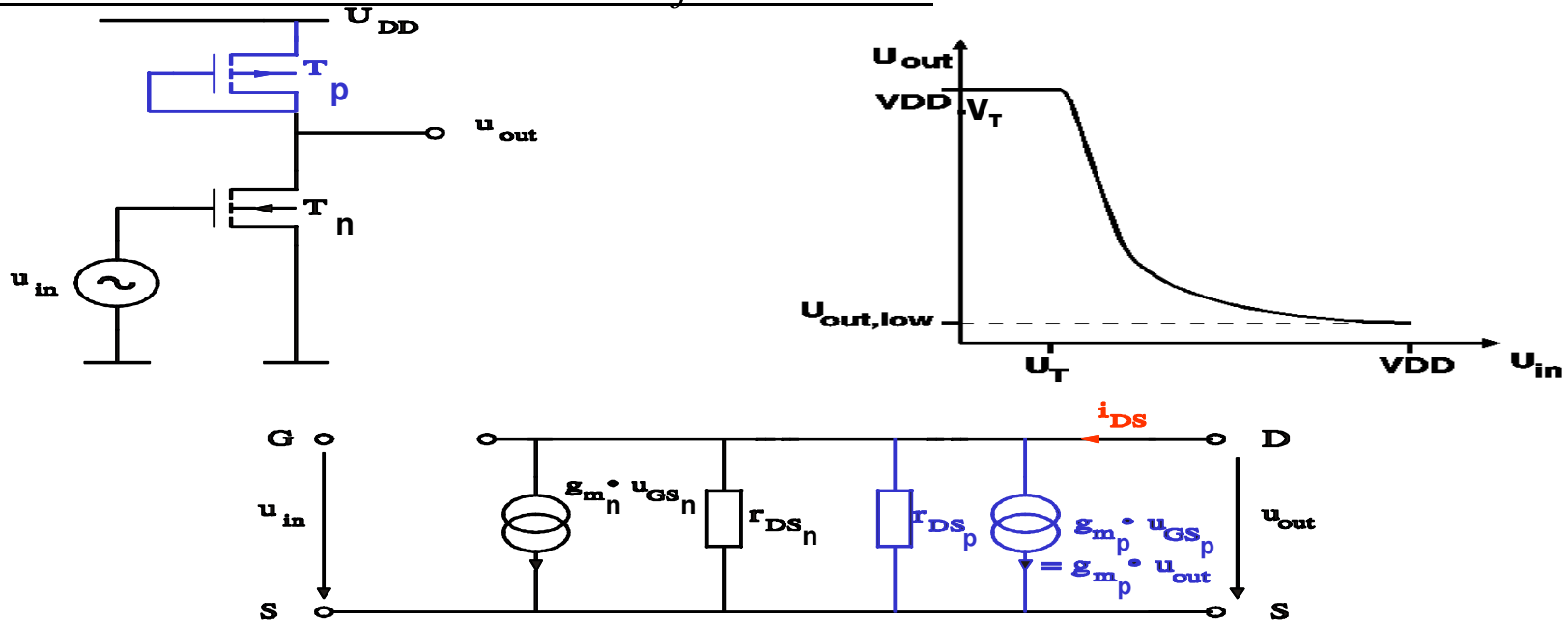b) p-channel transistor as the load of an inverter



$$A_V = -g_m \cdot r_{out}$$

with $g_m = g_{mn}$ und

$$r_{out} = \frac{1}{g_{mp} + g_{DSn} + g_{DSp}} \approx \frac{1}{g_{mp}}$$

$$A_V = -\frac{g_{mn}}{g_{mp}}$$

$$g_{mp} = \sqrt{2 \cdot I_D \cdot \beta_{0p} \cdot \left(\frac{W}{L}\right)_p} \quad g_{mn} = \sqrt{2 \cdot I_D \cdot \beta_{0n} \cdot \left(\frac{W}{L}\right)_n}$$

$$A_V = -\sqrt{\frac{\beta_{0n} \cdot \left(\frac{W}{L}\right)_n}{\beta_{0p} \cdot \left(\frac{W}{L}\right)_p}} \approx -\sqrt{\frac{3 \cdot \left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p}}$$

Example:



$$A_v = - \sqrt{\frac{\beta_{0n} \cdot \left(\frac{W}{L}\right)_n}{\beta_{0p} \cdot \left(\frac{W}{L}\right)_p}} \approx - \sqrt{\frac{3 \cdot \left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p}}$$

$$A_v = - \sqrt{\frac{3 \cdot \left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p}} = - \sqrt{\frac{3 \cdot \left(\frac{50}{5}\right)_n}{\left(\frac{5}{15}\right)_p}} \approx - 10$$

Summary: **MOS-diode provides only small resistance**,
as transconductance G_m contributes to the conductance.
 \Rightarrow long channel length is necessary


2) Transistor with fixed gate potential

  a) n-channel transistor with $U_G = \text{const.}$






$$r_{out} = r_{DS}$$

 b) p-channel transistor with $U_G = \text{const.}$



   b) Transistor with $U_G = \text{const.}$ as load of an inverter



$$A_v = -g_m \cdot r_{out}$$

with $g_m = g_{m\,n}$

and


$$r_{out} = r_{DSn} \parallel r_{DSp} = \frac{1}{g_{DSn} + g_{DSp}}$$

$$A_v = - \frac{g_{m\,n}}{g_{DSn} + g_{DSp}}$$

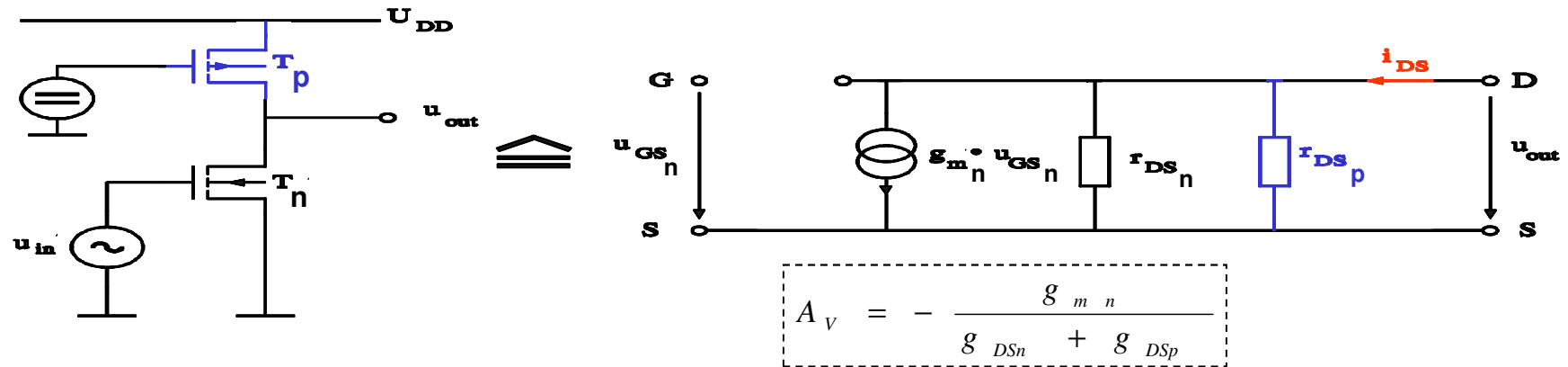Example:

$$A_v = - \frac{500 \, \mu S}{2.5 \, \mu S + 2.5 \, \mu S} \approx -100$$

Transistor with $U_G = \text{const.}$ as load



n-channel is driven /
p-channel as load

$$A_v = - \frac{g_{m_p}}{g_{DSn} + g_{DSp}}$$

p-channel is driven /
n-channel as load

