

Chapter 4

Basis of analog MOS circuit

- Inverter circuit
- Differential amplifier
- Current source / Current mirror
- Complete Circuit of an Amplifier

Current Source

Application:


Operating point biasing,
High ohmic load for
inverter / amplifier

Key parameters:


Output resistance r_{out} ,

Cutoff voltage


Absolute value (accuracy) I_0

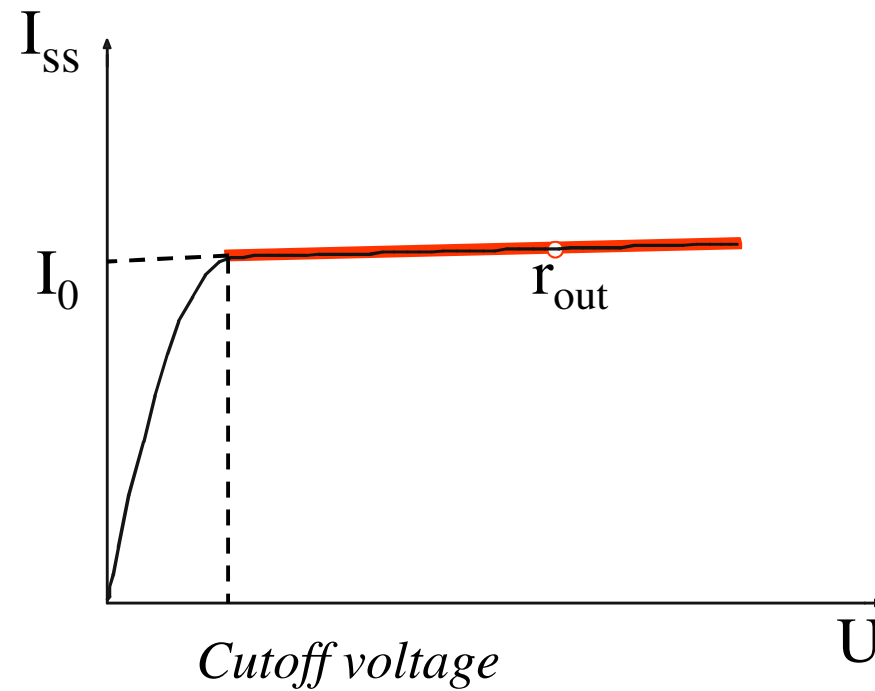

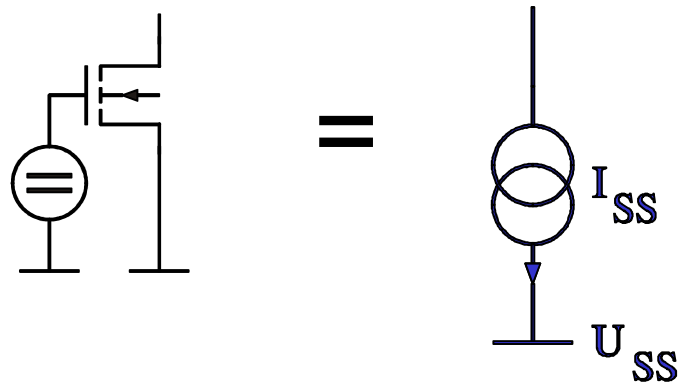
MOS-Output with fixed gate-source-voltage



Current sink

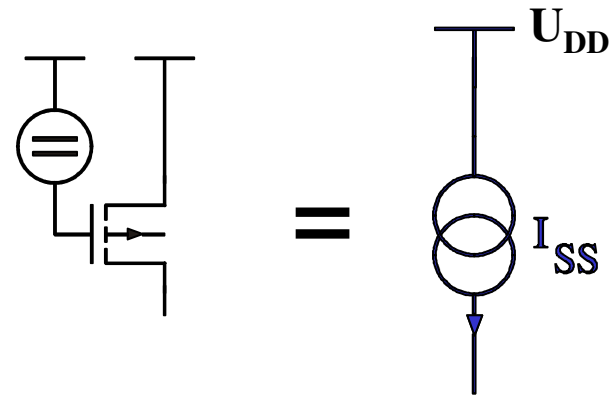

Current source

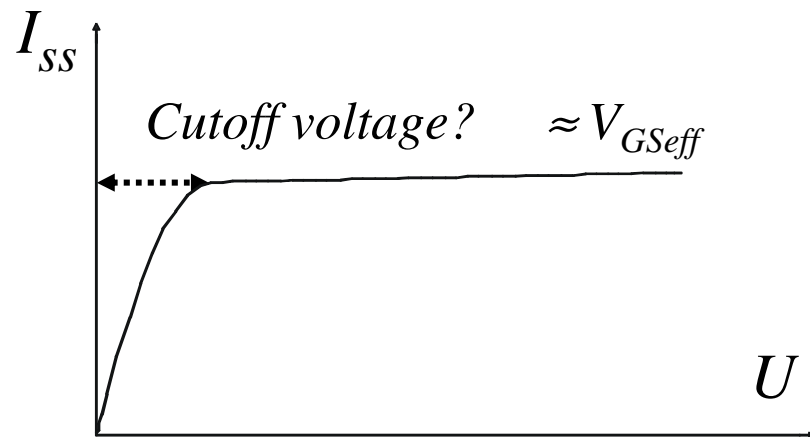

The transistor is mostly operated
in the Weak Inversion
/ Subthreshold mode.

How to achieve a fixed gate-source-voltage?


How to achieve a fixed gate-source-voltage?

Calculation of the operation point:

$$I_{ref} \cdot R_1 + U_{GS1} = U_{DD} + |U_{SS}|$$

$$U_{GS1} = U_{DD} + |U_{SS}| - I_{ref} \cdot R_1 = U_{GSeff} + U_T$$

$$U_{GSeff} \approx 0 \Rightarrow I_{ref} = \frac{U_{DD} + |U_{SS}| - U_T}{R_1}$$

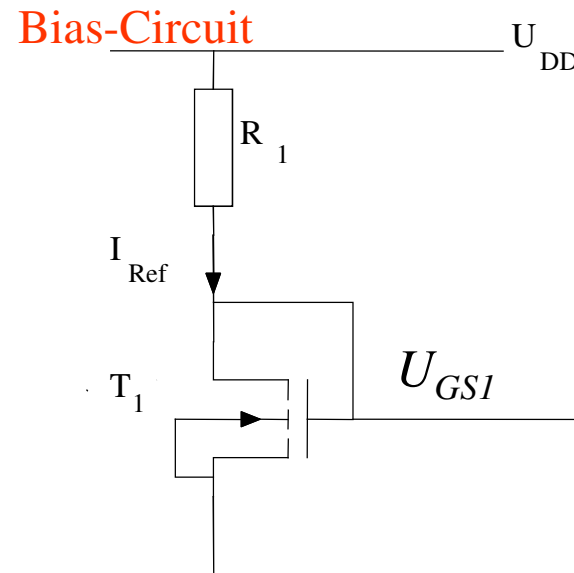

With this equation it is possible to set a reference current.

The transistor has to be dimensioned so that it operates in the subthreshold region.


The MOS-diode delivers the accordant U_{GS1}

Current mirror:

U_{GS1} constant ?

No, but I_{ref} nearly constant

$$I_{ref} \approx \frac{U_{DD} + |U_{SS}| - U_T}{R_1}$$

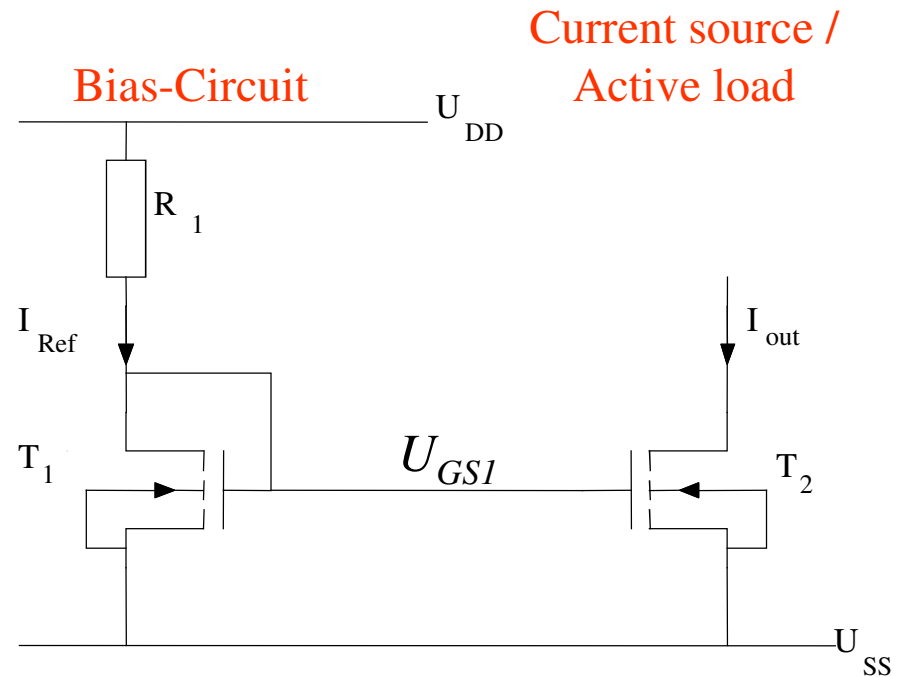

$$I_{ref} = I_{D1} = \frac{\beta_0}{2} \cdot \frac{W}{L} \bigg|_1 \cdot (U_{GS1} - U_{T1})^2$$

$$I_{D2} = \frac{\beta_0}{2} \cdot \frac{W}{L} \bigg|_2 \cdot (U_{GS1} - U_{T2})^2$$

$$I_{out} / I_{ref} = I_{D2} / I_{D1} = \frac{W}{L} \bigg|_2 / \frac{W}{L} \bigg|_1$$


if $T_1 = T_2$ ist $I_{D1} = I_{D2}$

But only if $U_{DS1} \approx U_{DS2}$

Or if L very large
($\lambda \approx 0$)

= mirror ratio

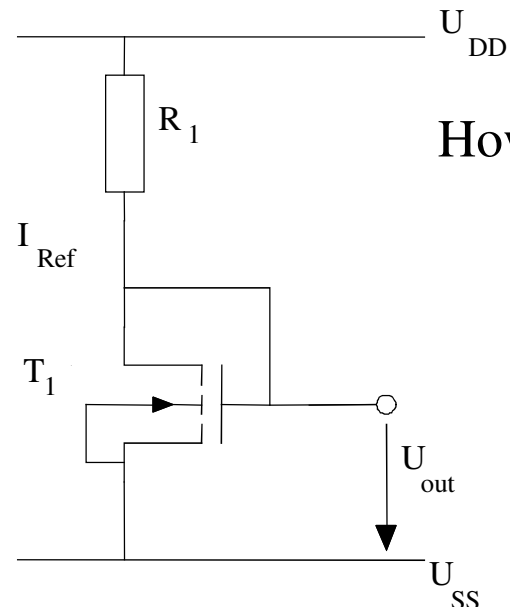Bias-circuit with MOS diode (p-channel) as the load




How to realize a bias-circuit with MOS solely?

$$U_{DD} = U_{GS3} + U_{GS1}$$

$$= \underbrace{\sqrt{\frac{2 \cdot I_D}{\beta_3}} + U_{T3}}_{U_{GSeff3}} + \underbrace{\sqrt{\frac{2 \cdot I_D}{\beta_1}} + U_{T1}}_{U_{GSeff1}}$$


$$\text{For } U_{T1} \approx |U_{T3}| \quad U_{GSeff1} \approx |U_{GSeff3}|$$

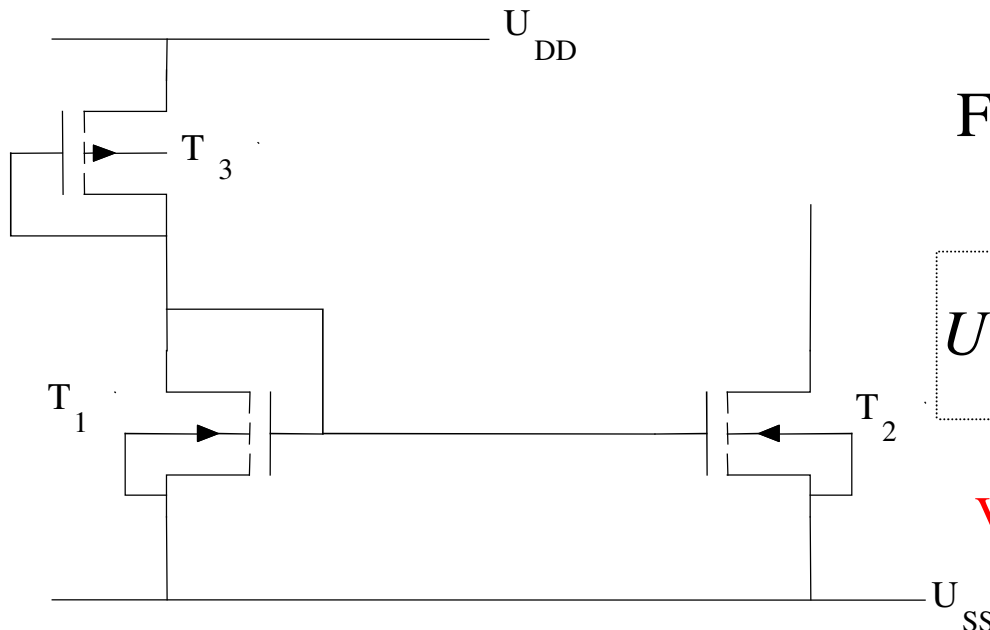

$$U_{GSeff} = \frac{U_{DD} - 2 \cdot U_T}{2} \Big|_{V_{dd}=5V} \approx 1,5V$$

Very small W/L required, e.g. 5/50

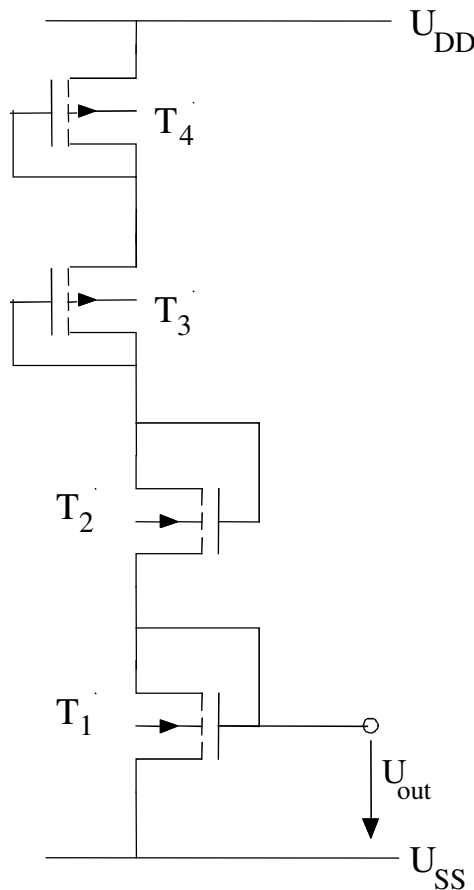Setting of current by effective gate-voltage



$$U_{GSeff} = \frac{U_{DD} - 4 \cdot U_T}{4} = \frac{5V - 4V}{4} = 0.25V$$

-> Reduction of U_{GS} to a reasonable value


$$\text{Bias-Strom: } I_D = \beta_0 \cdot \frac{W}{L} \cdot (U_{GS1} - U_{T1})^2$$

To consider:

Bulk ?


I_D sensitive to process variation

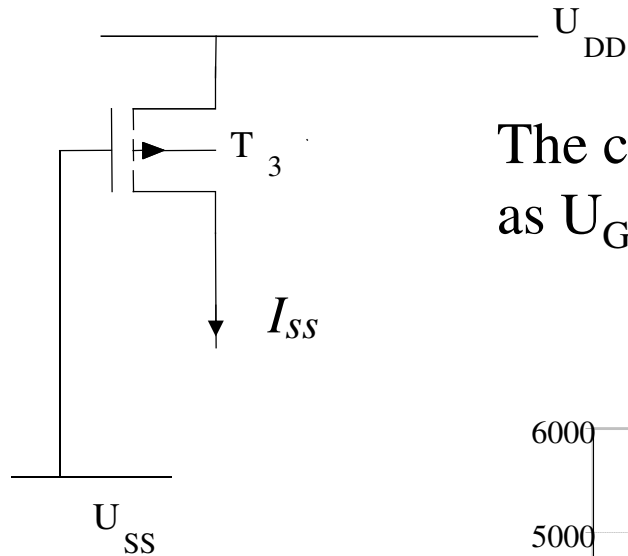Bias-circuit with supply voltage at gate-source




The characteristic curve is rather resistive,
as U_{GSeff} is very large.

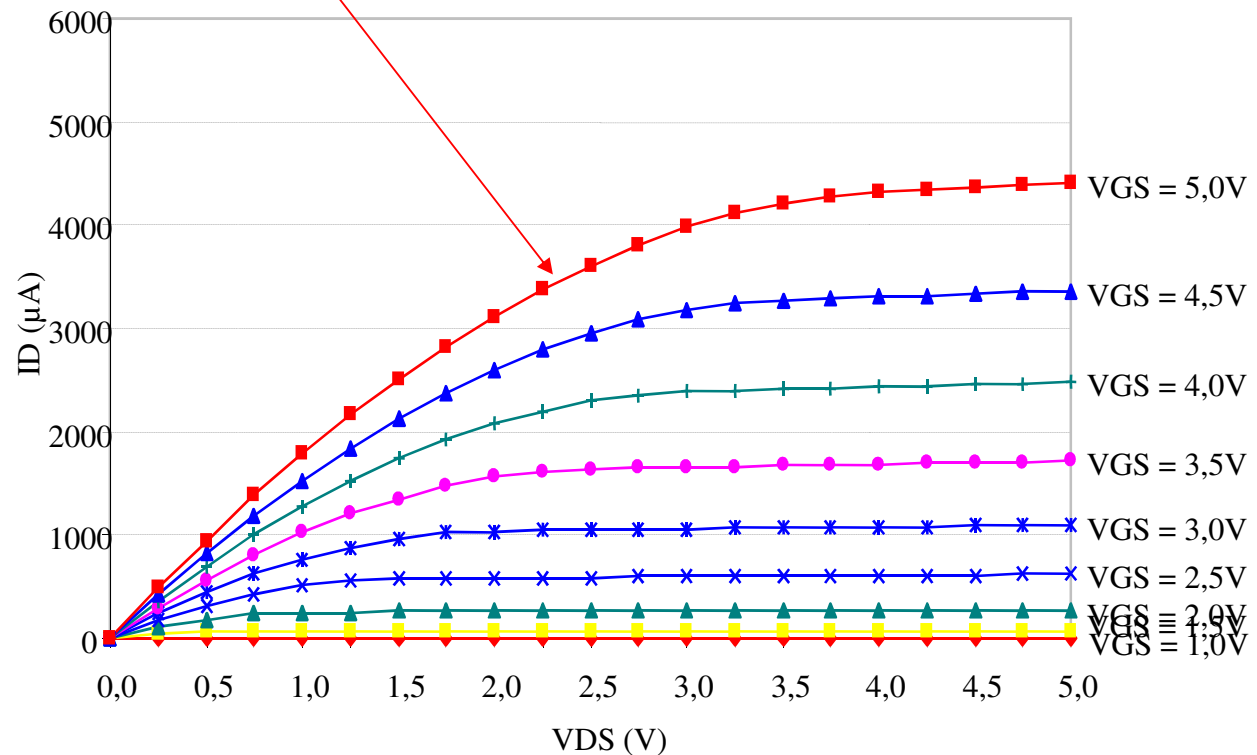Furthermore the current is high
or W/L has to be extremely low.



Reference current source using supply voltage for gate-source biasing

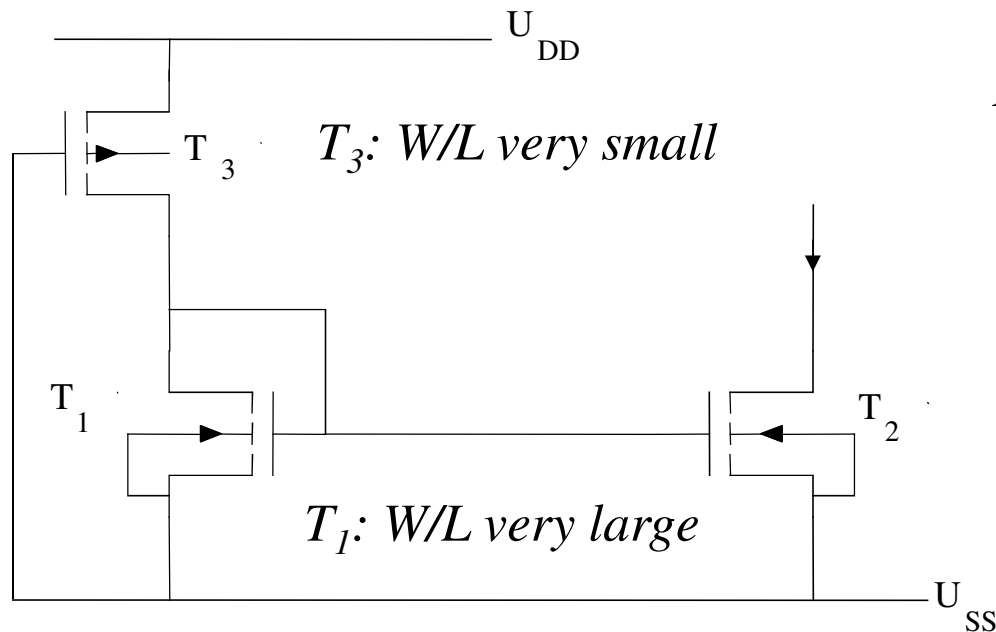Solution: the drain-potential is kept nearly constant and
is mirrored with a MOS-diode




$$I_{ref} = \frac{\beta_{0P}}{2} \cdot \frac{W}{L} \Big|_3 \cdot (U_{DD} - U_{T3})^2$$

*Layout for Current Mirror, e.g. $W_2 = 3*W_1$*


V_T depends also on (short) channel length and (narrow) channel width.

Aim of a current mirror: constant transmission ratio.

Solution: utilization of identical cells

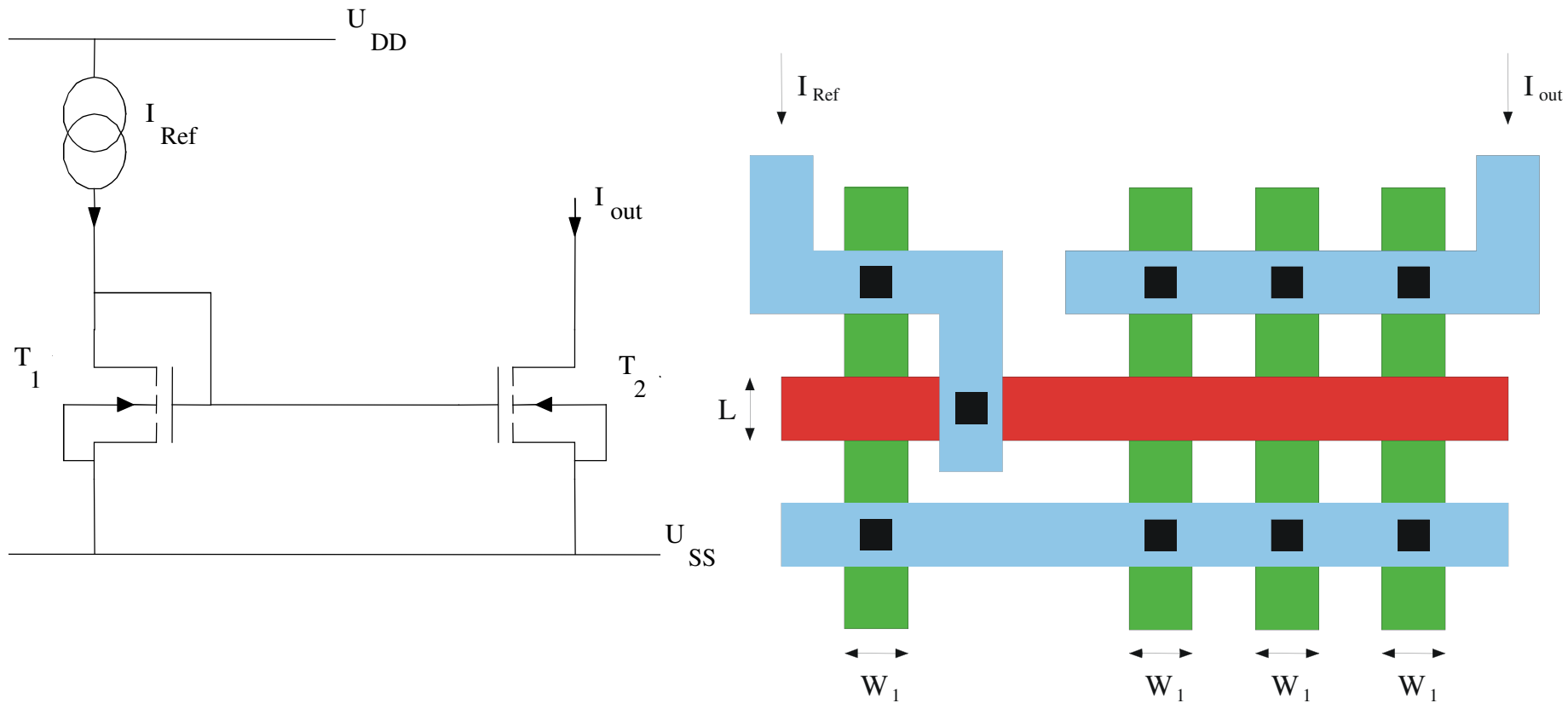

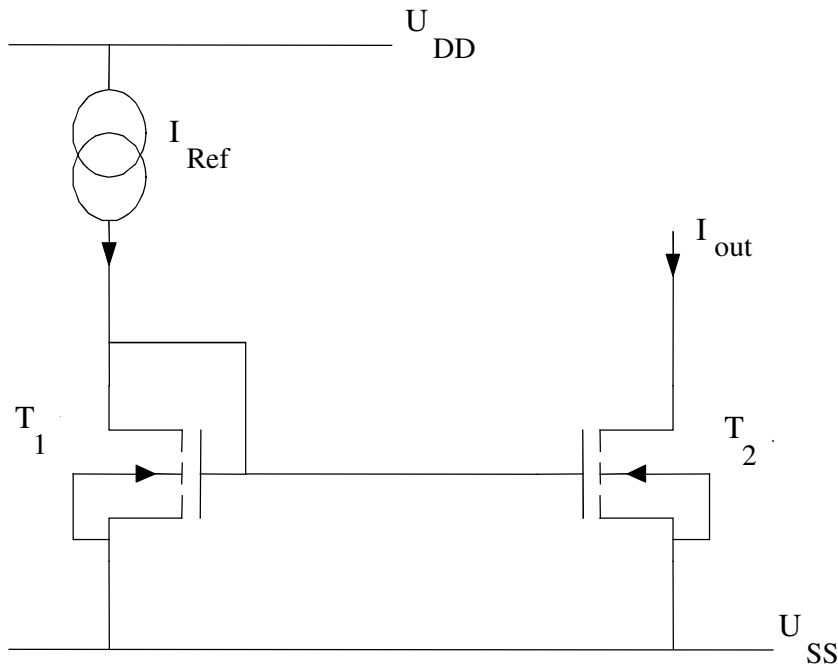Consideration of channel length modulation



$$I_{Out} = \frac{\beta_0}{2} \cdot \frac{W}{L} \Big|_2 \cdot (U_{GS2} - U_{T2})^2 \cdot (1 + \lambda_2 \cdot U_{DS2})$$

$$I_{Ref} = \frac{\beta_0}{2} \cdot \frac{W}{L} \Big|_1 \cdot (U_{GS1} - U_{T1})^2 \cdot (1 + \lambda_1 \cdot U_{DS1})$$

$$\frac{I_{Out}}{I_{Ref}} = \frac{\frac{W}{L} \Big|_2 \cdot (1 + \lambda \cdot U_{DS2})}{\frac{W}{L} \Big|_1 \cdot (1 + \lambda \cdot U_{DS1})}$$

For $L_1 = L_2$ and $U_{DS1} = U_{DS2}$

$$\frac{I_{Out}}{I_{Ref}} = \frac{W_2}{W_1}$$

Deviation for the case that $U_{DS1} \neq U_{DS2}$


So far:
$$\frac{I_{Out}}{I_{Ref}} = \frac{\left. \frac{W}{L} \right|_2 \cdot (1 + \lambda \cdot U_{DS2})}{\left. \frac{W}{L} \right|_1 \cdot (1 + \lambda \cdot U_{DS1})} = \frac{W_2}{W_1} \quad \text{if} \quad L_1 = L_2 \quad \text{and} \quad U_{DS1} = U_{DS2}$$

Conisderation of $U_{DS1} \neq U_{DS2}$


Case $\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2$

$$\begin{aligned} \frac{I_{Out}}{I_{Ref}} &= \frac{(1 + \lambda \cdot U_{DS2})}{(1 + \lambda \cdot U_{DS1})} \bigg|_{U_{DS2} = U_{DS1} + \Delta U_{DS}} = \frac{1 + \lambda \cdot U_{DS1} + \lambda \cdot \Delta U_{DS}}{1 + \lambda \cdot U_{DS1}} \\ &= 1 + \frac{\lambda \cdot \Delta U_{DS}}{1 + \lambda \cdot U_{DS1}} \quad \Rightarrow \quad L \gg \end{aligned}$$

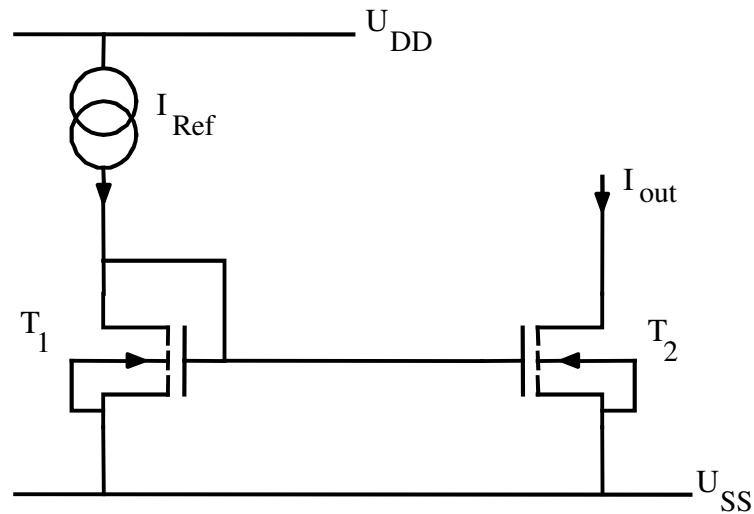Small signal consideration of current mirror




$$r_{out} = ?$$

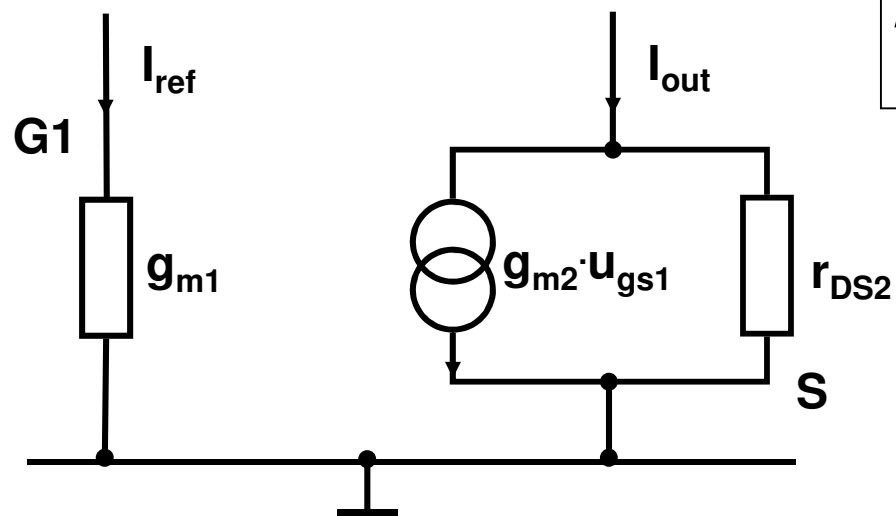

$$r_{out} \approx r_{DS2} = \frac{1}{\lambda \cdot I_{D2}}$$

Cascode-current source

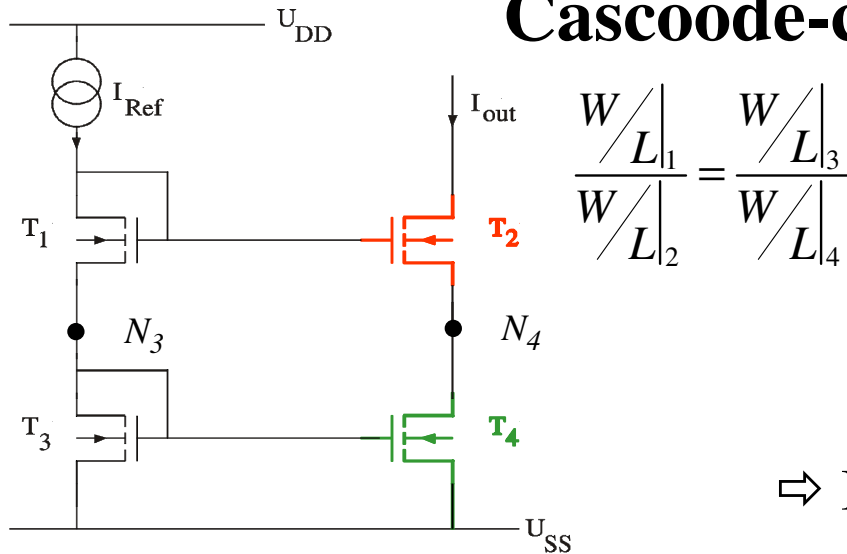


$$r_{out} = ? = \frac{u_{out}}{i_{out}} \Big|_{u_{in}=0} = \frac{u_{test}}{i_{test}} \Big|_{u_{in}=0}$$

$$u_{Test} = (i_{Test} - g_{m2} \cdot u_{GS2}) r_{DS2} + i_{Test} \cdot r_{DS4}$$

$$u_{GS2} + i_{Test} \cdot r_{DS4} = 0$$


$$r_{out} = g_{m2} \cdot r_{DS4} \cdot r_{DS2} + r_{DS2} + r_{DS4}$$
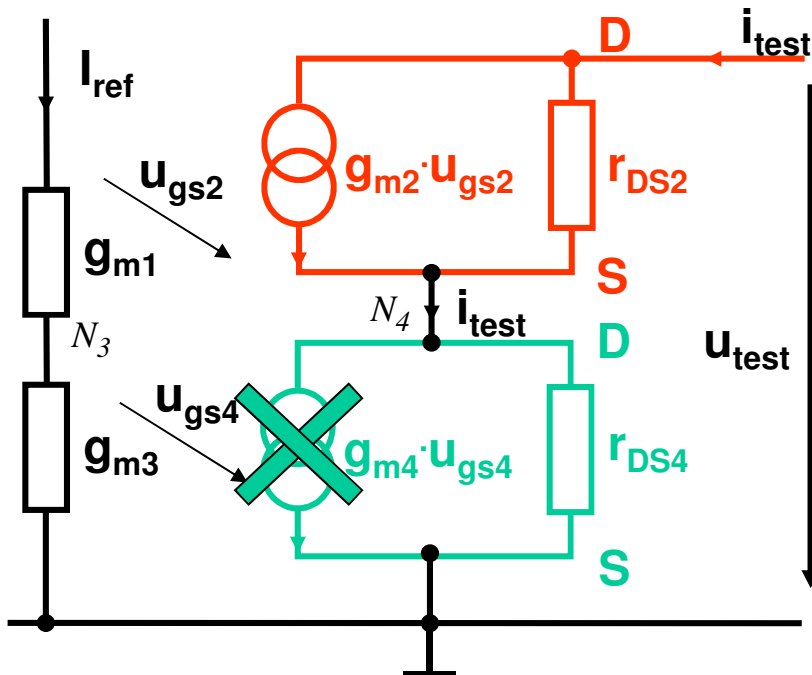
$$= \underbrace{g_{m2} \cdot r_{DS2}}_{\gg 1} \cdot r_{DS4}$$



Operation range of current sources

a) Simple current source

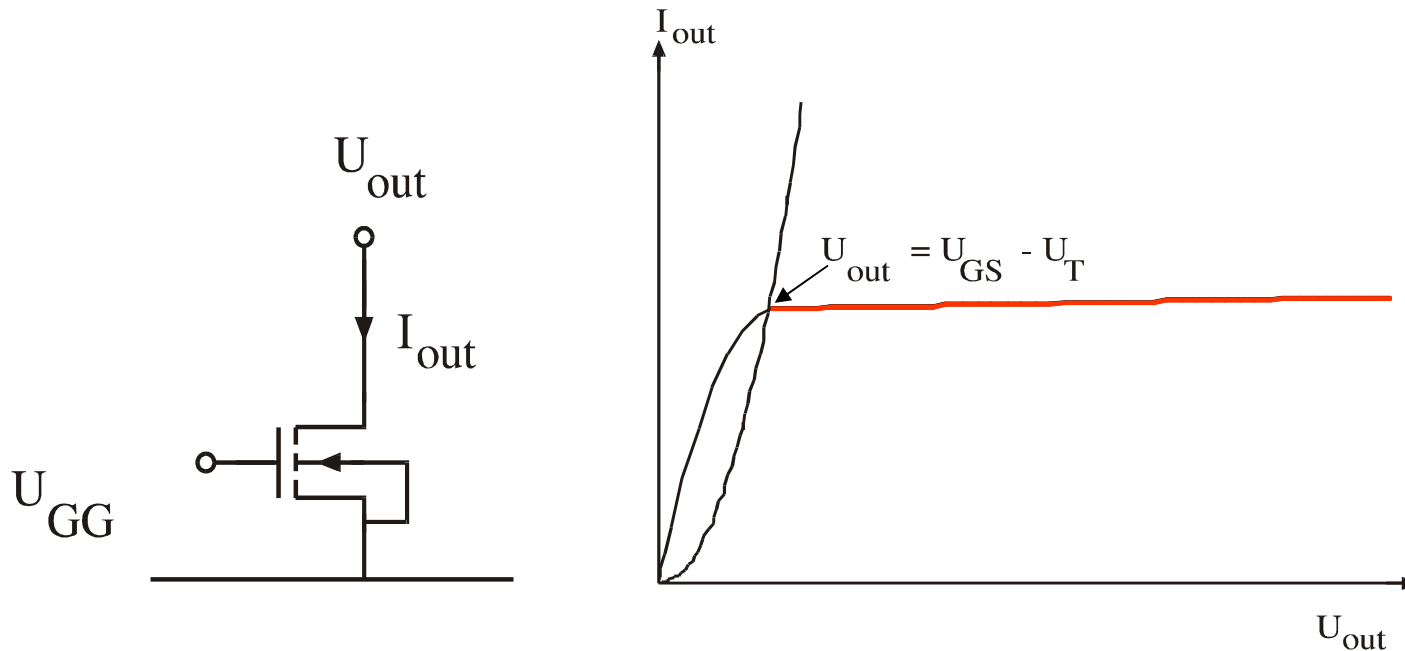


$$I_D = \frac{\beta}{2} \cdot (U_{GS} - U_T)^2 \quad U_{DS} > U_{Dsat} \approx U_{GS} - U_T = U_{GSeff}$$

$$U_{GSeff} = \sqrt{\frac{2 \cdot I_D}{\beta}} = \sqrt{\frac{2 \cdot I_D}{\beta_0 \cdot \frac{W}{L}}}$$

$$\frac{W}{L} \uparrow \Rightarrow U_{GSeff} \downarrow \Rightarrow$$

Large operation range

b) Cascode-current mirror/source

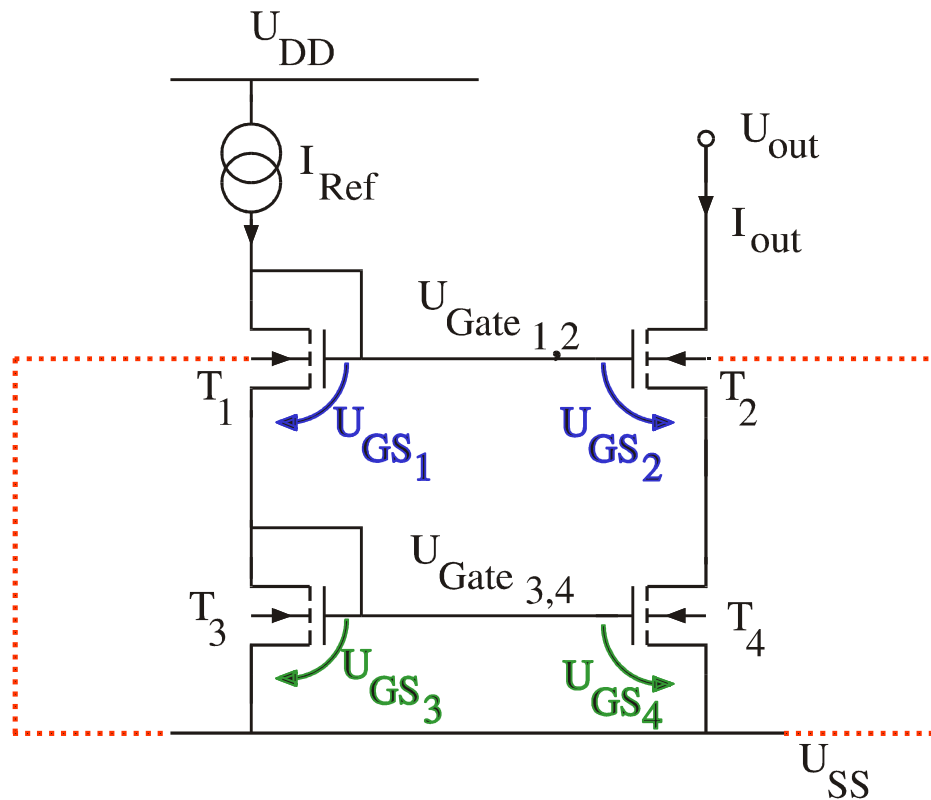

Due to $\frac{W/L_1}{W/L_2} = \frac{W/L_3}{W/L_4}$ and $U_{GS4} = U_{GS3}$

$$\Rightarrow U_{GS2} \approx U_{GS1}$$

Requirement: $U_{DS2} > U_{GS2} - U_{T2}$

$$\Leftrightarrow U_{D2} > U_{G2} - U_{T2}$$

Gate of T₂ is $U_{GS3} + U_{GS1}$

$$U_{G2} = U_{GS3} + U_{GS1}$$

$$U_{DS1} = U_{GS1} \quad U_{DS3} = U_{GS3}$$

$$\Rightarrow U_{DS1,3} > U_{GS1,3} - U_{T1,3}$$


$$U_{GS3} = U_{GS3eff} + U_{T3}$$

$$U_{GS1} = U_{GS1eff} + U_{T1}$$

$$U_{D2} > U_{GS3eff} + U_{T3} + U_{GS1eff} + \cancel{U_{T1}} - \cancel{U_{T2}}$$


$$U_{D2} > U_{GS3eff} + U_{T3} + U_{GS1eff}$$

Characteristics of current curves

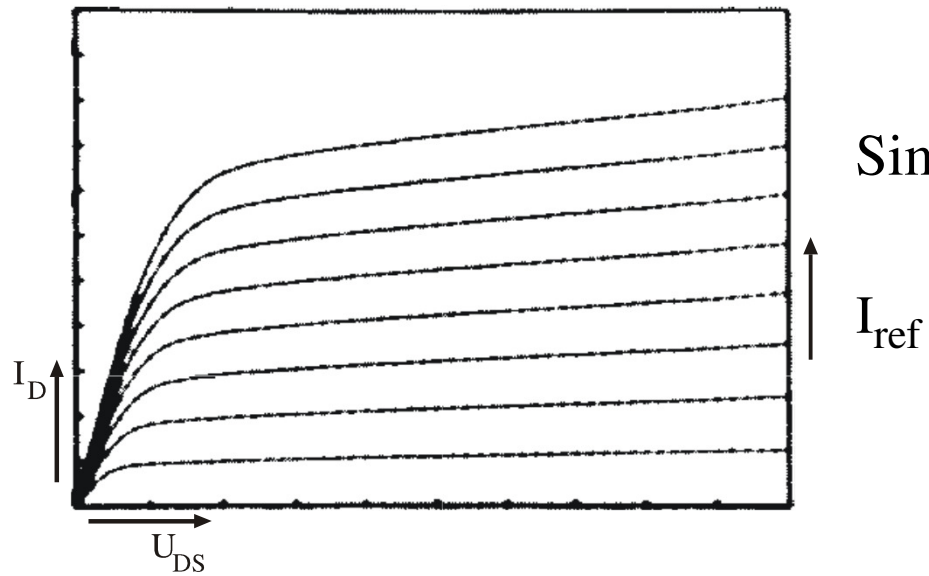

Simple current source

Kaskode current source

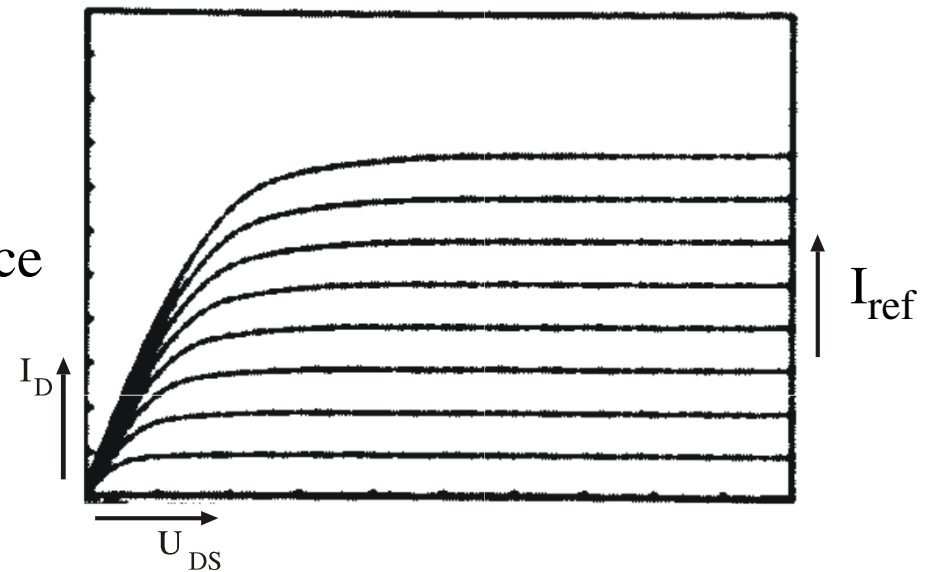


Cascode has a higher output resistance,
but a higher cutoff voltage.

Chapter 4

Basis of analog MOS circuit

- Inverter circuit
- Differential amplifier
- Current source / Current mirror
- Complete Circuit of an Amplifier

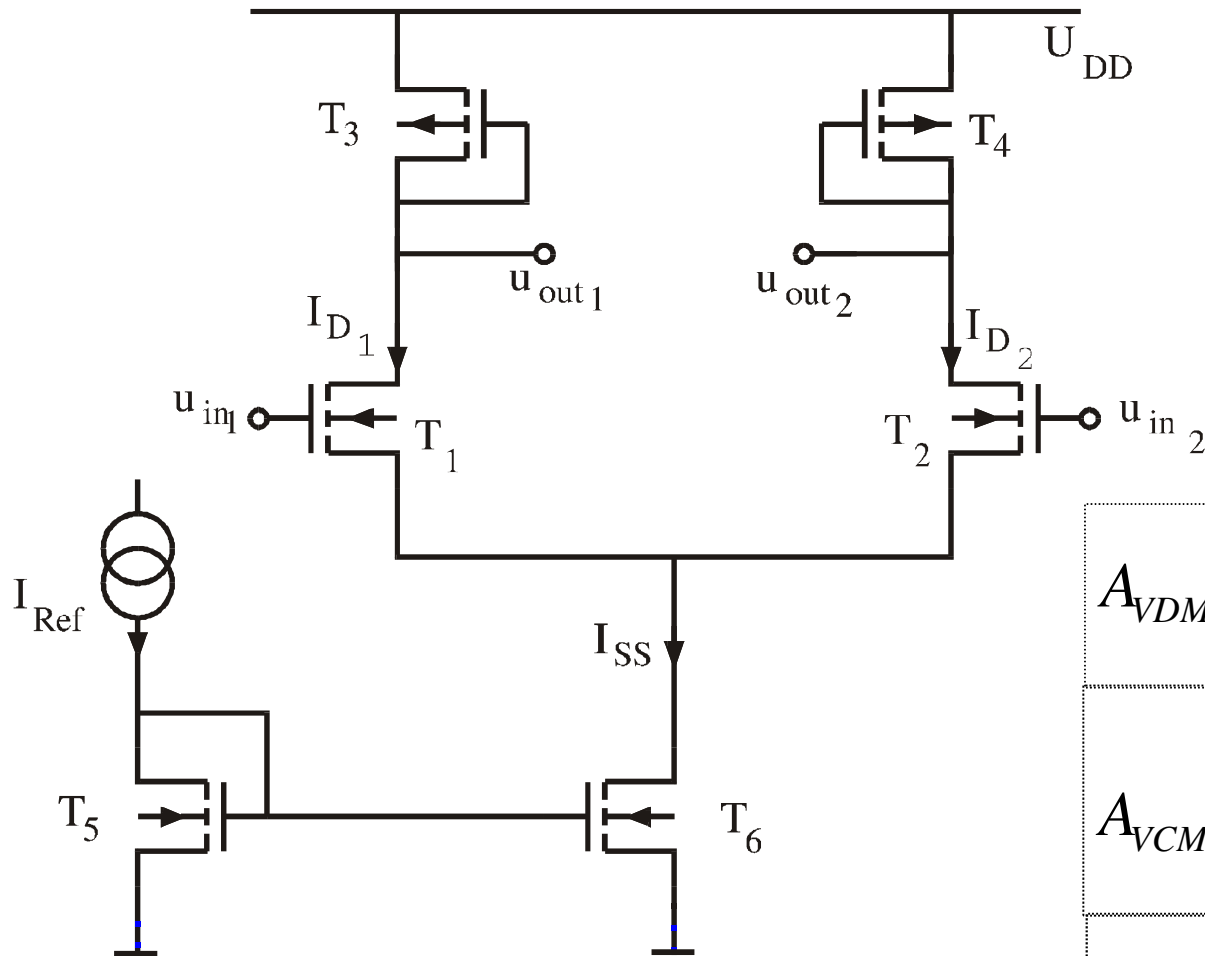Difference amplifier stage with diode load




$$A_{VDM} = -g_{m1} \cdot R = -\frac{g_{m1}}{g_{m3}}$$

$$A_{VCM} = -\frac{R}{2 \cdot R_{SS}} = -\frac{1/g_{m3}}{2 \cdot r_{DS6}}$$

$$CMRR = \frac{A_{VDM}}{A_{VCM}} = 2 \cdot r_{DS6} \cdot g_{m1}$$

Set-up of an amplifier stage

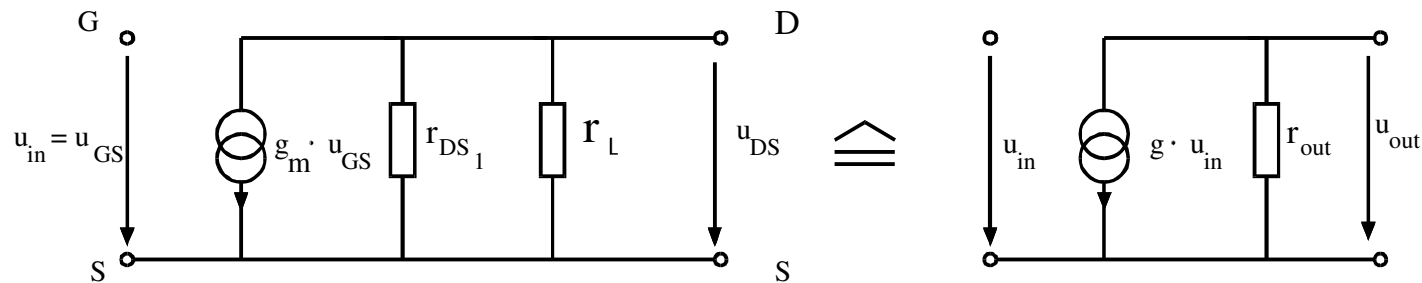


Inverter with resistive load r_L
or (active) transistor load

$$(r_{out} = r_{DS1} \parallel r_L)$$


$$A_V = -g_m \cdot r_{out}$$

Load dependance of amplifier

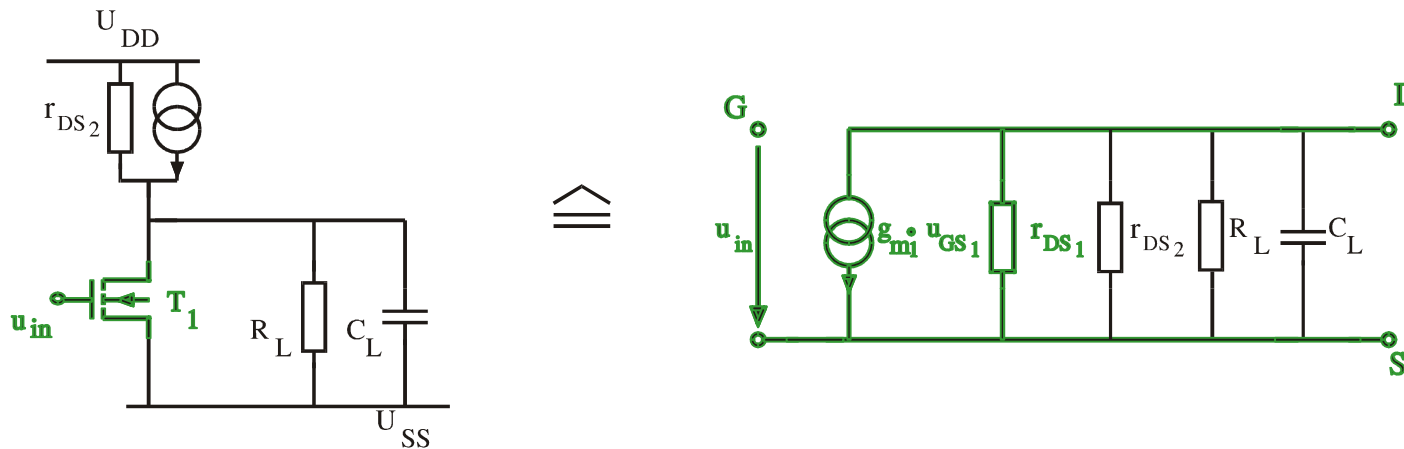


$$A_V = -g_{m1} \cdot (r_{DS1} \parallel r_{DS2} \parallel R_L) \approx -g_{m1} \cdot R_L$$

Corrective by Buffer

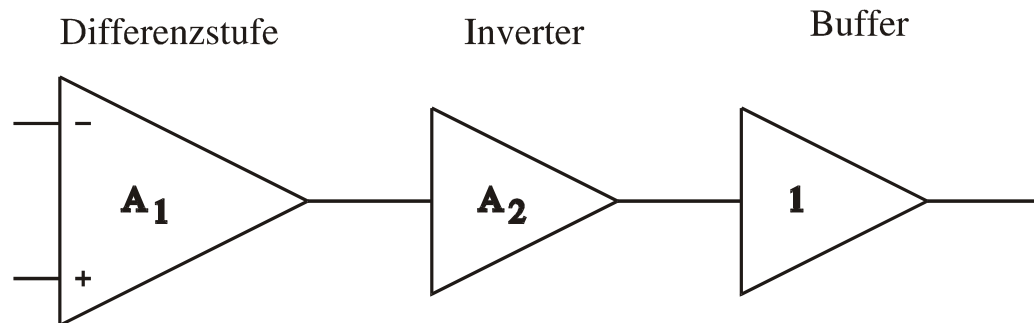

$$A_V = A_{V1} \cdot A_{V2} \cdot 1$$

Complete setup of an amplifier

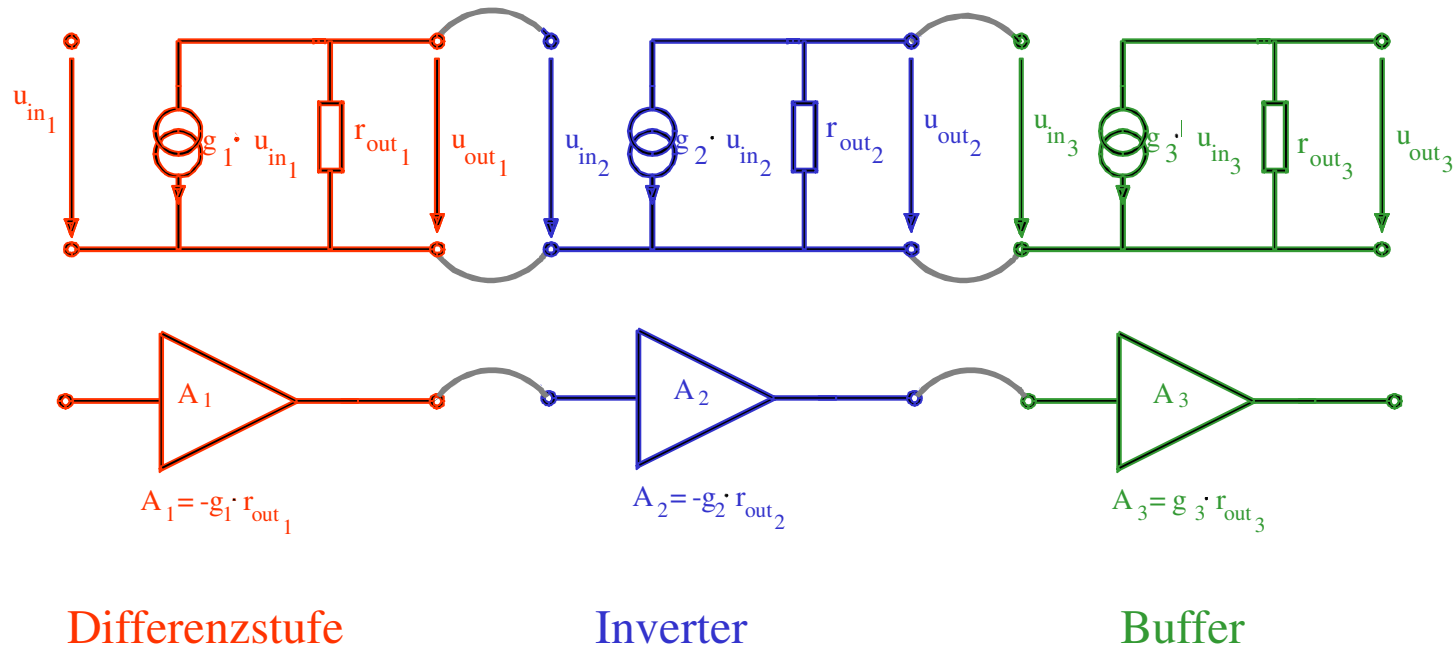

If $r_{in2} \gg r_{out1} \Rightarrow$ second stage will not alter the gain of the first stage


If $r_{in3} \gg r_{out2} \Rightarrow$ third stage will not alter the gain of the second stage

$$A_V = A_{V1} \cdot A_{V2} \cdot A_{V3}$$

$$= g_1 \cdot r_{out1} \cdot g_2 \cdot r_{out2} \cdot g_3 \cdot r_{out3}$$

Source follower as Buffer

A Common Drain Circuit is used

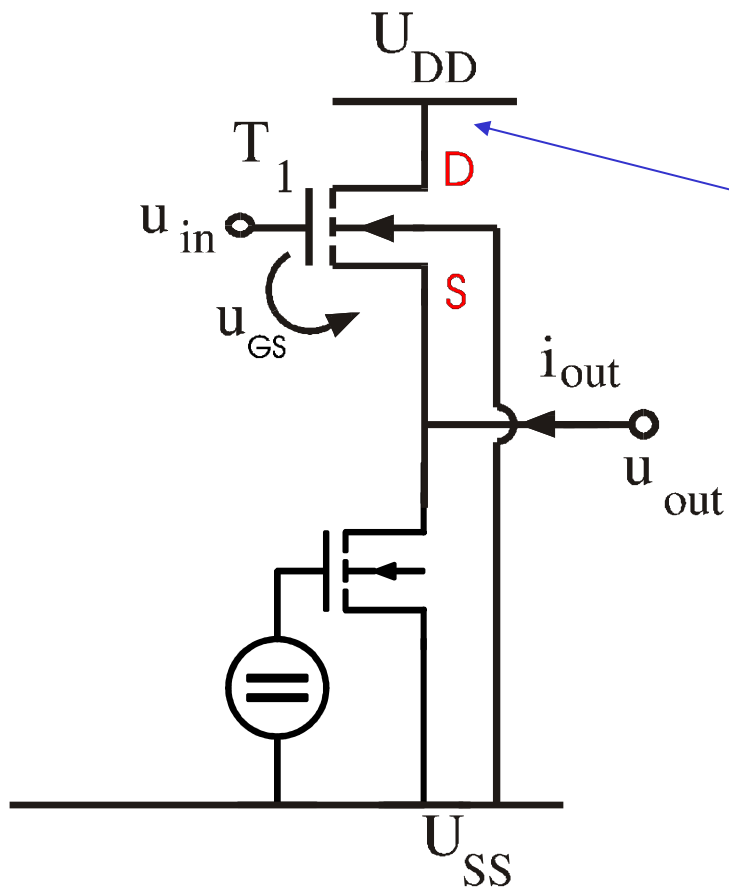

Constant Drain-Potential

$$I_D = \frac{\beta}{2} \cdot (U_{GS} - U_T)^2$$

$$I_D = \text{const.} \Rightarrow U_{GS\text{eff}} = \text{const.}$$

$$\Rightarrow A = 1 \text{ ?!}$$

Without Bulk bias ($V_{bs} = 0$)

$$A \approx 1$$



With Bulk bias ($V_{bs} > 0$)

$$A < 1$$

With load

$$A < 1$$

Multi-Stage amplifier

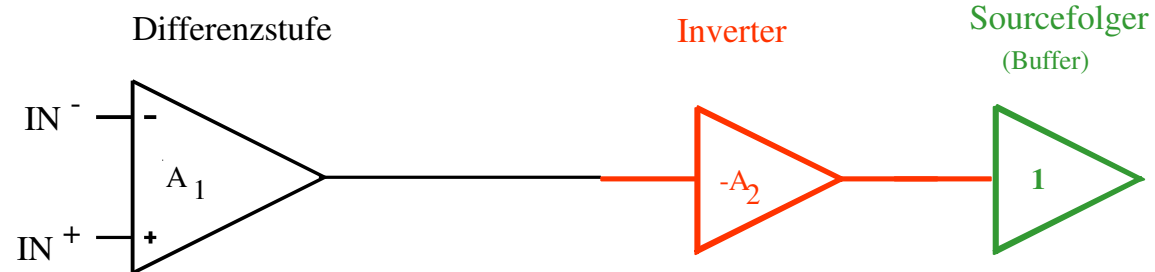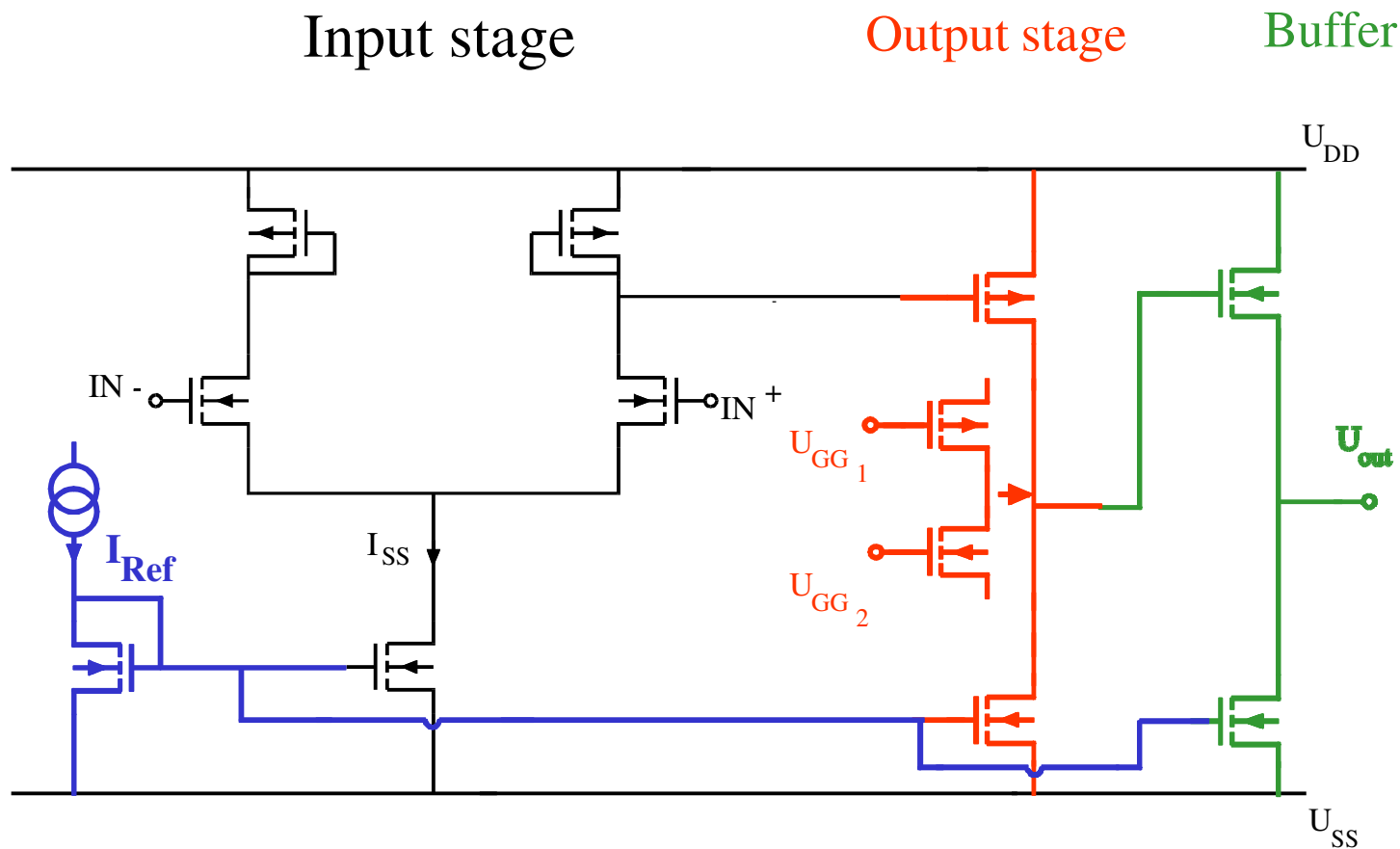

Most important parameters of a current source:

Output resistance r_{out} ,

Cutoff voltage,

Absolute value (accuracy) I_0

Task:

How to generate an exact reference current ?

Exact reference voltage in IC: Bandgap circuit $V_{ref} = 1,2 \text{ V}$

$I_{ref} = V_{ref} / R$, but no exact integrated resistance available

Solution: Usage of an external resistance (exact, $TC=0$)

Circuit to generate an exact reference current

