

Gates in CMOS-Technology

6. Standard/complex CMOS static logics gates

7. Special gates and the applications

7.1 Transmission gates

7.2 Clocked CMOS (Tri-state CMOS gates)

7.3 Bus-driver

7.4 Multiplexer

8. CMOS-circuit techniques (logic gates)

8.1 Pseudo-NMOS

8.2 Cascode-logics

9. Dynamic logics (Precharge-Evaluate)

10. Summary:

CMOS-circuit types for combinatorial circuits

10.1 Advantages and disadvantages of static logics

10.2 Advantages and disadvantages of dynamic logics

Dynamic Logics


Up to now: Static Logics

⇒ Logic level at the output is changing with changing inputs

⇒ Pseudo NMOS ideal for

chip size, speed &
dynamic power dissipation

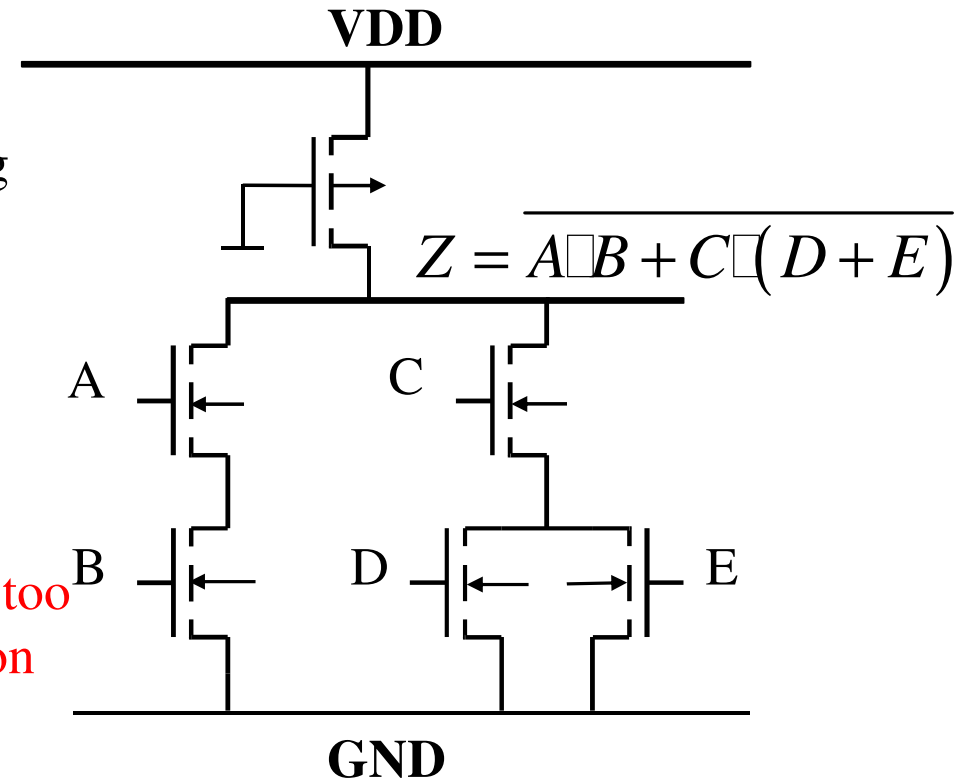but due to switched on
p-channel transistor there is too
much static power dissipation
at low-output




Dynamic Logics

⇒ Switch the p-channel „smartly“
(within one clock) on and off to save
the static power dissipation

≠ Register, Flip-Flop
but combinatorial functions

Precharge / Evaluate (P/E) Logics

 

Dynamic Logics Circuit

Clock : ϕ

Precharge

Evaluate

$Z=1$
charged

So that no
current flows
 \Rightarrow

Inputs
all =0!

\Rightarrow But
Outputs
all =1!

$Z=f(A,B,...)$
 \Rightarrow Inputs
can be active


if path to
GND exists:
 $\Rightarrow Z=0$

if not:
 $\Rightarrow Z=1$

capacitively
stored
(charged)

➤ Leakage
current

Improved Dynamic Logic Circuit

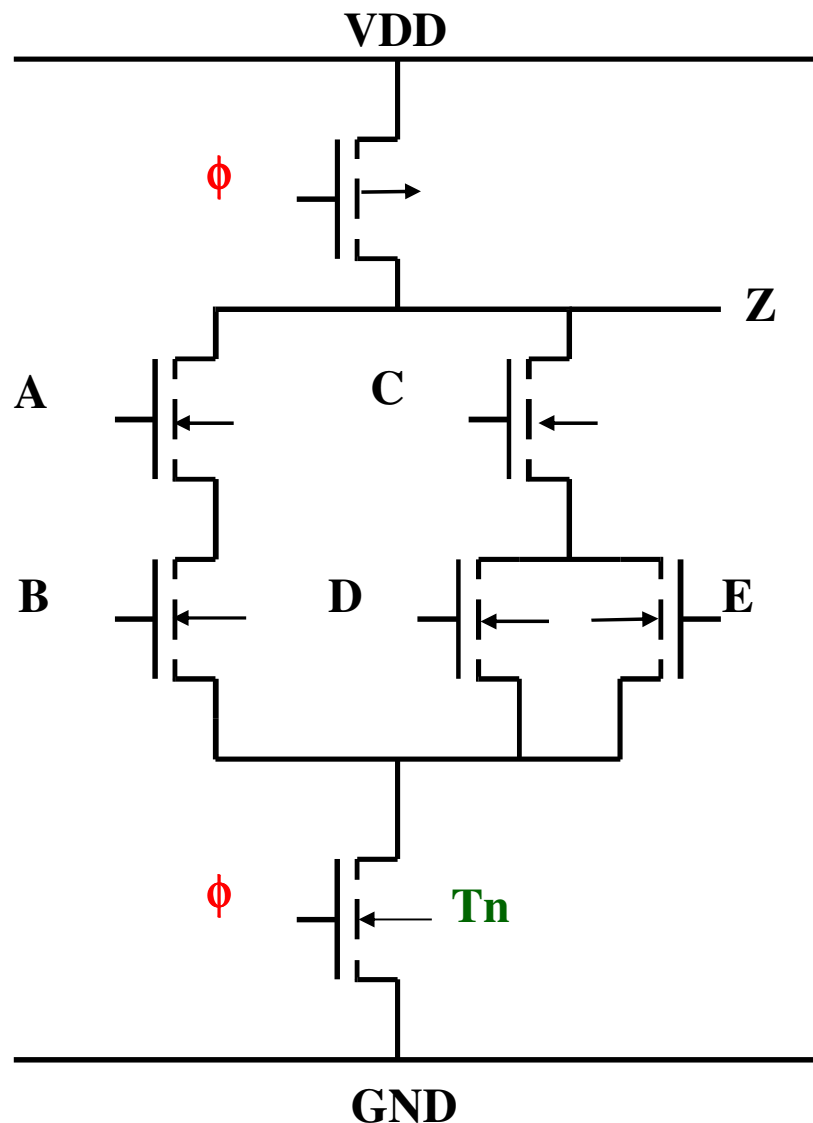

Clock: ϕ

Precharge

Evaluate

V_{DD} -Path

GND-Path

$Z=1$
charged

$Z=f(A,B,...)$
evaluated

T_n blocks:

T_n conducts:

Current
does not
flow \Rightarrow

if path to
GND exists

Inputs are
arbitrary!

$\Rightarrow Z=0$

if not:

$\Rightarrow Z=1$

capacitively
stored

(charged)

➤ Leakage
current

Advantages of Dynamic Circuit Technology


1. Low area requirements
(1 Transistor per input)
2. Low capacitive load
(1 Transistor per input)
($n+2$ instead $2n$ Transistors)
3. No static power loss

Disadvantages of Dynamic Circuit Technology


1. Clock for each gate
2. High-level only stored capacitively

Overview of Combinatorial Logics


Standard Logic

 


Pseudo NMOS

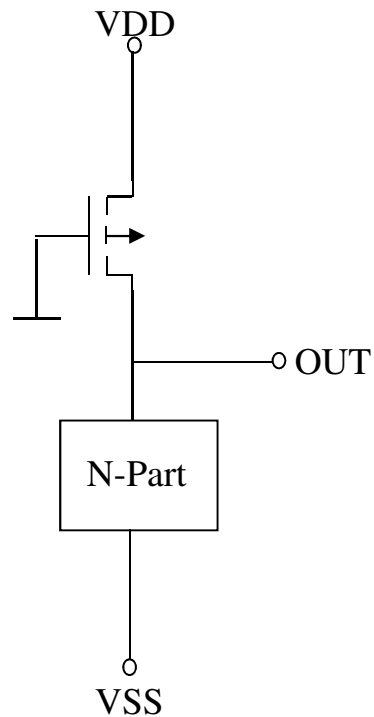



Dynamic
Logic
precharge/evaluate

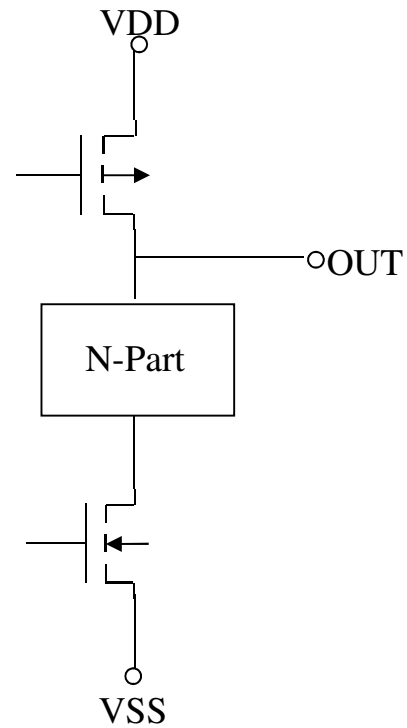

Clocked CMOS
Logic

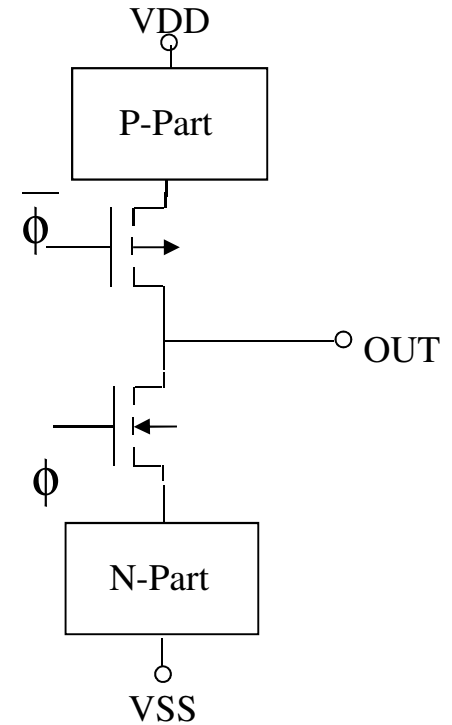

Comparison static/dynamic logic

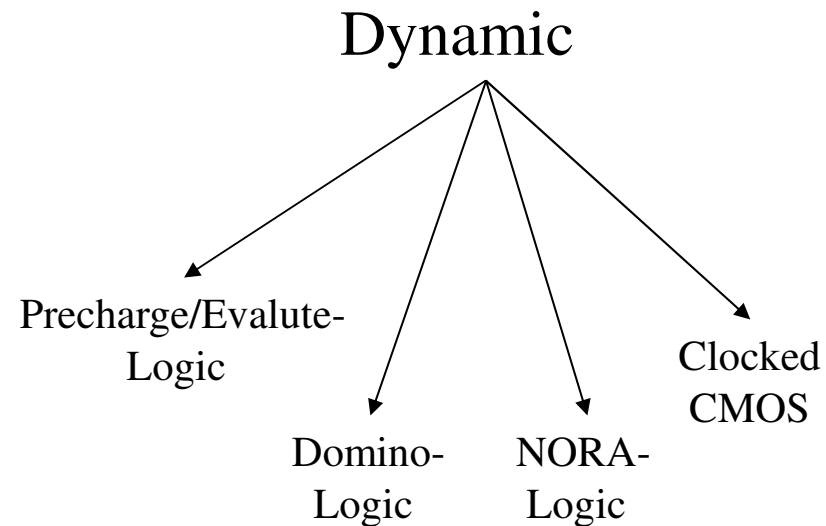 

Static

- **2n Transistors**
- **Large area**
- **High load capacity**
 - **High power loss**
 - **Long delay**
- + **good noise margin**
- + **power loss depends on frequency up to and including 0 Hz**

Dynamic

- **Layout and dimensioning is more difficult**
- **Clock supply is needed**
- **A “1” is only stored capacitively, clock must always be refreshed**
- + **low load capacity**
 - **small delay**
 - **low power loss**

11. Sequential Circuits

1. Realization of Registers (Latches, Flip-Flops)

- 1. Dynamic Registers**
- 2. Static Registers**

2. Pipeline

3. Clock Distribution – Clock Networks

4. Clock Generation

Limits of combinatorial Logics

Up to now we only considered the design of pure combinatorial logics.

The outputs of a gate network are only depending on the inputs applied at this time. Effects in time are only considered with regard to signal propagation from input to output (delay). Previous input assignments have no effect on circuit output (no storage; no memory)



Advantage: Simple structure, easy to understand and to design


Disadvantage: All input information has to be given simultaneously!

Sequential Circuits

A safer and more calculable design of a feedback structure by using of storage elements in the feedback loop as memory


Control of the storage elements by external system clock

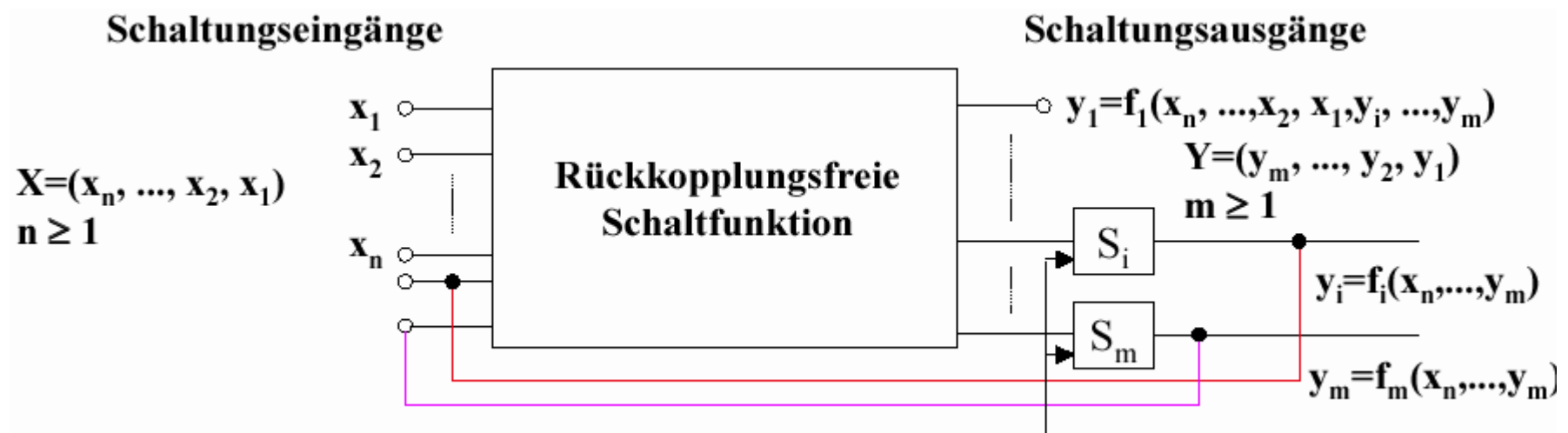Synchronous switching: Synchronous sequential circuit
(temporally decoupled)




Synchronization prevents Race and Oscillations.

8-bit Adder

 


Accumulator / Incrementer

Finite State Machine, FSM

 


Mealy-Machine
 $out=f(in,Q)$



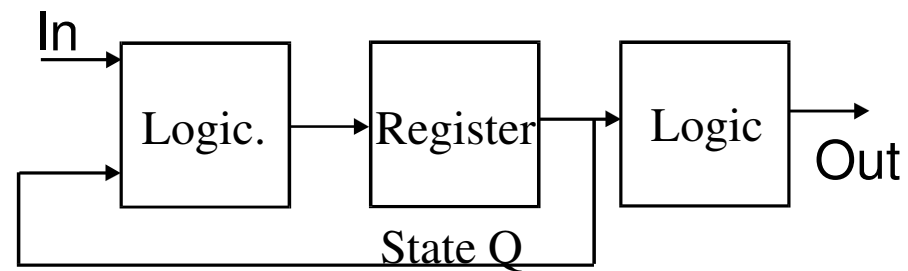


Moore-Machine
 $out=f(Q)$


CMOS Inverter for simple Latch

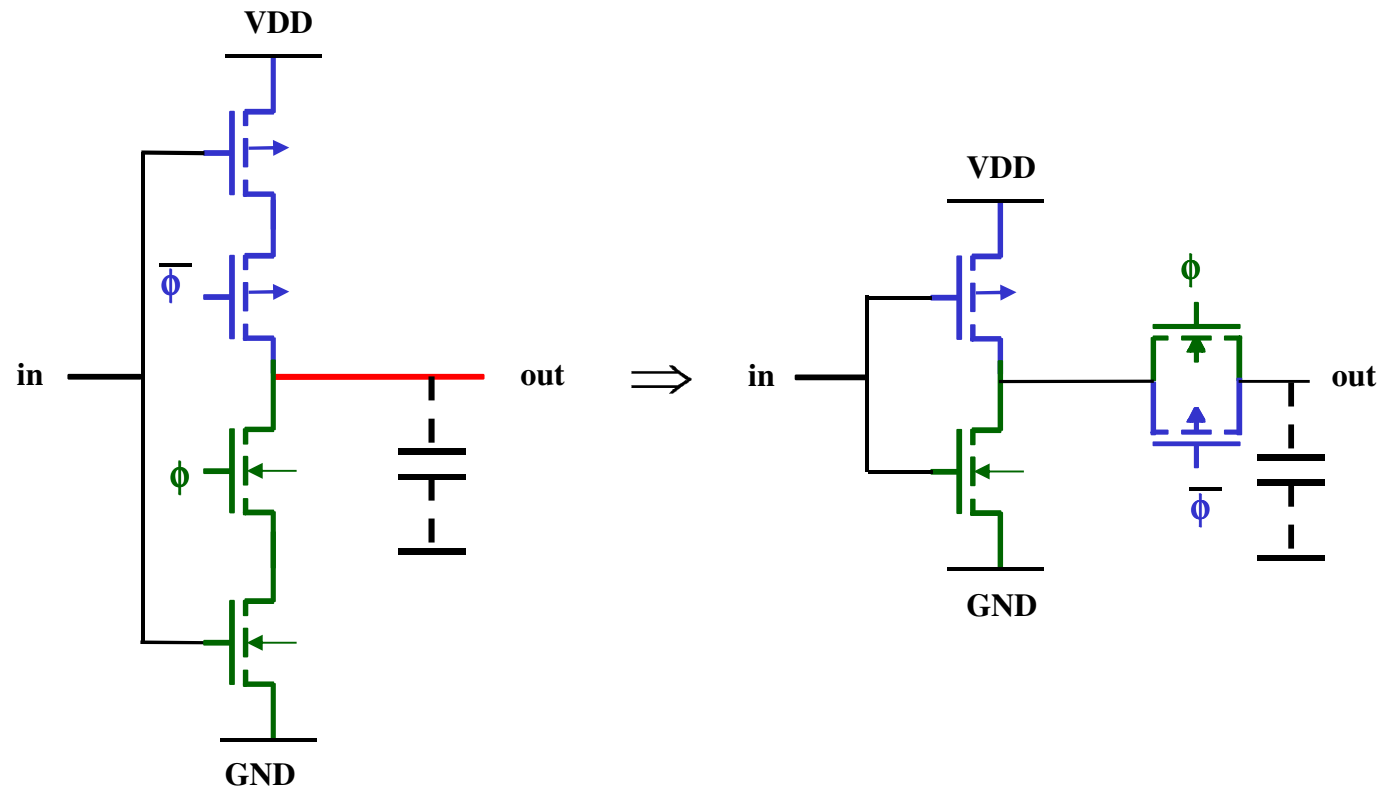


Inverting Latch

   

Function of Latch

 

Dynamic Latch

 


Timing of the Signals


$\phi = 1$: transparent (load), In is mapped directly on Out

$\phi = 0$: hold (storage), last state of Out is frozen


Dynamic Flipflop

 

Flipflop with two Latches

 


Timing of the Signals

 


Two-phase clock


Implementation of dynamic Flipflop

 

Register with two Latches


 


 Register with two-phase clock
and N-Transistor as Switch



Register with one-phase clock
and N- & P-Transistor as Switch


Transmission-Gate dynamic Flipflop

 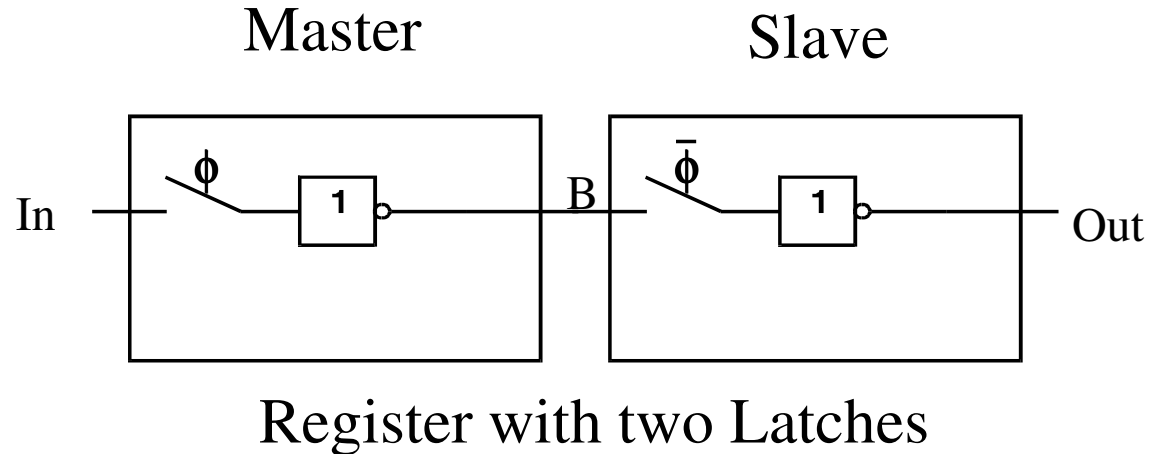

Register with two Latches and
Transmission-Gate as Switch

8 Transistors


Static Latch (with Transmission Gate)

 

Static Latch

$\Phi = 0$


Multiplexer

 


Static Latch

$\Phi = 1$

 Static Master-Slave Flip-Flop (with Transmission Gate)




Static Latch

 

Static Master-Slave Flip-Flop


16 Transistors

RS-Latch

 


Truth table of RS-Latch

R	S	Q	P
0	1	1	0
1	0	0	1
1	1	0	0
0	0	Q(t-1)	P(t-1)

 


same function

 


Storage

D-Latch

 


D	Q	P
1	1	0
0	0	1


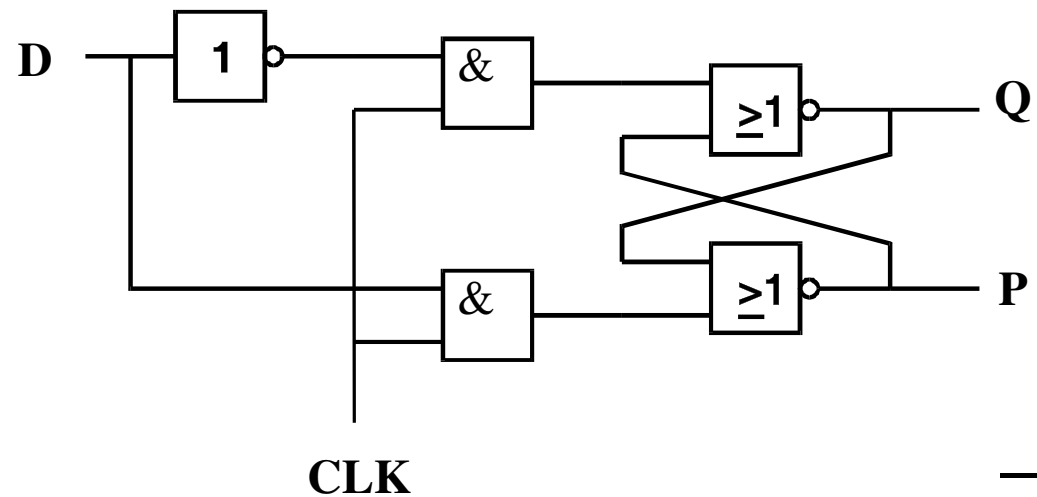


C	D	Q	P
1	1	1	0
1	0	0	1
0	X	Q(t-1)	P(t-1)


Clocked D-Latch

 

D-Flip-Flop

  


Clocked D-Latch

 

Master-Slave-Flip-Flop with two clocked D-Latches


Truth table of D-Flipflop

 

IN	CLK	OUT
X	0	OUT(t-1)
X	1	OUT(t-1)
0	\downarrow	0
1	\downarrow	1




Input data is only passed with (falling) edges.

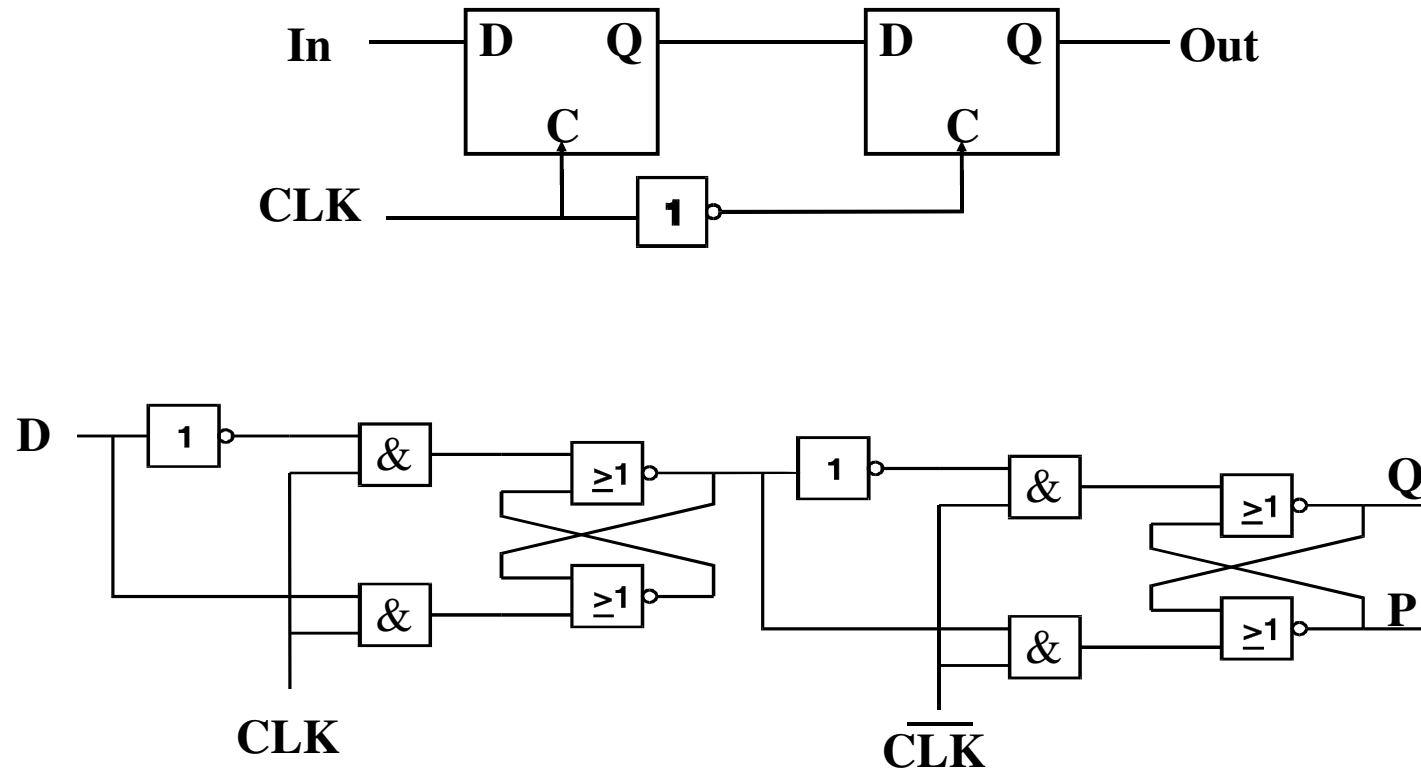Gate-Implementation of Master-Slave-Flip-Flop



Master-Slave-Flip-Flop of two clocked D-Latches

44 Transistors

  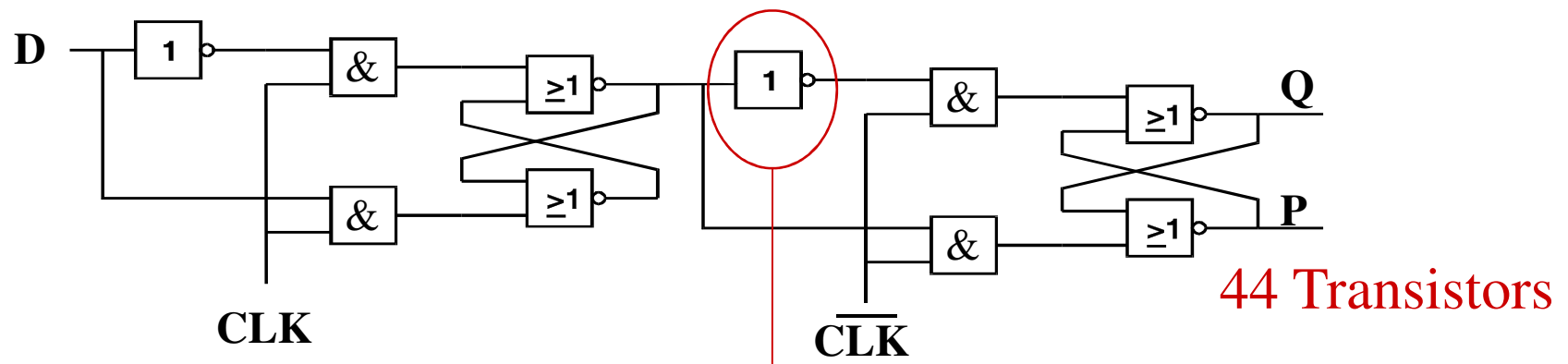

Summary of terms

Flipflop: bistable flipflop, basis of all sequential circuits

Level controlled: **Latch**

Edge controlled (transition of level): Flipflop in a narrow sense

⇒ 1-Bit-memory

Register: an Array of FlipFlops.

A 16- bit Register is also an Array of 16 D-Flip-Flops

with common clock

with common Clear, Enable, etc.

In- and outputs are combined to Busses (Data, Addresses)

11. Sequential Circuits

1. Realization of Registers (Latches, Flip-Flops)

1. Dynamic Registers
2. Static Registers

2. Pipeline



3. Clock Distribution – Clock Networks

4. Clock Generation


Pipeline

- Pipelining = **Consecutive processing** of a task.
Single steps are finished in one clock each
- Registers are needed for several steps/stages with logics inbetween
- The result is only available after a long **Latency** (counted in clocks).

$$\text{Processing : } Out = \log |a + b|$$

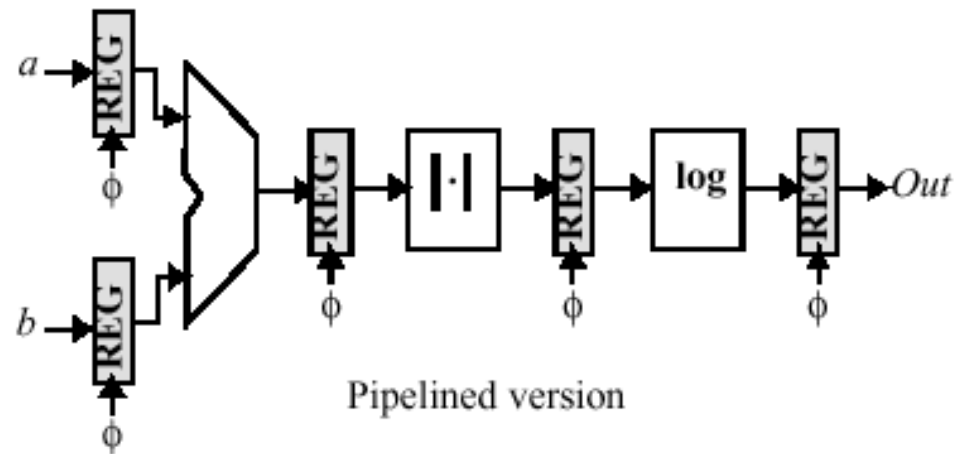 


Pipeline for $Out = \log|a + b|$

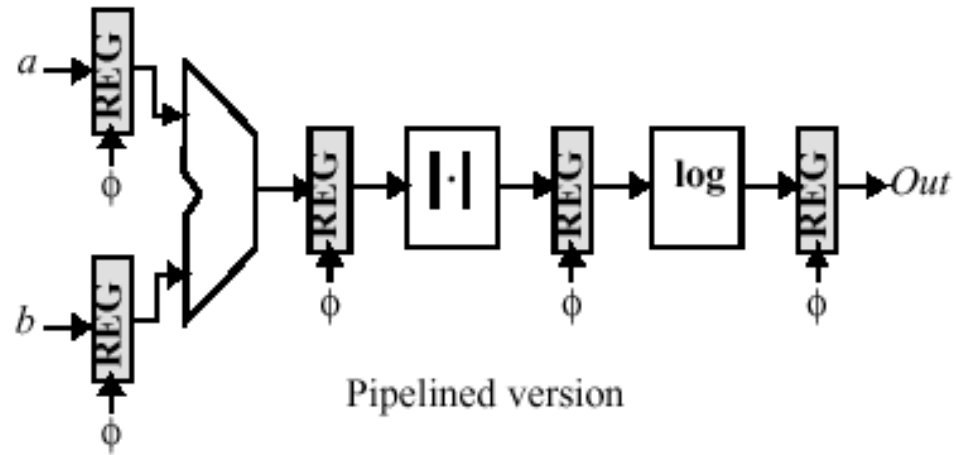

Clock Period	Adder	Absolute Value	Logarithm
1	a1+b1		
2	a2+b2	a1+b1	
3	a3+b3	a2+b2	log(a1+b1)
4	a4+b4	a3+b3	log(a2+b2)
5	a5+b5	a4+b4	log(a3+b3)

Pipeline-Implementation

1) Flipflops, one phase

 

2) Latches, two phases
(not overlapping)

