

Up to Now:

Devices are transistors (diodes), resistances etc.

You can make analog circuits like
inverter, amplifier or current source

And the next?


How to design **digital circuits**
with these devices / transistors?

Chapter 4 Contents

- Introduction of digital circuitry
- Digital MOS-circuits
- CMOS - complementary MOS
- Pseudo-NMOS (p-channel-transistor as load)
- Delays
- Power Consumption


Advantages of digital circuit technology

 - Possibility of simple and error-free processing, so that great complexity can be mastered.
- Tolerant to variation in production




- Digital means **discrete values** (binary) and **discrete time**!
- High resolution is achieved by more bits (parallel) and clocks (sequential).

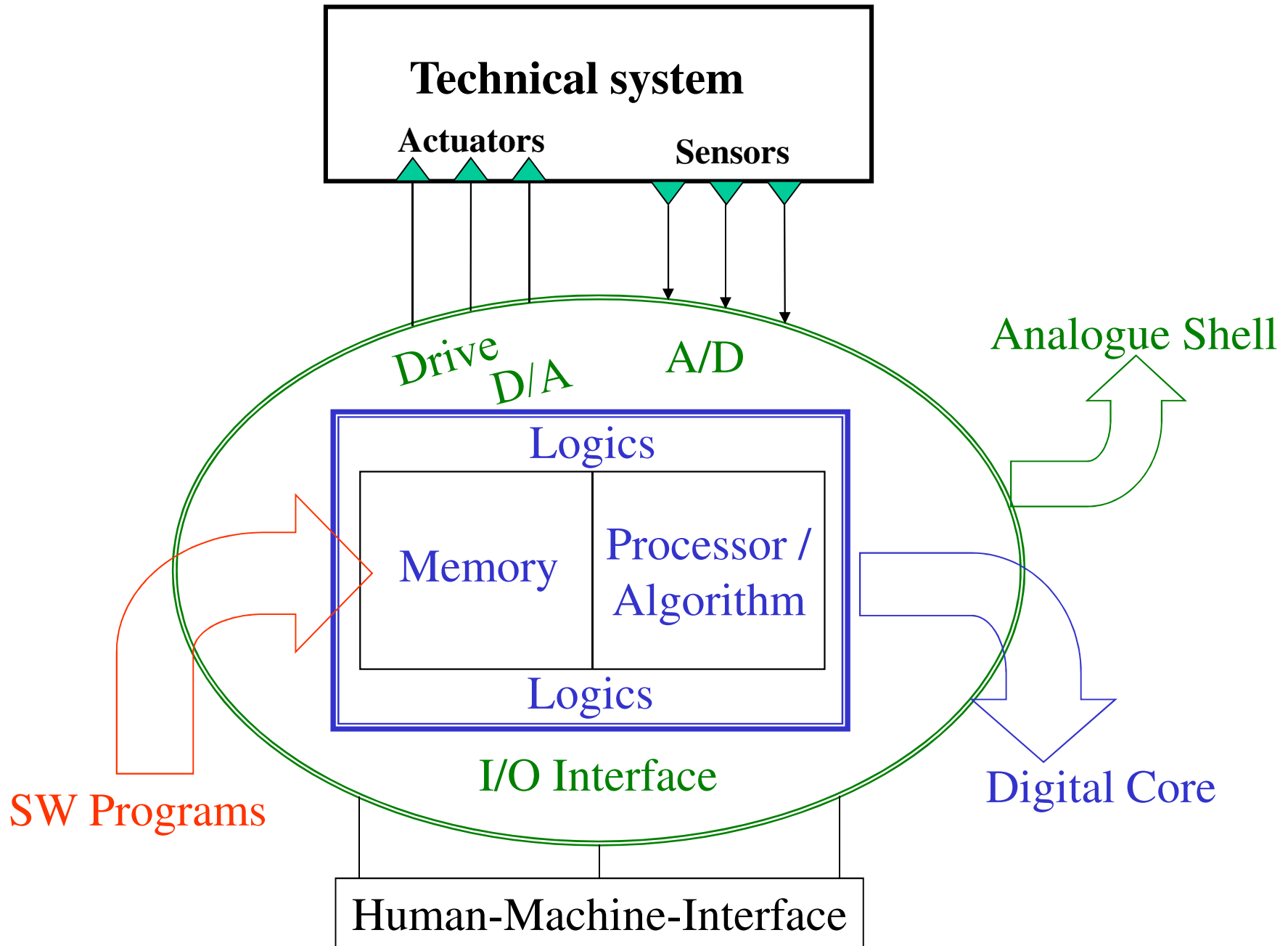
Necessary: clock generator, A/D- and D/A-converter



Yield Dependence on Chip Size

 

 
The yield of digital circuits does not depend on design.
Precondition: process, models and library are alright



Switch Network

Digital circuit (bipolar, MOS)

Transistor as a switch

 

A	State	X		Y
0	Switch on	1	Switch off	0
1	Switch off	0	Switch on	1

BUT


These switches are transistors and have a threshold voltage.

These switches have a on-resistance.


Switch on: $U_{in} > U_T$; Switch off: $U_{in} < U_T$

Switch on: Voltage divider $U_{out} = ?$

Realization of Gates

 


NAND-Gate

 

NOR-Gate

Gate is the lowest abstraction level of digital circuitry.


NMOS-Circuit technology

 

Inverter with resistance

- Depending on load elements different circuit technology
 - Resistance
 - MOS-diode
 - Current source



Inverter transfer characteristics

 


Poor design:

$$V_{out,low} > V_T$$

R: $2k\Omega$ \square $5k\Omega$

  


Noise Margin

 

Characteristic of an inverter

Digital MOS-Circuit technology

 

Inverter with resistance

- Depending on load element different circuit technology
 - resistance
 - MOS-Diode
 - Current source




Disadvantage: with $U_{in} = \text{high}$, there is always a current flowing;
 U_{out} is not ground

Solution: **CMOS**

Chpater 4 Contents

- Introduction Digital circuit technology
- Digital MOS-circuits
- CMOS - complementary MOS
- Pseudo-NMOS (p-channel-transistor as load)
- Delay times
- Power loss


CMOS-Complementary MOS

  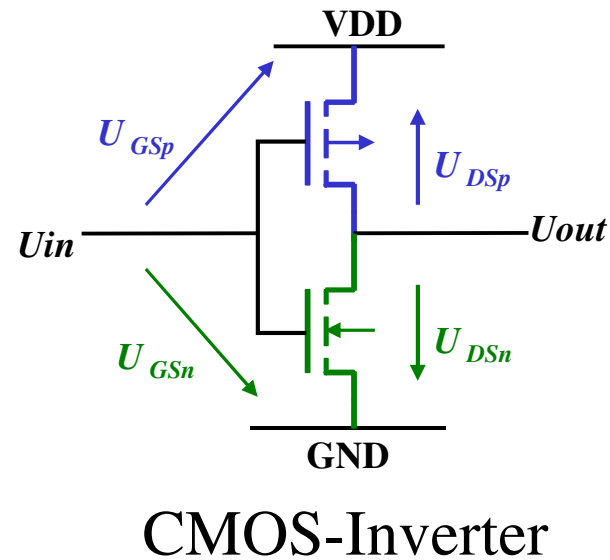

Switch Representation of CMOS-Inverter



PMOS can be regarded as the load of NMOS.
Or vice versa: NMOS is the load of PMOS.
It is active load, as U_{gs} of load is changing.

Realization of a NAND-Gate in CMOS

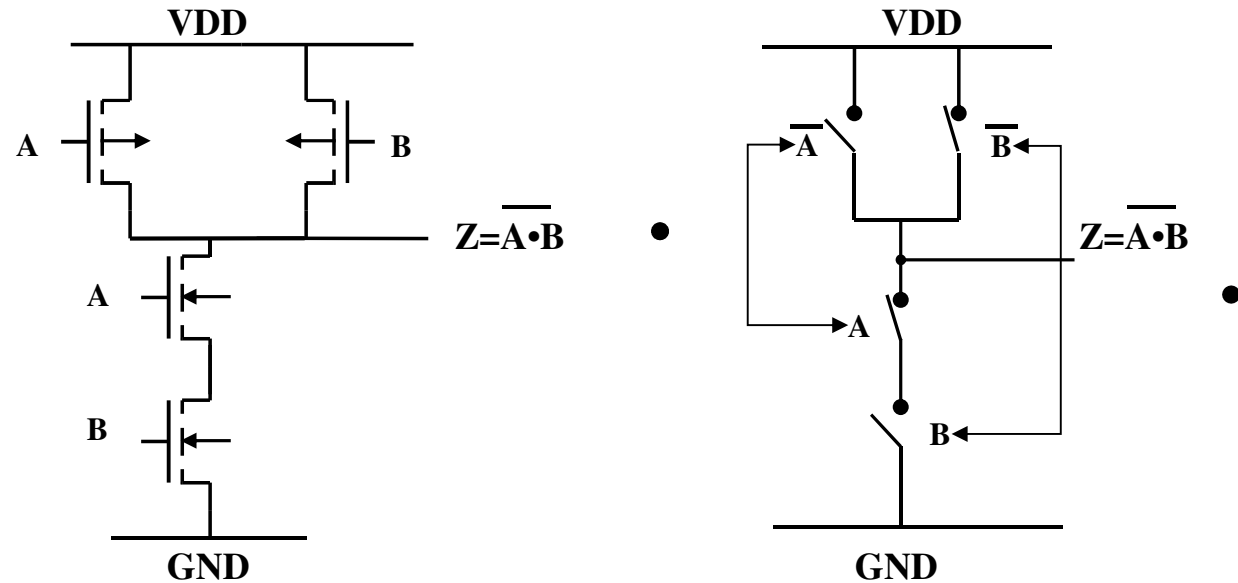


A	B	Z
1	1	0
0	1	1
1	0	1
0	0	1

Realization of a NOR-Gate in CMOS

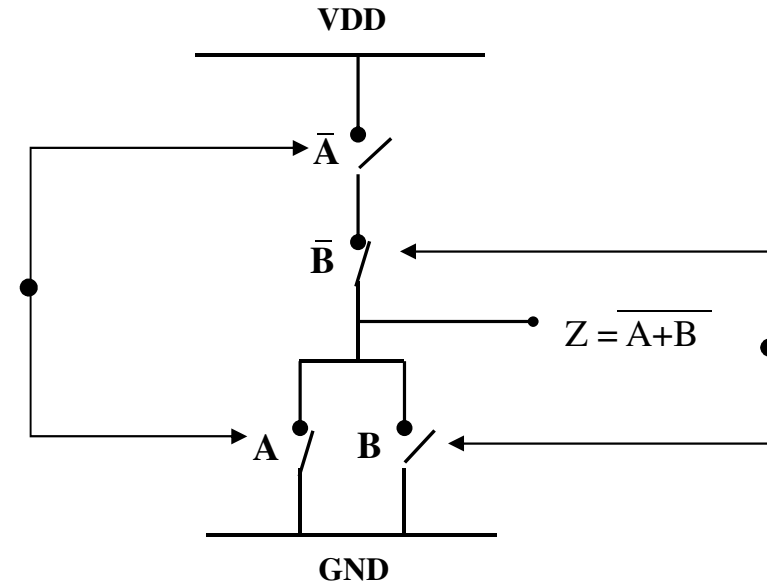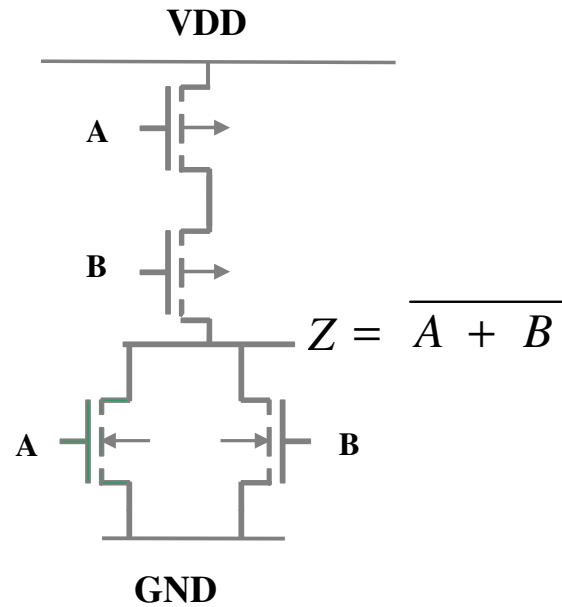

A	B	Z
1	1	0
0	1	0
1	0	0
0	0	1

 Close view of the transfer characteristic of a CMOS-Inverter




$$I_{Dn} = I_{Dp}$$

$$U_{GSn} = U_{in}$$




$$U_{DSn} = U_{out}$$

$$U_{GSp} = |V_{DD} - U_{in}|$$


$$U_{DSp} = |V_{DD} - U_{out}|$$

 

Determining CMOS-Inverter-Characteristic

   


Current of a CMOS-Inverter

 

Transfer characteristic

- There is no static current;
- Output level always „clean“ on high or low
- During the transition there is a short circuit current

 Noise Margin calculation for CMOS-Inverter



Definition:

$$V_M = V_{IN} = V_{OUT}$$

A_V : Gain

$$V_{IN} \leq V_{IL} \Rightarrow V_{OUT} = \text{High}$$

$$V_{IN} \geq V_{IH} \Rightarrow V_{OUT} = \text{Low}$$

V_M Calculation for CMOS-Inverter

$$I_{DN} = \frac{\beta_N}{2} \cdot (V_M - V_{TN})^2$$

$$|I_{DP}| = \frac{\beta_P}{2} \cdot (V_{DD} - V_M - |V_{TP}|)^2$$

$$I_{DN} = |I_{DP}|$$

$$V_M = \frac{V_{TN} + \sqrt{\beta_P / \beta_N} \cdot (V_{DD} - |V_{TP}|)}{1 + \sqrt{\beta_P / \beta_N}}$$



Common designs are symmetric.

$$\Rightarrow \beta_P \approx \beta_N \quad (W_P \approx 3 * W_N)$$

$$V_{TP} = V_{TN}$$

$$V_M = V_{DD} / 2$$

  Calculation of A_V and Noise Margin for CMOS-Inverter




Small Signal-Equivalent circuit diagram

$$A_V = -\frac{g_{mn} + g_{mp}}{g_{DSn} + g_{DSp}}$$

Operation point is V_M / V_M (in, out).

 
A_V is twice as large as that of inverter with current source





$$NM_L = V_{IL} = V_M - \frac{V_{DD} - V_M}{|A_V|}$$

$$NM_H = V_{DD} - V_{IH} = V_{DD} - V_M \left(1 + \frac{1}{|A_V|}\right)$$

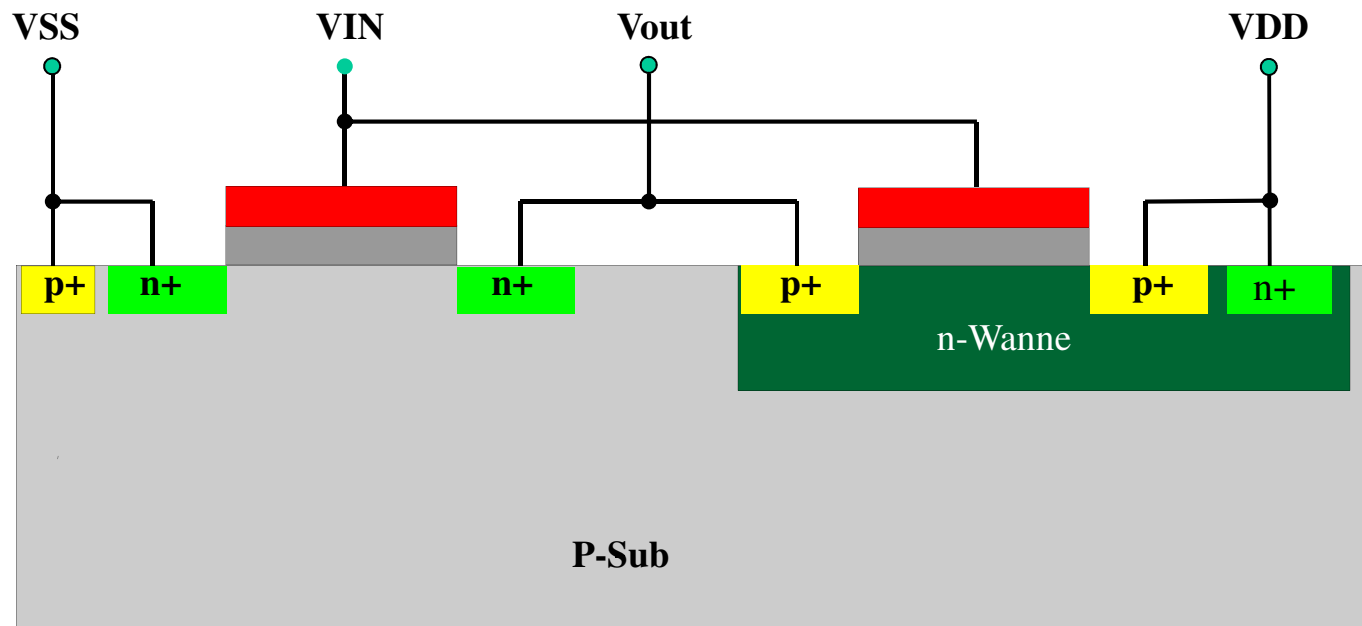
Implementation of CMOS-Inverter in a wafer process





Layout

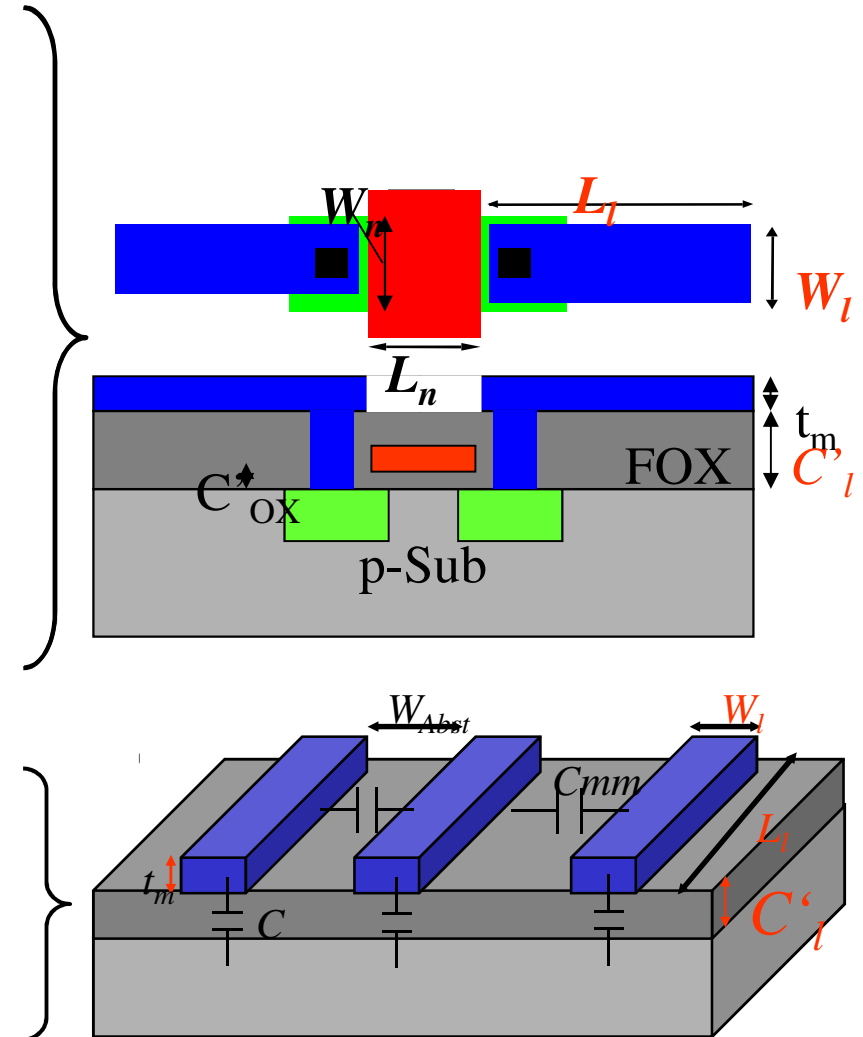 

 Pseudo-NMOS: P-Channel Transistor as Load




Pseudo-NMOS-Inverter

  

Transfer characteristics

Pseudo-NMOS-NOR

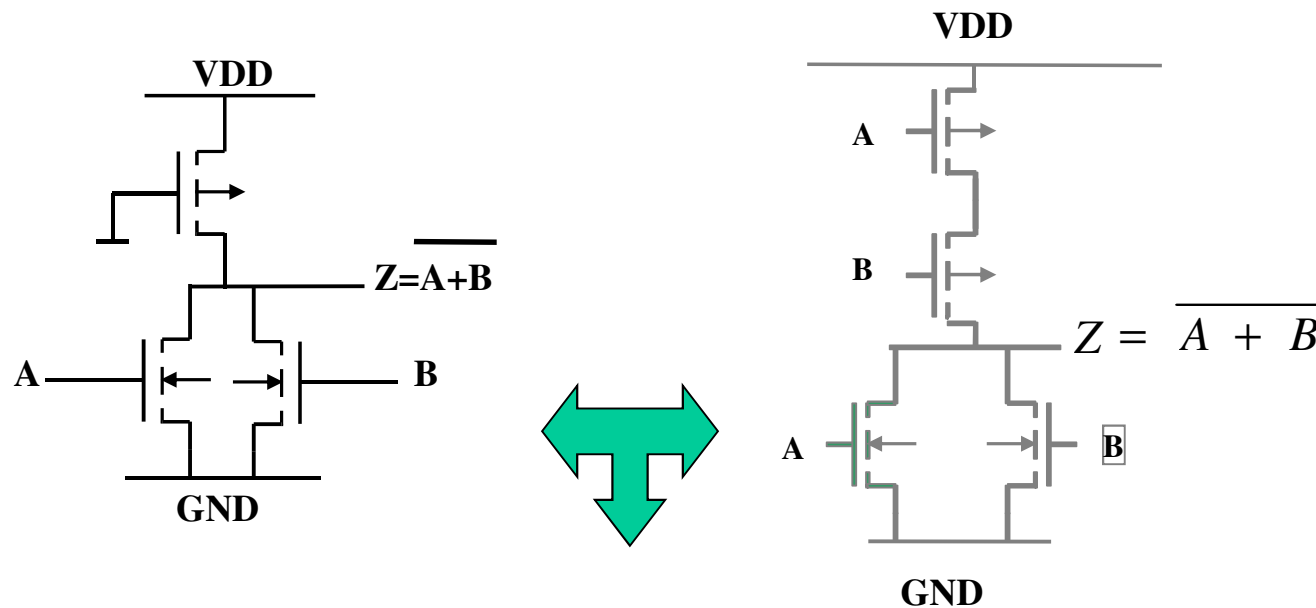

Disadvantage: **DC current at Low**

Advantages over standard CMOS NOR:

Lower size and higher speed

particularly with NOR with many inputs.

Chapter 4 Contents

- Introduction digital circuit technology
- Digital MOS-circuits
- CMOS - complementary MOS
- Pseudo-NMOS (p-channel-transistor as load)
- Delays
- Power Consumption