

Chapter15 Flipflop-Circuit

1. Counter
2. Register

Chapter 16 Memory

1. RAM - Random Access Memory
static RAM (SRAM)
dynamic RAM (DRAM)
2. NVM (non-volatile memory)
3. ROM - Read Only Memory

Standard Logic Devices

1. PLA – Programmable Logic-Arrays
2. FPGA

Digital Counters

Applications?

Counters are needed for:

Program counter

Event counter


Frequency divider

Microcontroller-embedded Systems

Sensors and Aktors, Programs (if i=x then ...)


Core Clock <> System Clock

 System clock may be a reference event (insusceptible to disturbances).





Thermally stabilized (TCXO)


Digital Counters

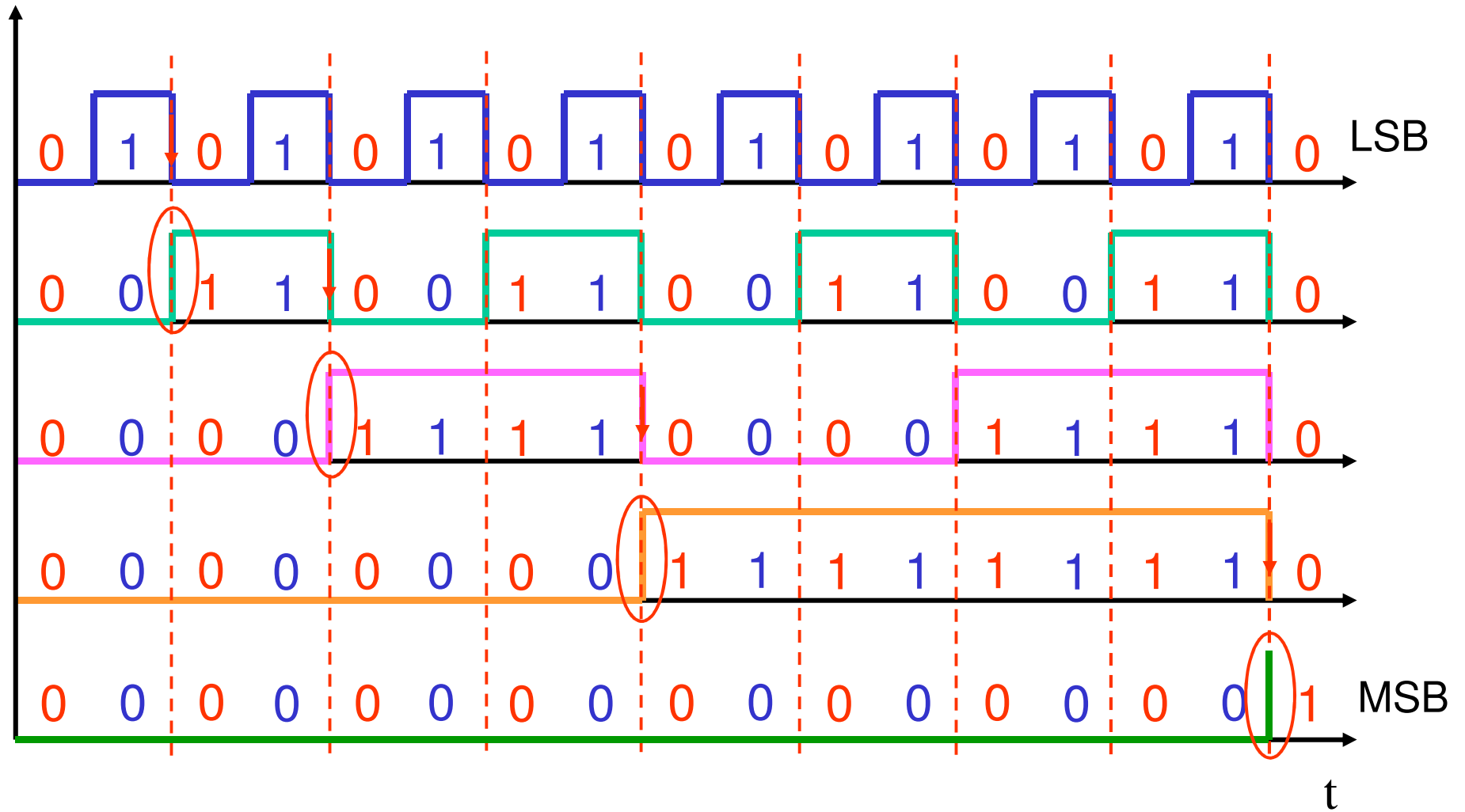


Digital Counter-Realization

 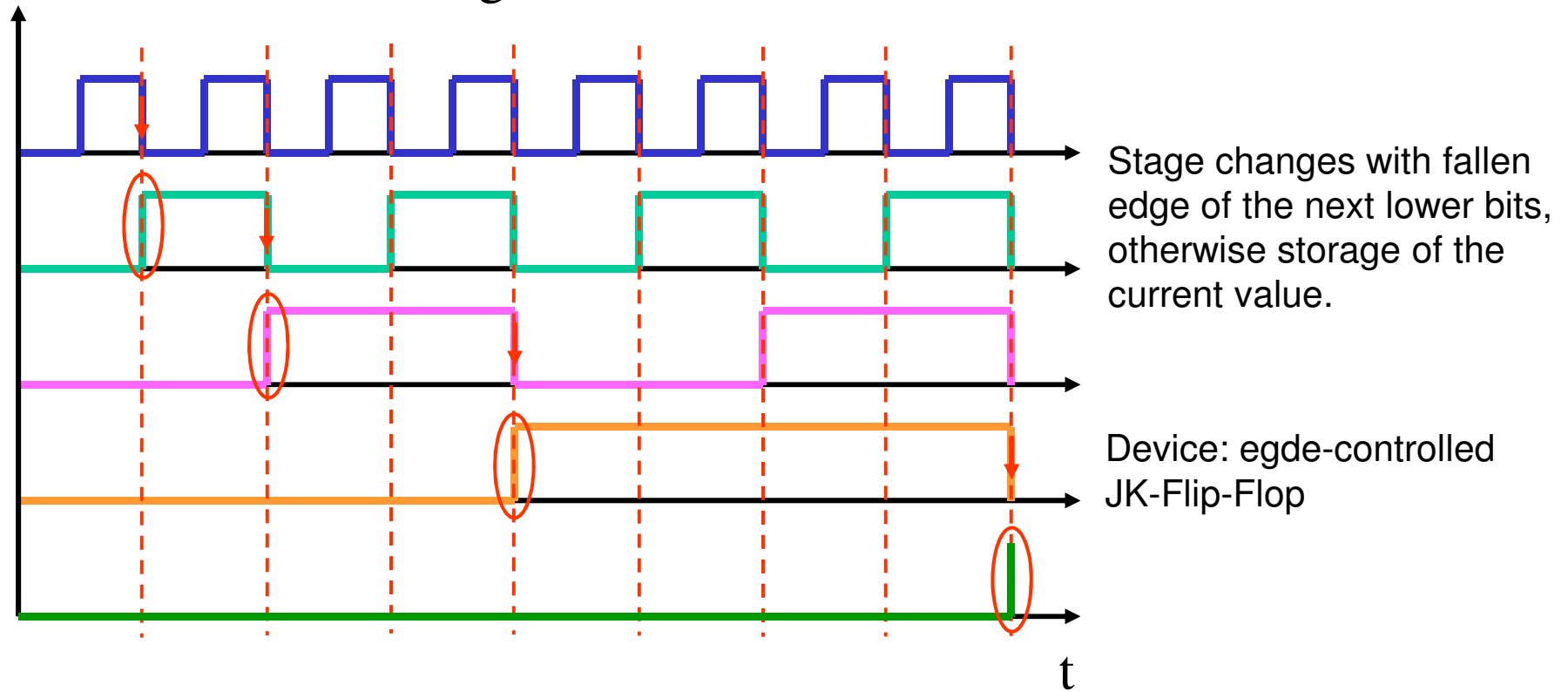

J	K	Q_n	Q_n
0	0	Q_{n-1}	Q_{n-1}
0	1	Q_{n-1}	0
1	0	Q_{n-1}	1
1	1	Q_{n-1}	$\overline{Q_{n-1}}$

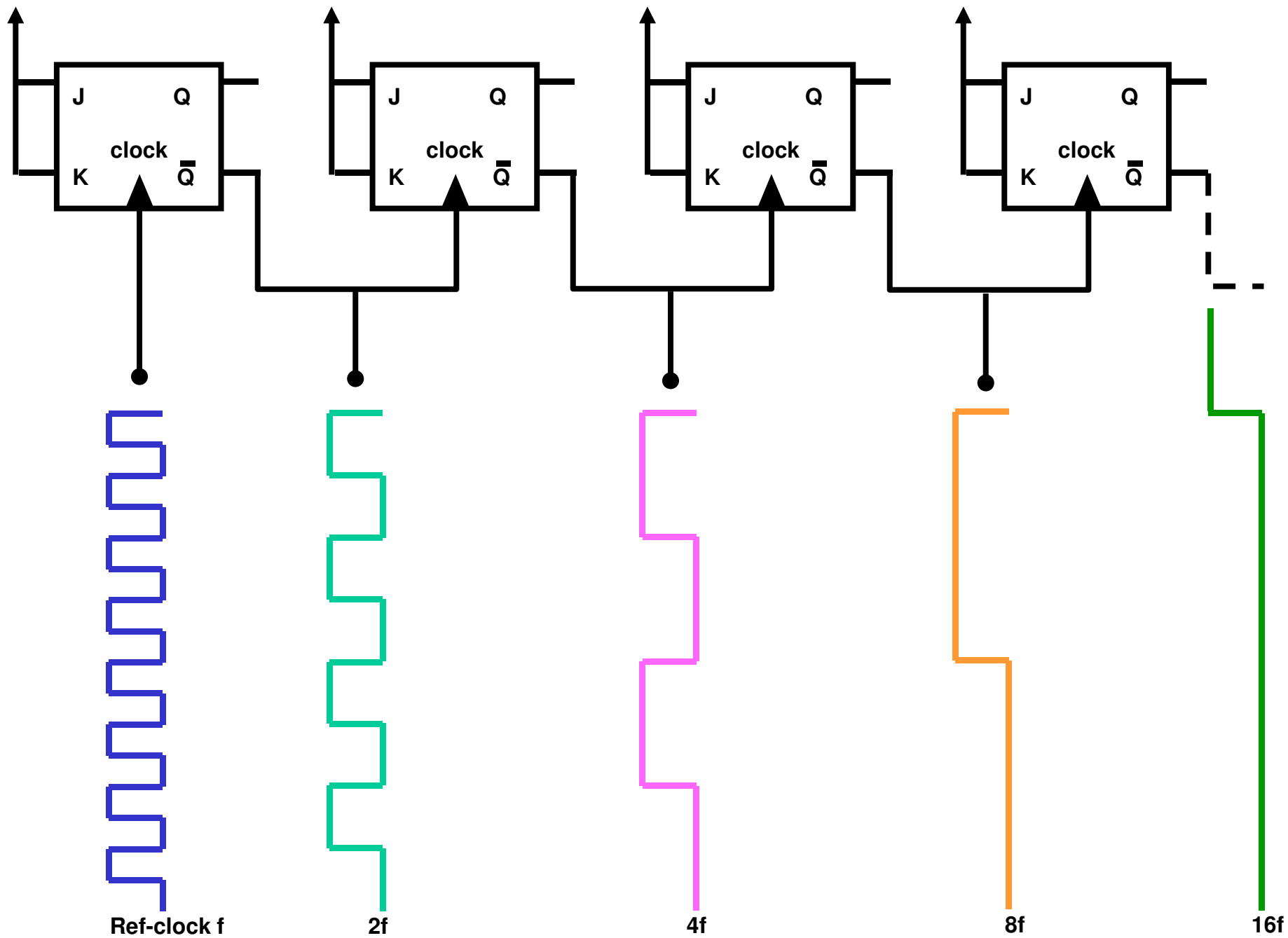



State storage

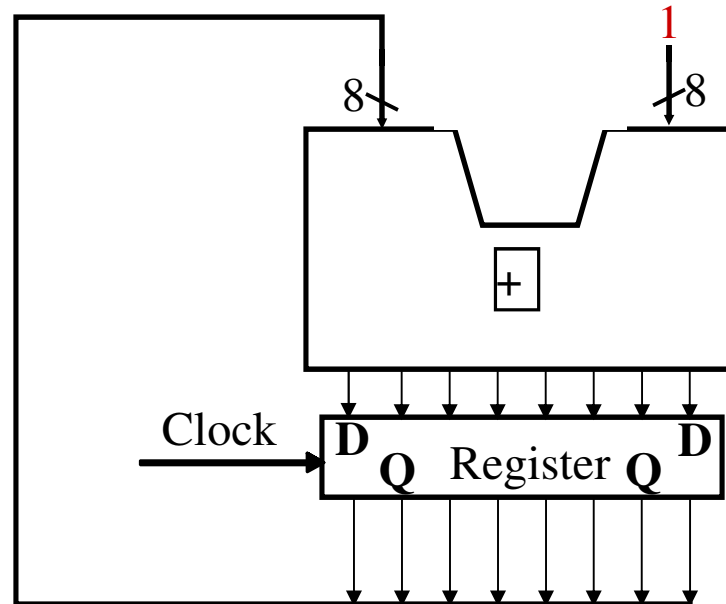


Accumulator / Incrementer

Parallel Register

Shift register (FIFO)

  

 FIFO memory with word width of 8 bit and depth of 7



Chapter15 Flipflop-Circuit

1. Counter
2. Register

Chapter 16 Memory

1. RAM - Random Access Memory
Static RAM (SRAM)
Dynamic RAM (DRAM)
2. NVM (non-volatile memory)
3. ROM - Read Only Memory



Standard Logic Devices

1. PLA - Programmable Logic-Arrays
2. FPGA


Pentium 4



Schematic Structure of a Memory-Array

  


Schematic Structure of a RAM

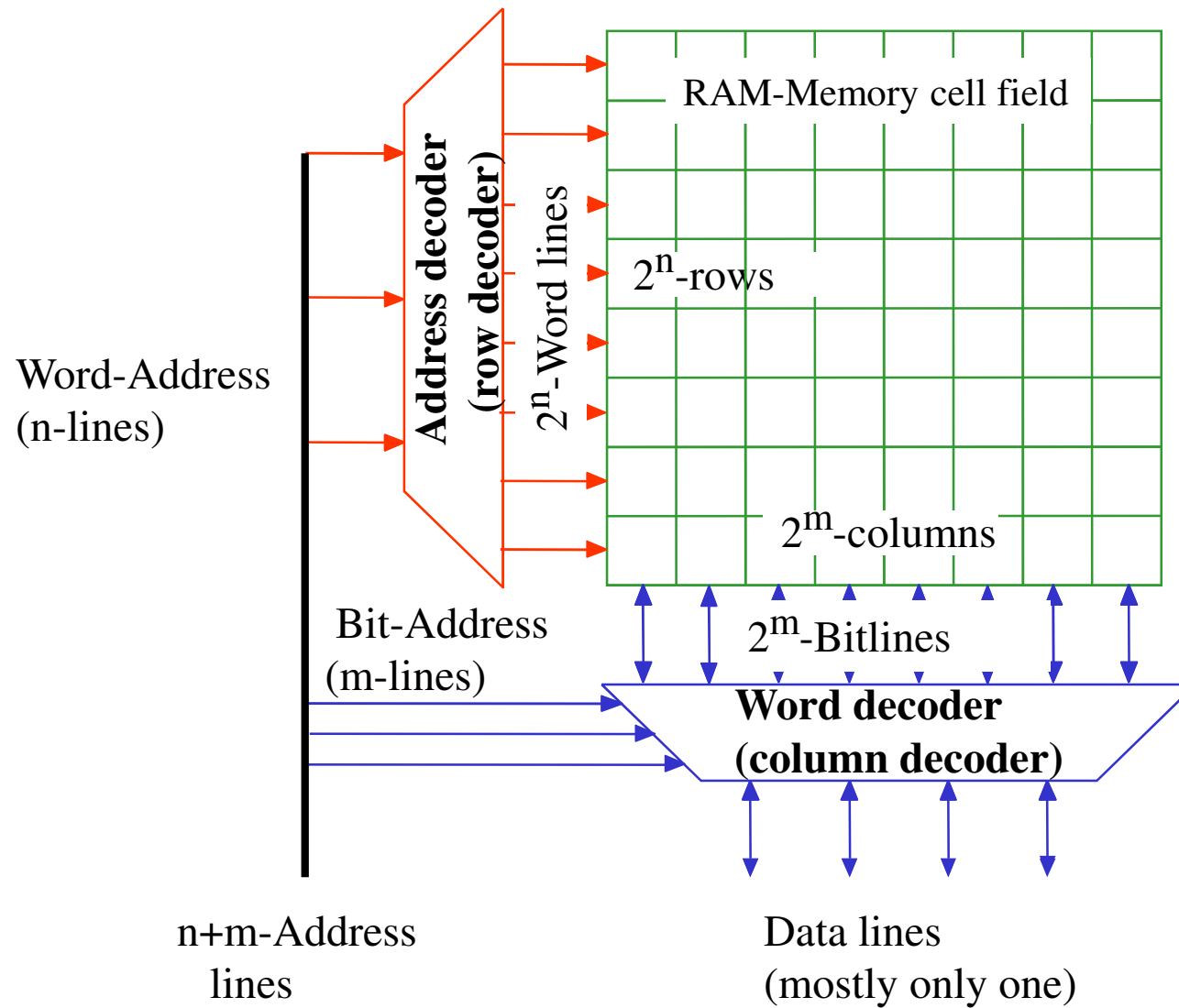


Functional Structure of a Row Decoder


Word-Address
(n-lines)

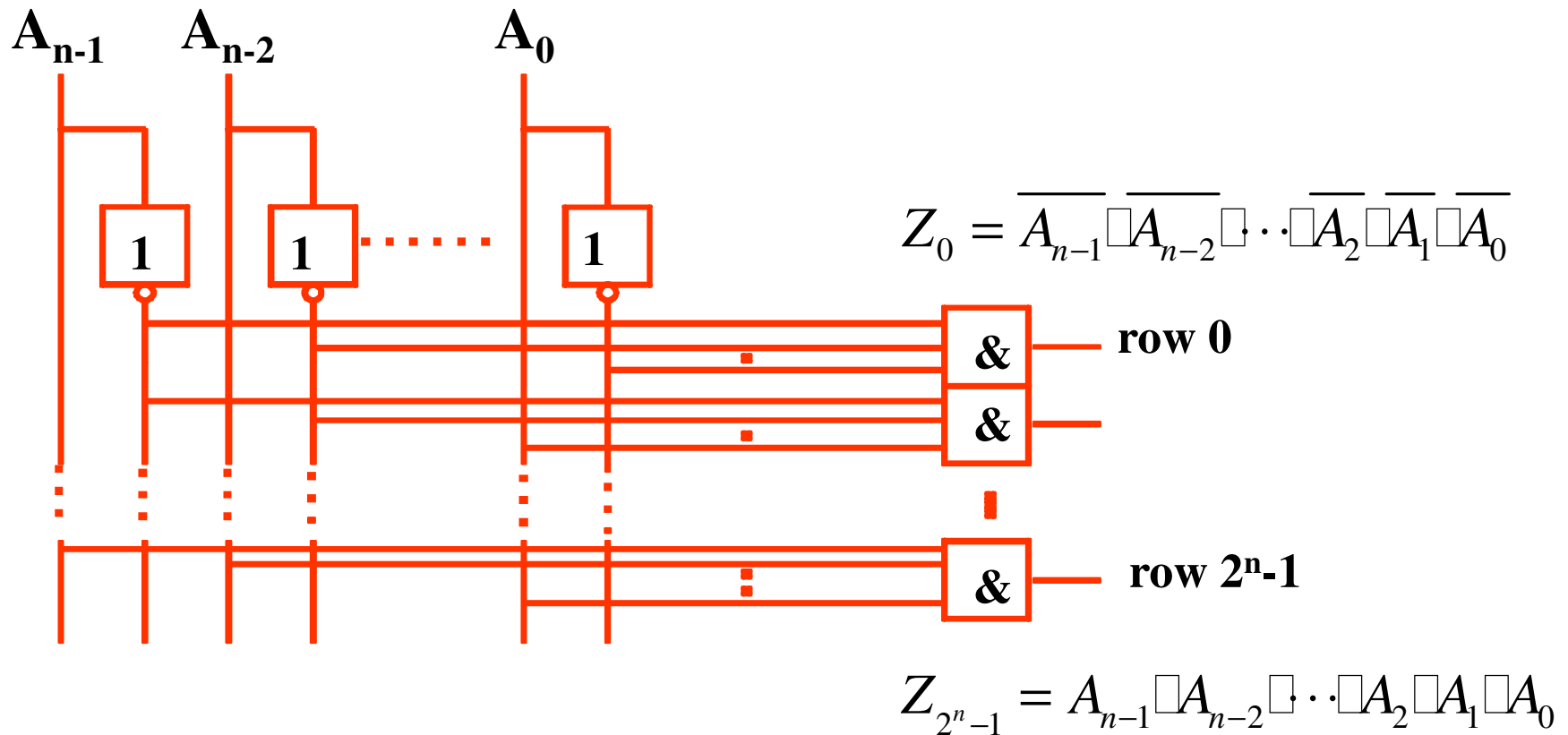

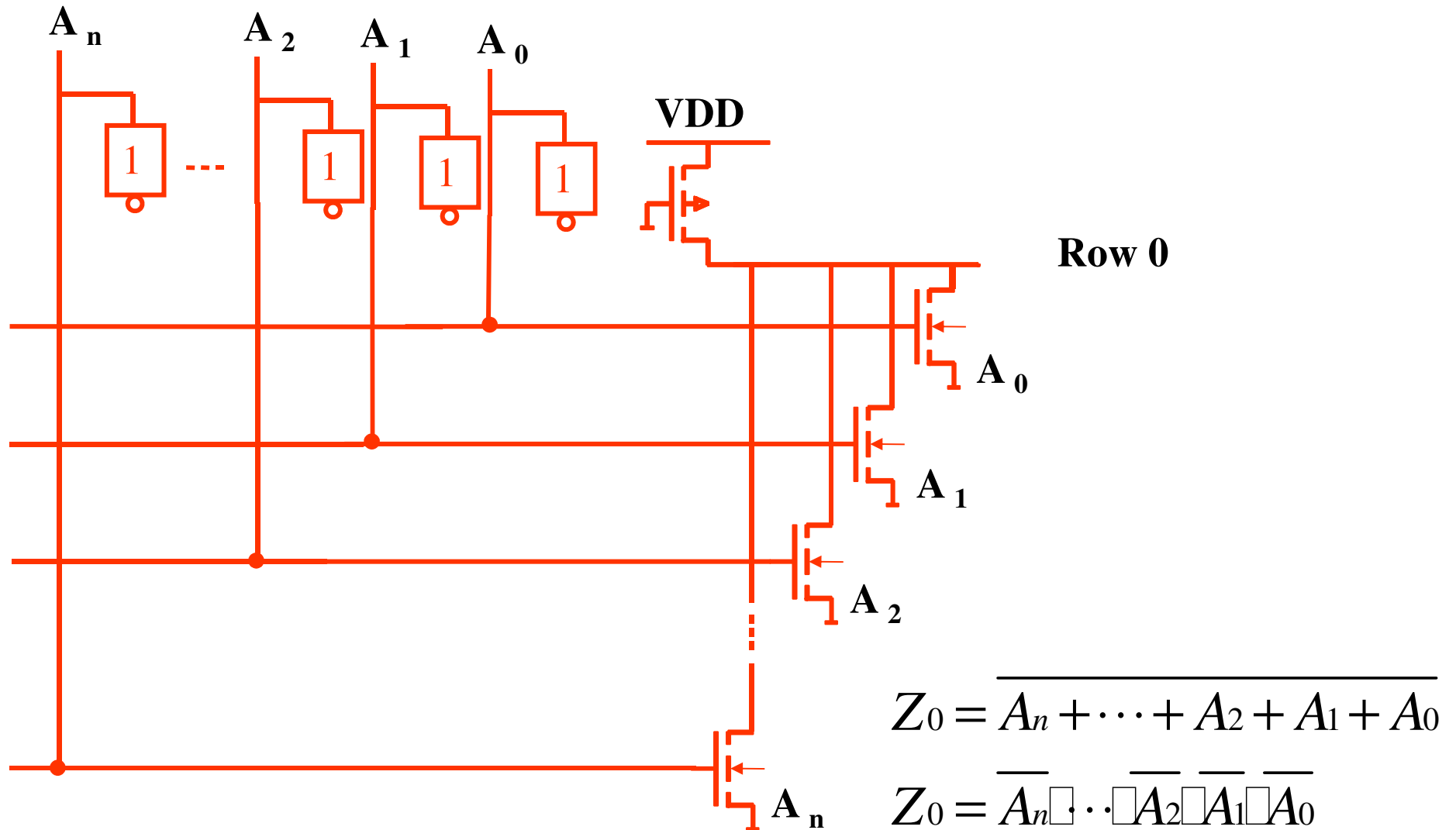
Structure of a NOR in Row Decoder for row 0



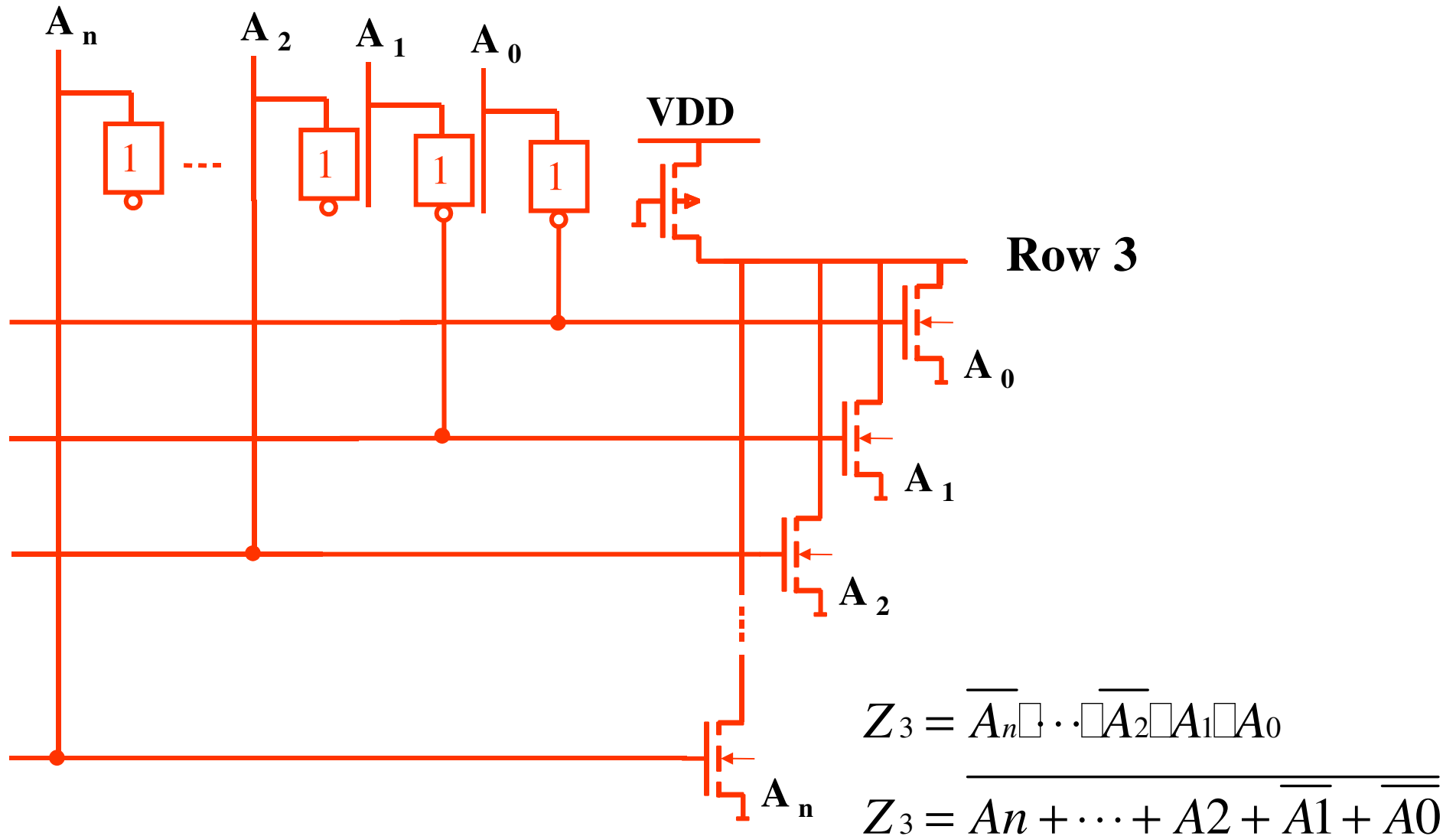Structure of a NOR in Row Decoder for row 3




Structure of a Column Decoder

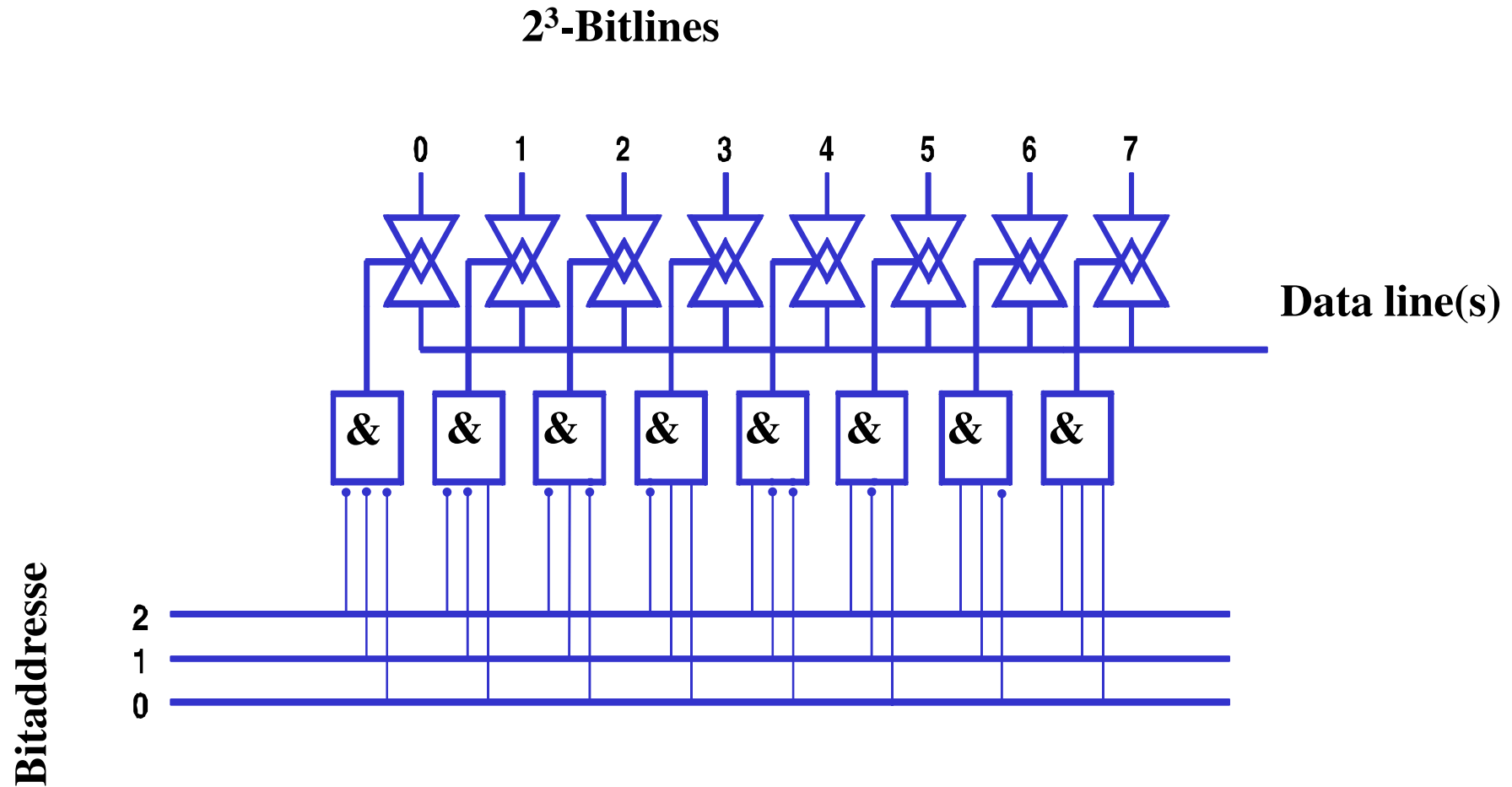


2^n Transmission Gate and 2^n AND with n-inputs

Column Decoder as Multiplexer

2^3 -Bitlines

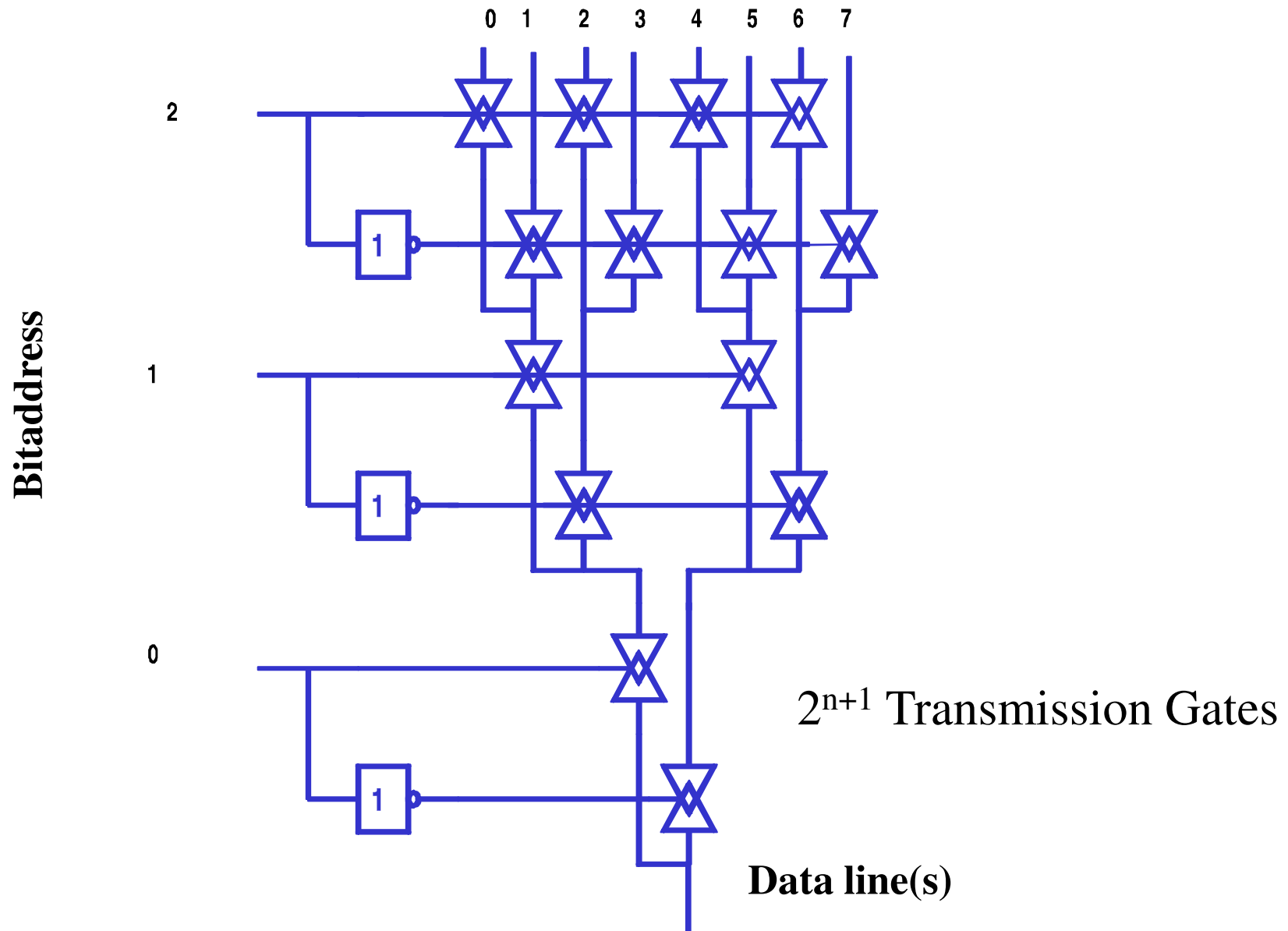

RAM-Cells - Static

 

Static 6-Transistor-RAM-Cell


$WR_j = 1$ Select read and write
 $WR_j = 0$ no activity, only storage

For writing: $Q = \text{Bit}$, Latch is overturned


For reading: $Q = 0 \Rightarrow \text{Bit} = 0; 1 > \overline{\text{Bit}} > 0$

$Q = 1 \Rightarrow 1 > \text{Bit} > 0; \overline{\text{Bit}} = 0$

Read-Write-Circuit

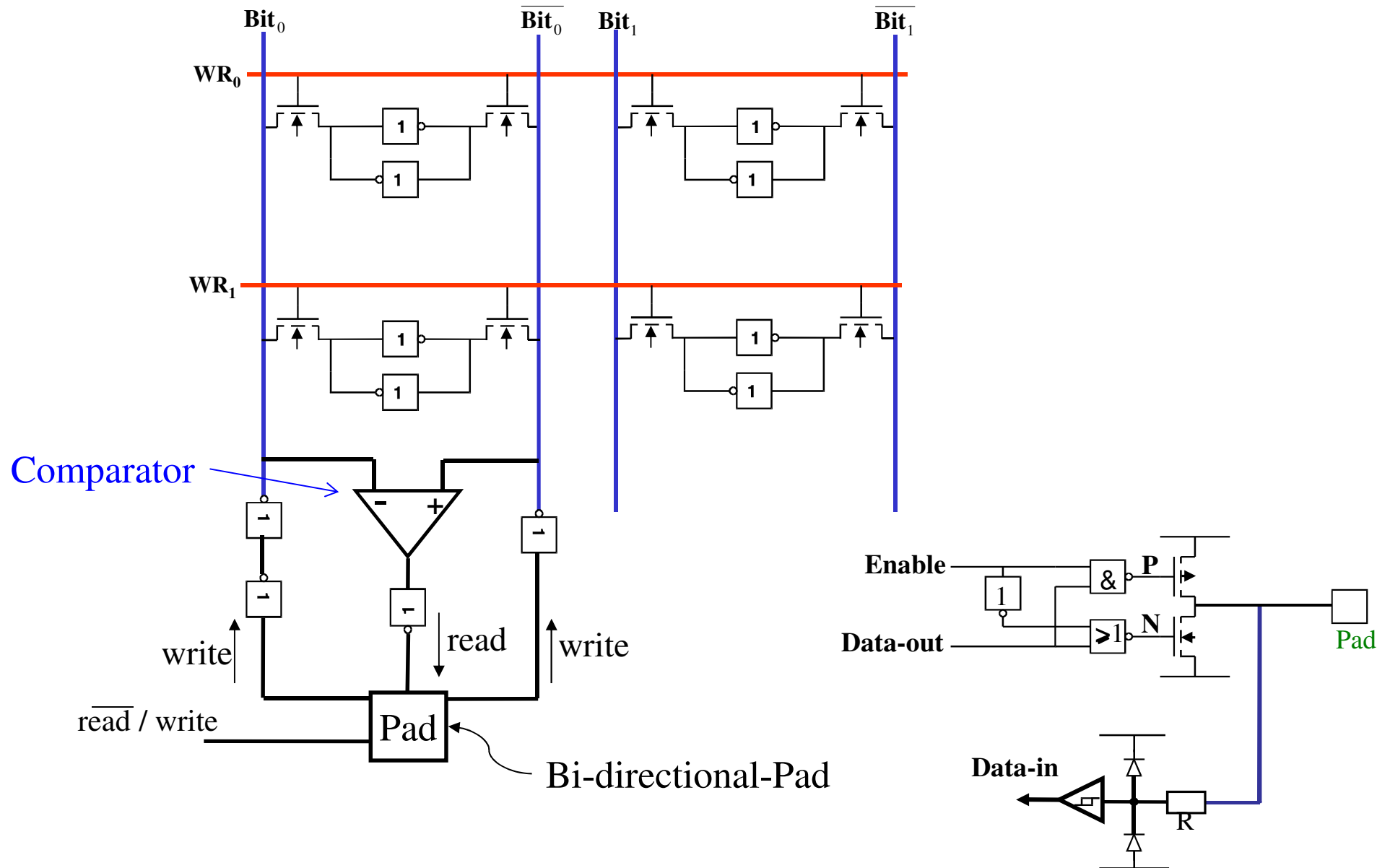


SRAM-Cell-Layout

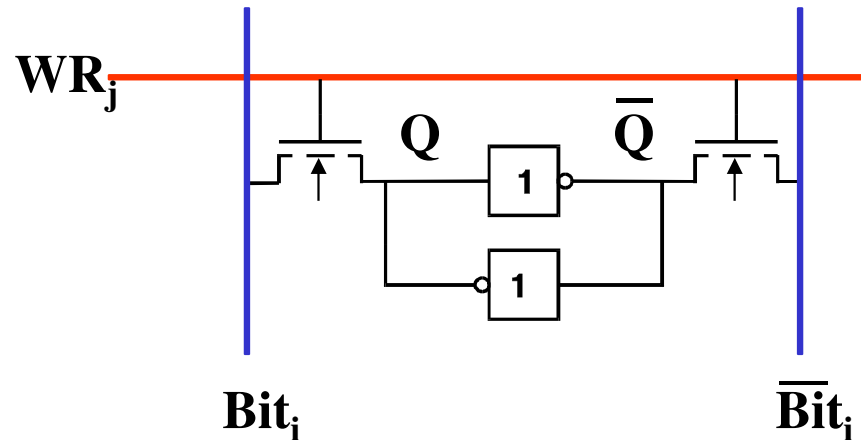


Specifics:

 - extremely dense
- **general Design Rules are violated**
- SRAM designs are produced by Generator SW. Inputs: size, form, connections etc.
Supplier: IP Vendor
- SRAM cell is the mostly used unit in a digital chip!




4T- SRAM-Cells

 

+ smaller area ?
- static current

Static 4-Transistor-RAM-Cell

RAM-Cells - Dynamic

 


+ smaller area
- „refresh“ necessary


Dynamic 4-Transistor-RAM-Cell

How could the cell be minimized ?



Dynamic 1-Transistor-RAM-Cell

 

 - + smaller area
- susceptible to disturbance
- loss of charge while reading



  Trench-Condensator Realizations of Dynamic 1-Transistor Cell



A specific (Trench-) Process required.

NVM: Non-Volatile Memory

RAM: no storage, once the **supply is interrupted**.

ROM: **not programmable**.

NVM: non-volatile memory

Previous name:	PROM (Programmable ROM) EEPROM (electrically erasable PROM)
----------------	--

Current name:	OTP (one-time programmable) MTP (many-time programmable)
---------------	---

Special Process:	Flash Memory
------------------	--------------

Basic principle of NVM

Floating Gate as Memory

Programming by high electrical field in oxide
(Fowler-Nordheim Tunnel effect, Hot Carrier Injection)

Reading by cell current

Specifics of NVM


Programming / Method: **High voltage necessary**
(e.g.: 7V for 7 nm gate oxide),
Defined (slow) Transient

Quality: **Data Retention** (e.g. 10 years)
 Endurance (e.g.: 10 K programming)

Testing: Programming -> Baking -> Retest

Redundancy: install more bits, to detect and correct failures

EEPROM (MTP)

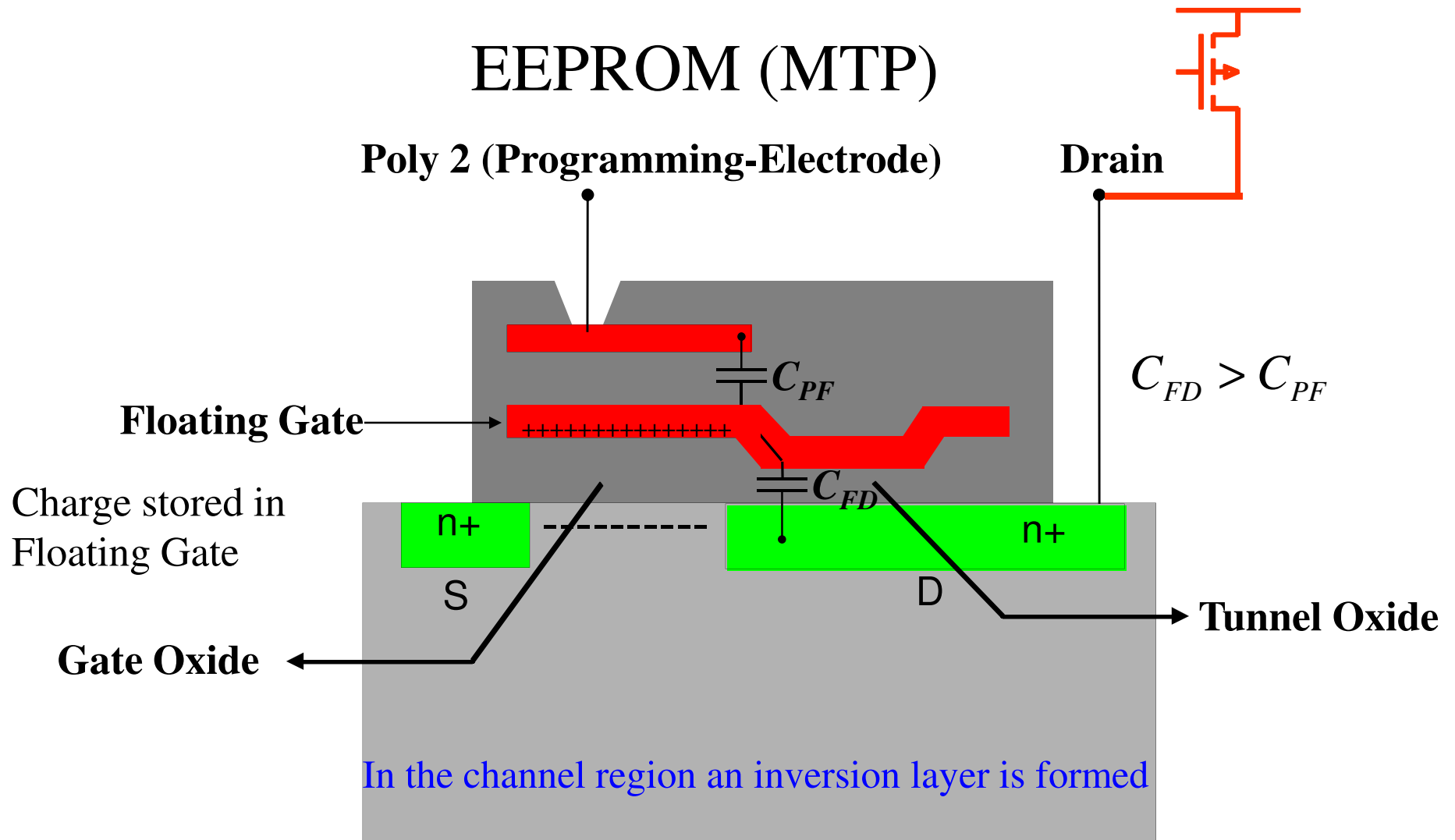


Between Drain- and Programming-Electrode a Programming Voltage V_{pp} can be applied.

Cell current is read out.

In modern OTP/MTP the cell is realized lateral.

Cross section of a Flash-Storage Cell

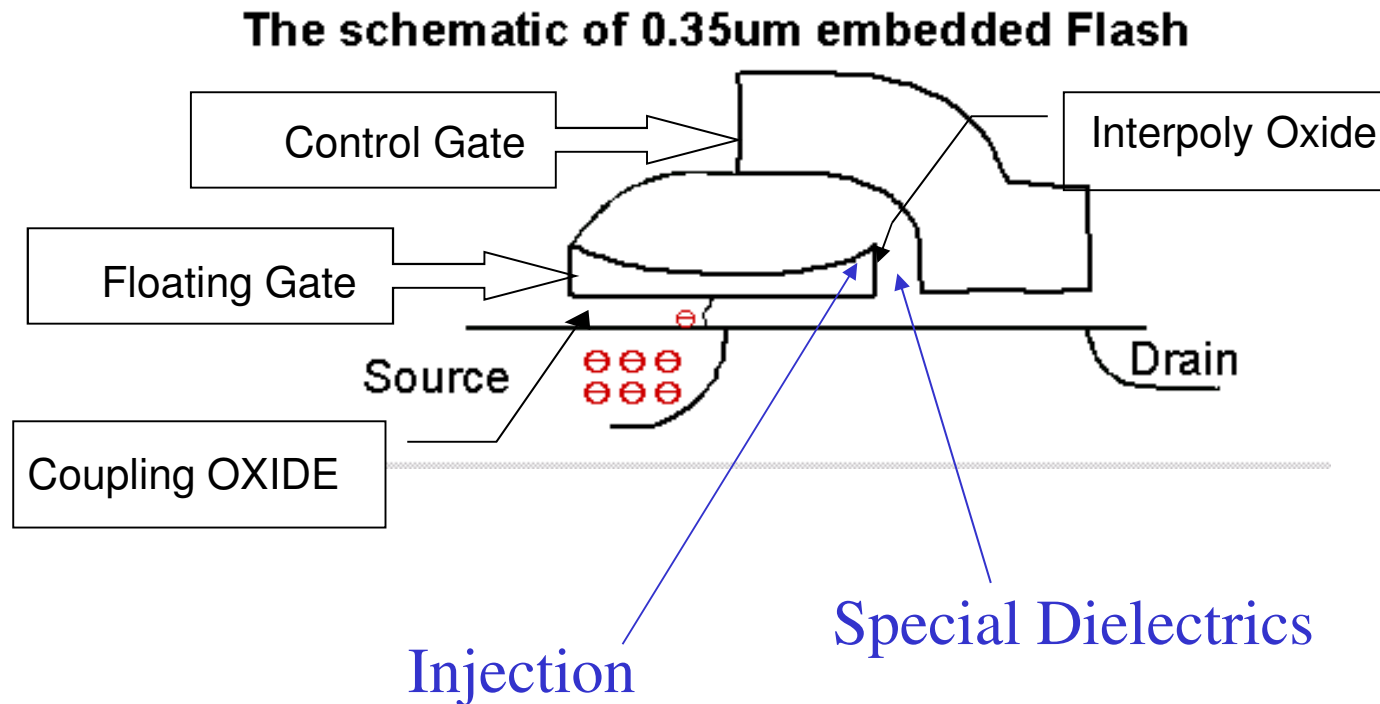

Flash needs a special process.

For system on a chip: **embedded flash process**
(ca. 30 % more expensive than standard CMOS process).

Comparison Memory-Technologies

Type	Density	Access Time	Energy per Bit for writing	Retention	Endurance
SRAM	1	1	1	as long as supply is active	infinite
DRAM	10	20	10	<< 1 second, refresh required	infinite
Flash	30	200000	0.05	10 years	10000

Implementations

- SRAM: Standard CMOS, integrated/embedded
- DRAM: DRAM Process, discrete chip
- Flash: Flash Process, own device

Comparison SRAM – DRAM – NVM

SRAM	<ul style="list-style-type: none">+ fast+ in standard process always available- large
DRAM	<ul style="list-style-type: none">+ high storage density- slow- special process, thus rarely embedded DRAM
OTP / MTP	<ul style="list-style-type: none">+ in standard process with medium thick gate oxide (e.g. 7 nm) feasible- very large- extremely slow programming
Flash	<ul style="list-style-type: none">+ high storage density- expensive- extremely slow programming